

s-parameter

N part network

→ Incident sgl $\Rightarrow v_n^+$ + reflected sgl $\Rightarrow v_n^-$

$$\begin{bmatrix} v_1^- \\ v_2^- \\ \vdots \\ v_N^- \end{bmatrix} = \begin{bmatrix} s_{11} & s_{12} & \dots & s_{1N} \\ s_{21} & s_{22} & \dots & s_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ s_{N1} & s_{N2} & \dots & s_{NN} \end{bmatrix} \begin{bmatrix} v_1^+ \\ v_2^+ \\ \vdots \\ v_N^+ \end{bmatrix}$$

For 2 part network

$$\begin{bmatrix} v_1^- \\ v_2^- \end{bmatrix} = \begin{bmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{bmatrix} \begin{bmatrix} v_1^+ \\ v_2^+ \end{bmatrix}$$

Impedance is characterised into z_0 then

$v = p$

$$p = \frac{v^2}{R} = vI = v\left(\frac{v}{R}\right)$$


$$\frac{P_1}{P_2} = \frac{V_1^2}{V_2^2} \text{ provided same } R \text{ (Impedance)}$$

$$[v_n^-] = [s][v_n^+]$$


$$s_{ij} = \frac{v_i^-}{v_j^+} \quad s_{ij} = \frac{v_i^-}{v_j^+} \quad v_k^+ = 0; k \neq j$$

↑
observed part ↑
Incident point

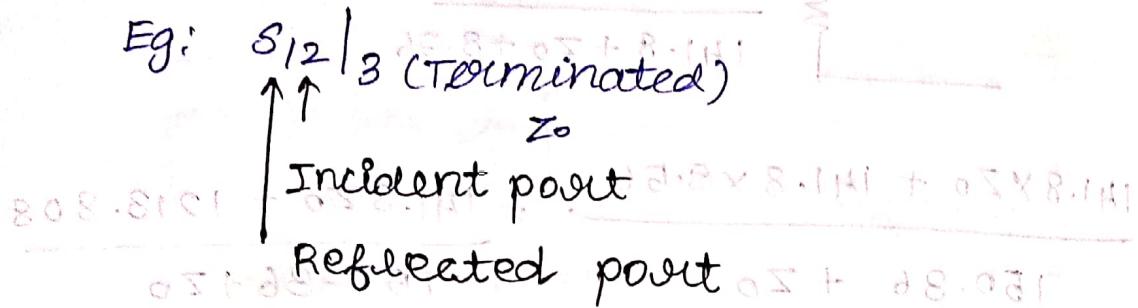means Terminated with Z_0 , no reflection back.



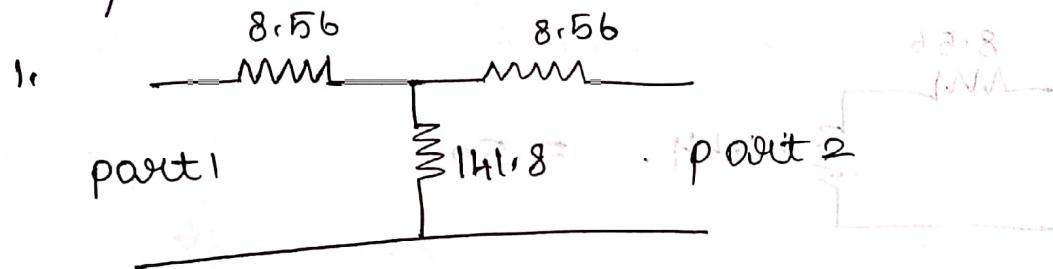
part 1 \rightarrow part 2 \rightarrow part 3 terminated.
superheterodyne principle & parts at
idle with termination for directional
coupler



$$\text{For } S_{11} = \frac{V_1^-}{V_1^+} \mid v_2^+ = 0 = |T| = \text{Reflection coefficient}$$

$$T = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \mid v_2^+ = 0$$

Z_{in} terminated with Z_0 .

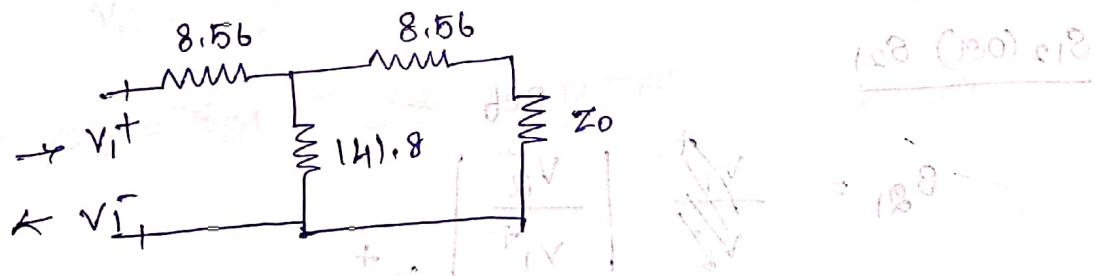

$Z_0 + 8.56$ primary stub w/ load
primary w/ load
primary w/ load
load w/ load

most dominant
primary stub w/ load
primary w/ load
load w/ load

load w/ load


$$\frac{(141.8)(Z_0 + 8.56)}{141.8 + Z_0 + 8.56}$$

$$\frac{141.8 \times Z_0 + 141.8 \times 8.56}{150.36 + Z_0} = \frac{141.8 Z_0 + 1218.808}{150.36 + Z_0}$$

$$Z_0 = 50 \Omega$$

$$= \frac{7090 + 1218.808}{200.86} = 8803.808$$

$$= 41.444,$$

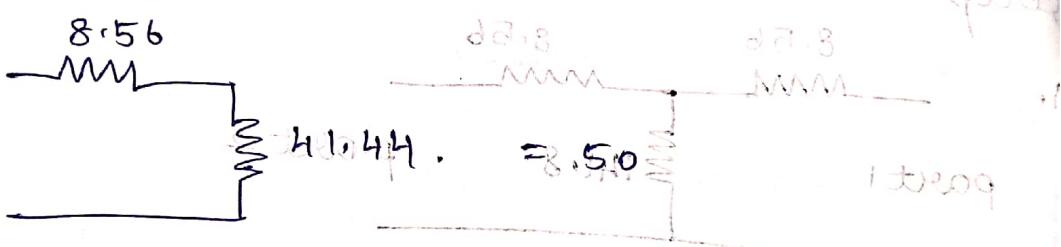

$$Z_{in}^{(1)} = 50 \Omega$$

$$S_{11} = \frac{Z_{in}^{(1)} - Z_0}{Z_{in}^{(1)} + Z_0} = 0$$


$$S_{11} = S_{22} = 0 \text{ (dilnear network)}$$

$$S_{12}(0\Omega) S_{21}$$

$$S_{21} = \frac{V_1^+}{V_2^-}$$

Ref


Inc

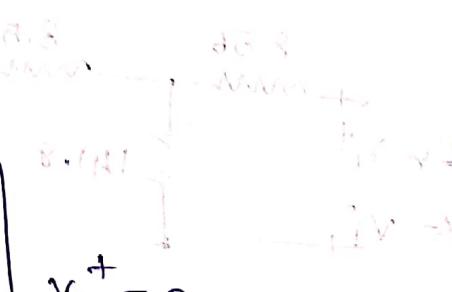

mismatch from
load produce standing
waves terminating
sgl will not reflect
back

CNO Incident
Sgl from V2
(Terminated
with Z0)

$v_1^+ = v_1$ and $v_2^- = v_2$ if α

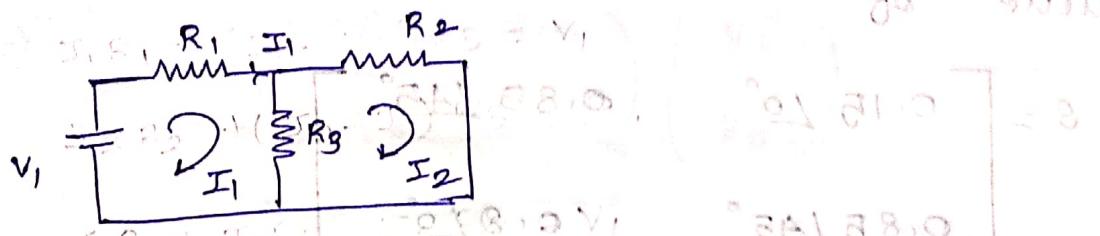

current division

$$I_2 = \frac{I_1 R_3}{R_3 + R_2}$$

~~at 3. 9. 1972~~ ~~in the way of~~
~~To the following notes oral. statement~~
Voltage division

Voltage division

$$VR_2 = \frac{V_1 R_2}{R_1 + R_2}$$

$$I \text{ block } R_0 = 880 \Omega, (R_2 + R_3) = 100 \Omega$$

~~Coloring~~ 821 ~~lives~~ ~~now~~ ~~is~~ ~~growing~~ ~~in~~ ~~the~~ ~~forest~~ ~~near~~ ~~the~~ ~~river~~ ~~and~~ ~~the~~ ~~waterfall~~ ~~is~~ ~~very~~ ~~old~~ ~~and~~ ~~big~~ ~~it~~ ~~has~~ ~~a~~ ~~long~~ ~~trunk~~ ~~and~~ ~~thin~~ ~~limbs~~ ~~it~~ ~~is~~ ~~green~~ ~~and~~ ~~yellow~~ ~~and~~ ~~red~~ ~~it~~ ~~is~~ ~~very~~ ~~big~~ ~~it~~ ~~is~~ ~~the~~ ~~biggest~~ ~~tree~~ ~~in~~ ~~the~~ ~~forest~~ ~~it~~ ~~is~~ ~~the~~ ~~biggest~~ ~~tree~~ ~~in~~ ~~the~~ ~~forest~~

$$\frac{V_2}{R_2 + R_3} = \frac{V_1 R_2}{R_2 + R_3}$$

$$V_2 = \left(\frac{41,44}{41,44 + 8,5} \right) \cdot \left(\frac{50}{50 + 8,5} \right) V_1$$

$$V_2 = \frac{0.707 V_1}{(2\pi f_{crossover} Q_2)^2 + (Q_1 Q_2)^2}$$

$$S_{12} = S_{21} = \frac{V_2}{V_1} = \frac{0.707 V_1}{V_1} = 0.707$$

$$S_{12} = S_{21} = -3 \text{ dB} = 20 \log (0.707)$$

Hence it is a 3dB attenuator (iii)

$$\text{dinear } N/W = (S_{11})^2 + (S_{22})^2 = 1$$

If (3dB for $S_{12}, S_{21} \Rightarrow$ Amplifier)

Q. The Network has - S parameter
value of

$$S = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle 45^\circ \\ 0.85 \angle 45^\circ & 0.12 \angle 0^\circ \end{bmatrix}$$

- i) determine whether linear or not
- ii) If part 2 is terminated with matched load what might be its return loss.
- iii) If part 2 is shorted what will be the impact of return loss on part 1
- iv) $V_2^+ = -V_2^-$ (standing wave will generate)
- v) $RL = -20 \log (\Gamma)$
 $= -20 \log (811)$

i) Linear Network - $|S_{11}|^2 + |S_{22}|^2 = 1$

$$|S_{11}|^2 + |S_{22}|^2 = 1$$

$$(0.15)^2 + (0.12)^2 = 0.0225 + 0.04 = 0.0625$$

$$\text{Ratio} = \frac{0.0625}{1} = 0.0625$$

Hence not linear system

ii) $RL = -20 \log (\Gamma)$
 $= -20 \log (811)$
 $(= -20 \log (0.15))$

$$R_L = 16.478 \text{ dB}$$

(iii) $\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^+ \end{pmatrix}$

$$V_2^+ = -V_2^-$$

$\begin{pmatrix} V_1^- \\ V_2^- \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} V_1^+ \\ -V_2^+ \end{pmatrix}$

$$V_1^- = S_{11} V_1^+ - S_{12} V_2^+ \quad (1)$$

$$V_2^- = S_{21} V_1^+ - S_{22} V_2^+ \quad (2)$$

From (2)

$$V_2^- + S_{22} V_2^+ = S_{21} V_1^+ \quad \text{cancel } V_2^+$$

$$V_2^- (1 + S_{22}) = S_{21} V_1^+ \quad \text{cancel } V_2^-$$

From (3) $V_2^- = \left(\frac{S_{21}}{1 + S_{22}} \right) V_1^+ \quad \text{cancel } V_2^-$

Now $V_1^- = S_{11} V_1^+ - S_{12} \left(\frac{S_{21}}{1 + S_{22}} \right) V_1^+ \quad \text{cancel } V_1^+$

$$V_1^- = S_{11} V_1^+ - \frac{S_{12} S_{21}}{1 + S_{22}} V_1^+ \quad \text{cancel } V_1^+$$

$$\frac{V_1^-}{V_1^+} = S_{11} - \frac{S_{12} S_{21}}{1 + S_{22}}$$

$$\begin{aligned}
 &= (0.15 \angle 0^\circ) - \frac{(0.85 \angle 45^\circ)(0.85 \angle 45^\circ)}{1 + 0.2 \angle 10^\circ} \\
 &= (0.15 \angle 0^\circ) - \frac{0.7225 \angle 90^\circ}{1.2 \angle 10^\circ} = \underline{\underline{0.15 \angle 0^\circ}}
 \end{aligned}$$

$$= 0.15 \angle 0^\circ - 0.602 \angle 90^\circ$$

$$= 0.15 - 0.602j = \underline{\underline{0.15 - 0.602j}}$$

$$T = 0.620$$

$$-20 \log(0.620) = 4.152 \text{ dB}$$

$$-20 \log(0.620) = 4.152 \text{ dB}$$

06.08.25

(2) more

signal Flow Graph

→ primary components:

- Nodes

part i has 2 nodes a_{ii} & b_{ii}


→ Node a_{ii} (wave entering part i)

→ Node b_{ii} (wave reflected from part i)


→ voltage at a node equal to sum of signals entering node

- Branch

Directed path between two nodes

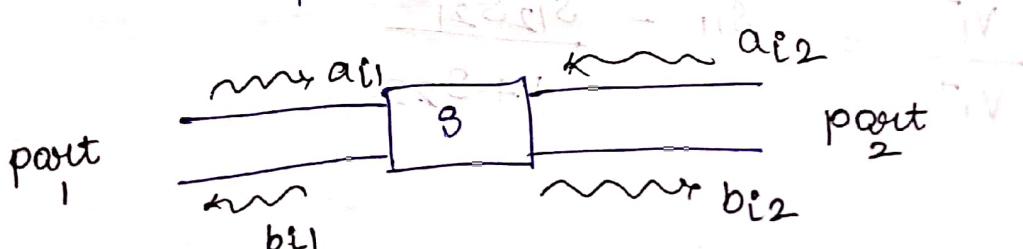


In SFG₁ of 3 port network

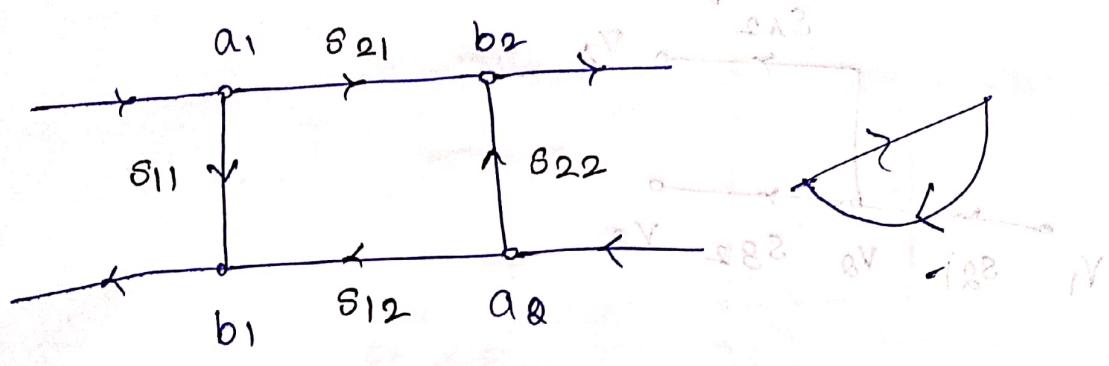


Mason's Rule

Rule: 1 series Rule

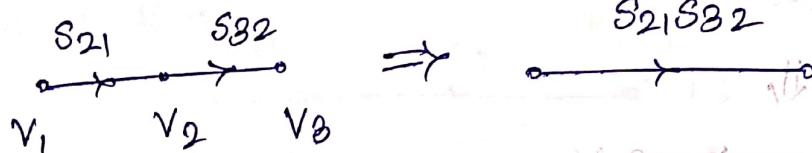


$$V_{23} = V_{123} - V_{132}$$

Rule: 2 parallel Rule

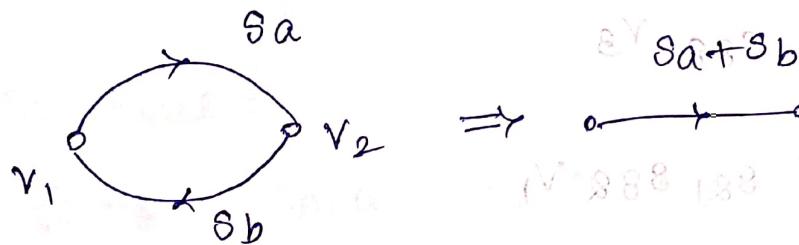


$$V_{23} = V_{123} - V_{132}$$

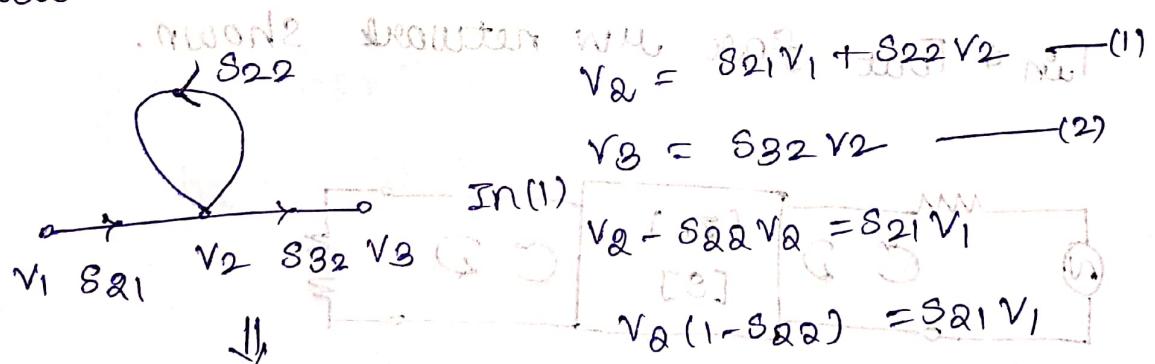Rule: 3 self loop rule, derived at 273 saw.



$$v_2 - s_{22}v_2 = s_{21}v_1$$

$$v_2(1 - s_{22}) = s_{21}v_1$$

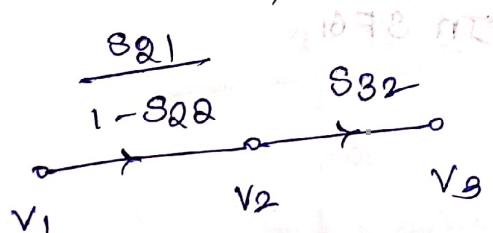


$$v_2 = \frac{s_{21}v_1}{1 - s_{22}}$$

IN (2)

$$v_3 = \frac{s_{32}s_{21}v_1}{1 - s_{22}}$$

Arecuring Req. & its PTE at


Rule 4: Splitting Rule

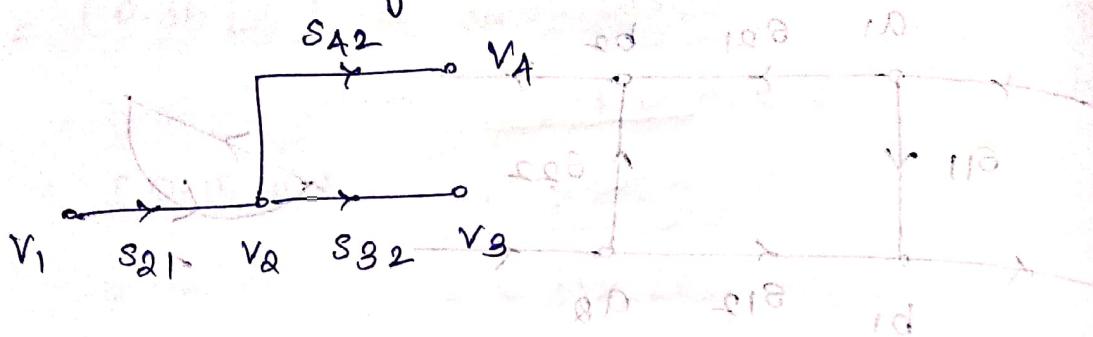

$$V_A = S_{42} V_2$$

$$\text{But } V_2 = S_{42} V_1$$

$$V_A = S_{42} S_{21} V_1$$

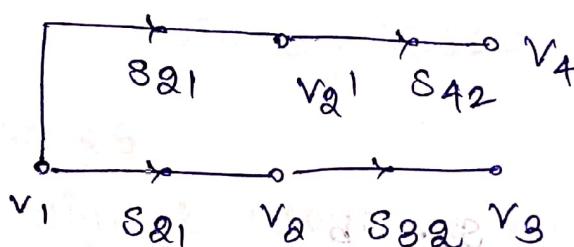


$$V_3 = S_{21} S_{32} V_1$$

1. Use SFG to derive expressions for

(1) T_{in} & T_{out} for MW network shown.

(2)

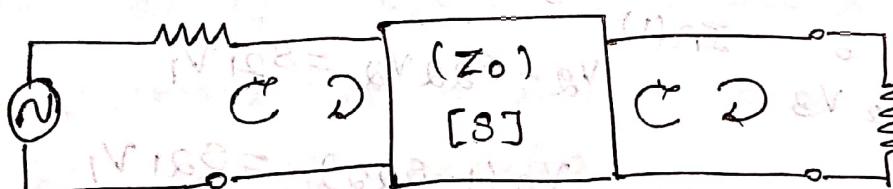


In SFG



$$V_{123} = 0$$


$$V_{123} = 0$$

The SFG is given as follows.

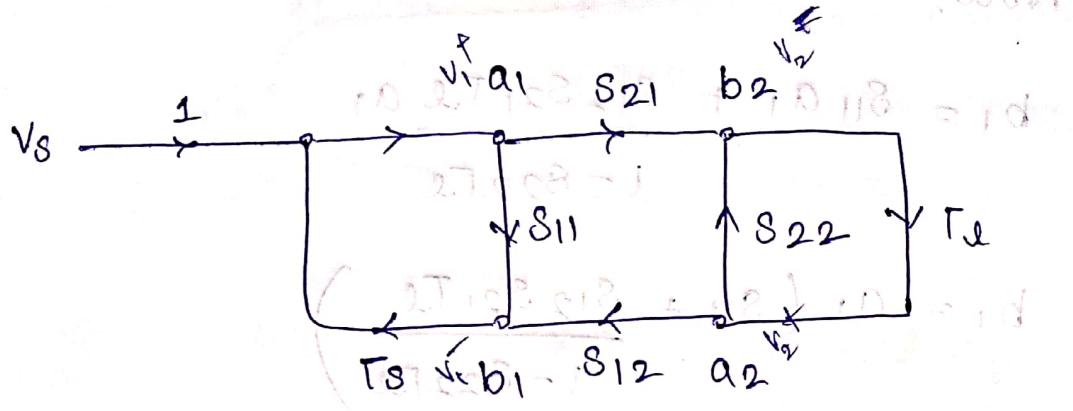

$$T_{in} = \frac{b_1}{a_1} + T_{out} = \frac{b_2}{a_2}$$

By Rule 1

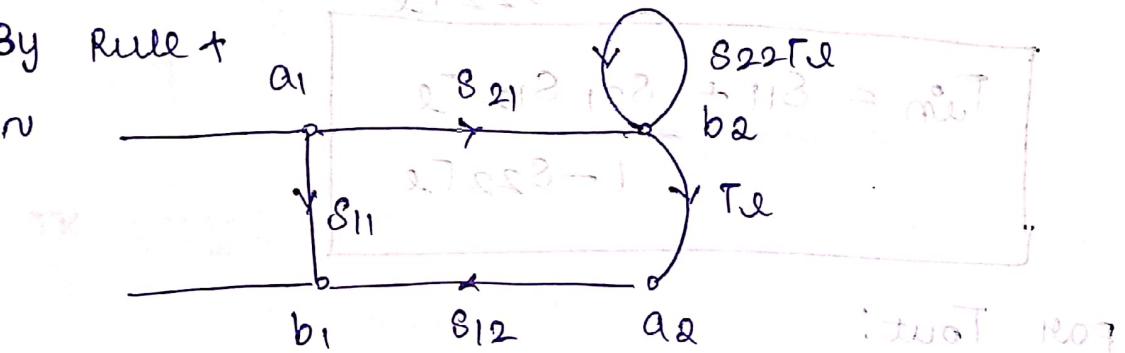

By Rule 3


$$\sqrt{b_2} = s_{21}a_1 + s_{22}T_{in}b_2$$

$$b_2 - s_{22}T_{in}b_2 = s_{21}a_1$$

$$b_2(1 - s_{22}T_{in}) = s_{21}a_1$$

$$b_2 = \frac{s_{21}a_1}{1 - s_{22}T_{in}}$$

$$1 - s_{22}T_{in} \neq 0$$

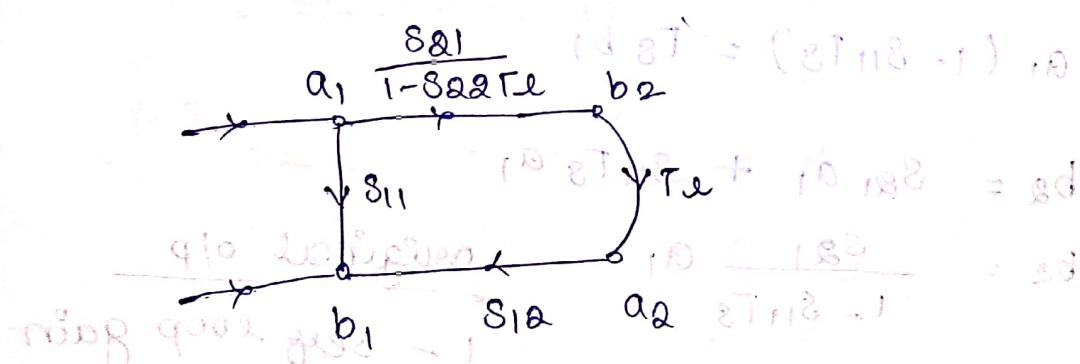

NOW:


$$b_1 = s_{11}a_1 + \frac{s_{12}s_{21}T_e a_1}{1 - s_{22}T_e}$$

$$b_1 = a_1 \left(s_{11} + \frac{s_{12}s_{21}T_e}{1 - s_{22}T_e} \right)$$

$$\frac{b_1}{a_1} = s_{11} + \frac{s_{12}s_{21}T_e}{1 - s_{22}T_e}$$

$$T_{in} = s_{11} + \frac{s_{21}s_{12}T_e}{1 - s_{22}T_e}$$

For T_{out} :

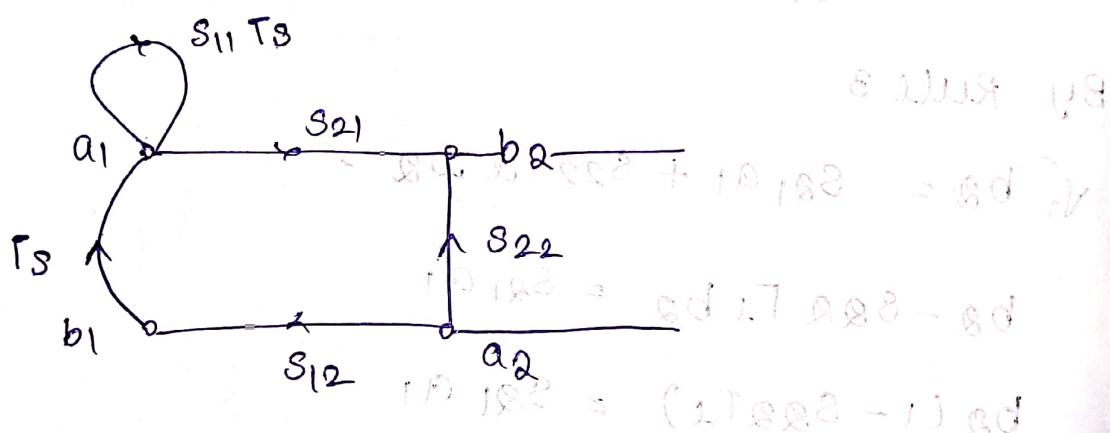

$$a_1 = T_s b_1 + s_{11} T_s a_1$$


$$a_1 - s_{11} T_s a_1 = T_s b_1$$

$$a_1 (1 - s_{11} T_s) = T_s b_1$$

$$b_2 = s_{21} a_1 + s_{12} T_s a_1$$

$$b_2 = \frac{s_{21}}{1 - s_{11} T_s} a_1$$

original o/p
1 - self loop gain

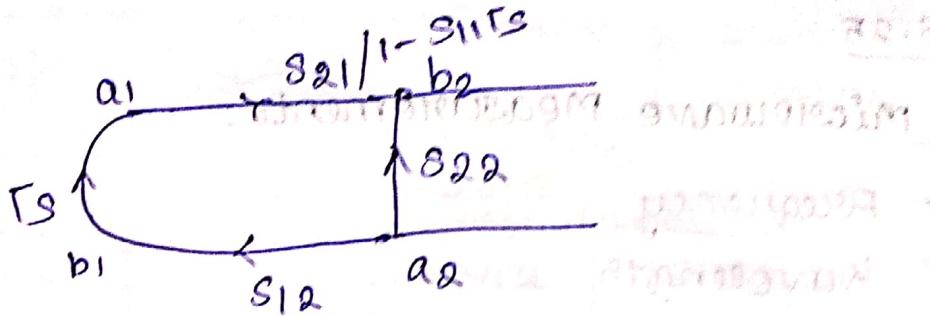

$$b_2 = S_{22} a_2 + \frac{S_{21} S_{12} T_3}{1 - S_{11} T_3} a_2$$

$$\boxed{\frac{b_2}{a_2} = S_{22} + \frac{S_{21} S_{12} T_3}{1 - S_{11} T_3}}$$

TX coefficient

$$\frac{b_2}{a_1} \text{ (or)} \quad \frac{b_1}{a_2}$$

$$\frac{b_2}{a_1} \Big|_{a_2=0} \quad \text{hence} \quad = \frac{S_{21}}{1 - S_{22} T_3}$$

$$\frac{b_1}{a_2} \Big|_{a_1=0} \Rightarrow b_1 = S_{11} T_3 b_1 + S_{22} a_2$$

$$\frac{b_1}{a_2} \Big|_{a_1=0} \quad b_1(1 - S_{11} T_3) = S_{12} a_2$$

$$\boxed{\frac{b_1}{a_2} = \frac{S_{12}}{1 - S_{11} T_3}}$$

$$b_1 = S_{11} a_1 + S_{12} a_2 \quad (1)$$

$$b_2 = S_{21} a_1 + S_{22} a_2 \quad (2)$$

$$(2) \Rightarrow b_2 = S_{21} a_1 + S_{22} T_e b_2$$

$$b_2 (1 - S_{22} T_e) = S_{21} a_1$$

$$\boxed{\frac{b_2}{a_1} = \frac{S_{21}}{1 - S_{22} T_e}}$$

12.08.25

Microwave Measurements:

- Frequency
- Wavelength
- VSWR
- Impedance
- power



Reflex → Isolator → Detector

Rejection

(safe from
or
Reflections)
[stops one
way only
 $I_{in} \rightarrow O_{out}$]

any MW
other


RF
power
Supply


$$27 + 12 + 18 = 57$$

dB

$$\frac{10}{10} \text{ dB}$$

Bench set up

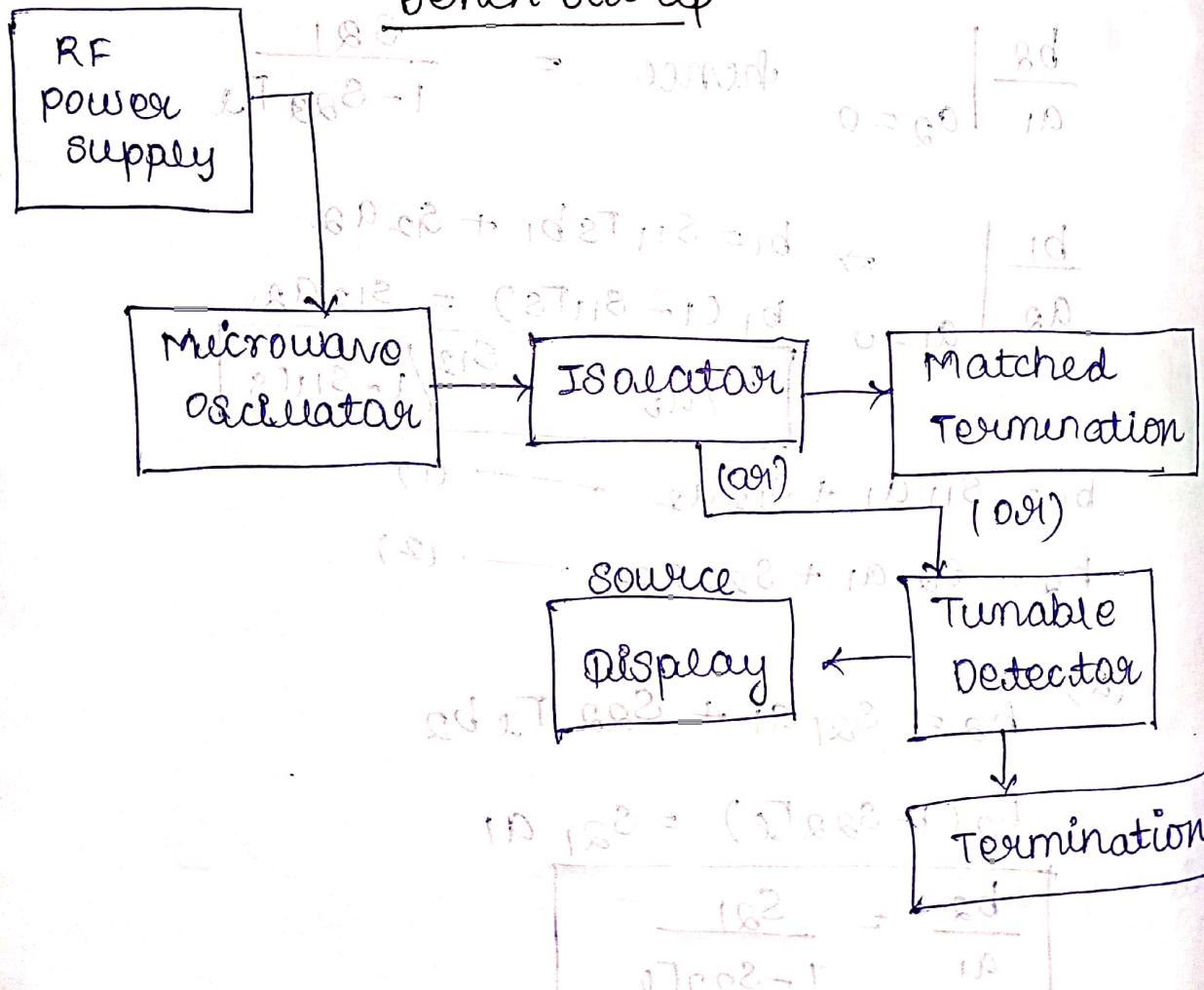

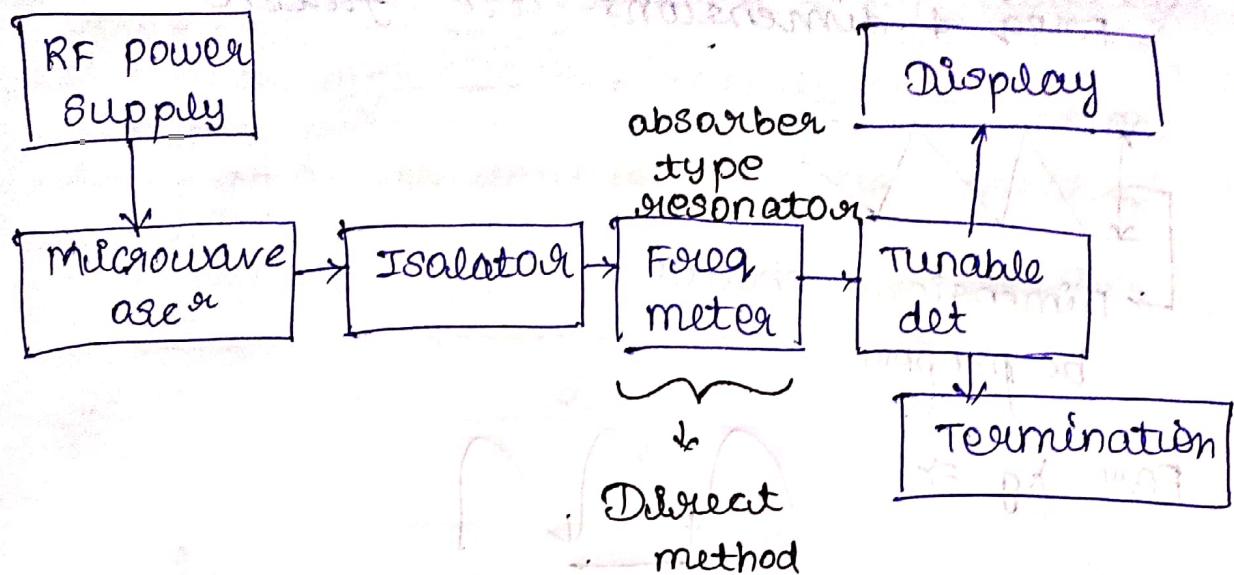


Indirect method:

$$\lambda_0 = \lambda c / f_0 = 0.6$$

$$c = 3 \times 10^8 \text{ m/s}$$

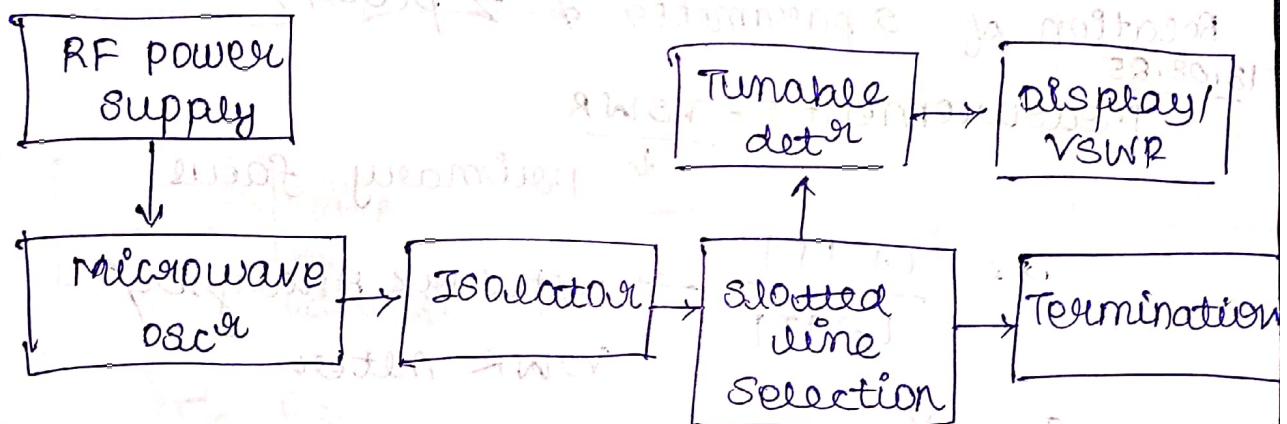
Indirectly measuring λ_0 we will get f_0 .



$$\frac{1}{\lambda_0^2} = \frac{1}{\lambda_g^2} + \frac{1}{\lambda_c^2}$$

λ_g = guided wavelength

λ_c = freq of operation.

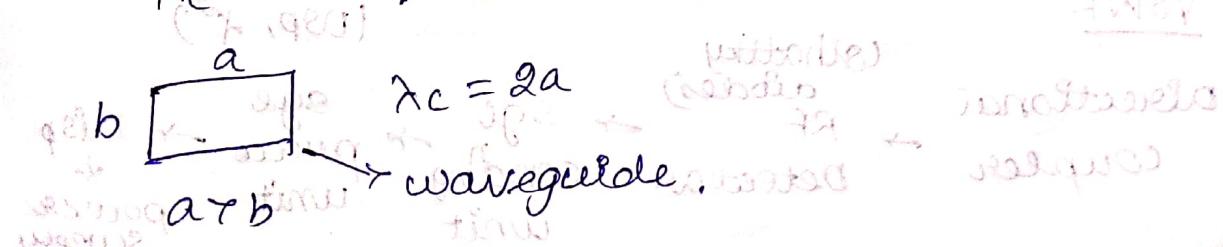


freq & dimensions are fixed



dimensions should

be proper

$$\text{For } \lambda_g \Rightarrow$$

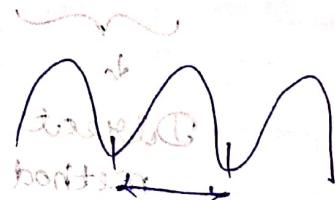

$$d_{\min} = \frac{\lambda_g}{2}$$

: ~~minimum distance~~ to well

$$\lambda_g = 2 d_{\min}$$

Explain test bench then explain the procedure briefly.

Relation of δ parameter & Z parity

Measurement s - VSWR

primary face

$$\delta = \frac{1 + |\Gamma|}{1 - |\Gamma|} \rightarrow \text{Network Analyser}$$

VSWR meter

$$\delta = \frac{V_{\max}}{V_{\min}}$$

$$\frac{1 + \sqrt{\delta}}{1 - \sqrt{\delta}}$$

Network Analyser \rightarrow Refⁿ coefficient

VSWR

VSWR

Directional coupler

(shottky diodes)

RF

Detector biasing

\rightarrow Sge \rightarrow Sge \rightarrow DSB

unit

differential
(DSP, x⁹)

power supply


VSWR_{min} low $\Rightarrow \text{VSWR} \leq 4$ directly read

VSWR_{min} high $\Rightarrow \geq 4$ (Analytical calculation)


we go with double minima method

slotted line section
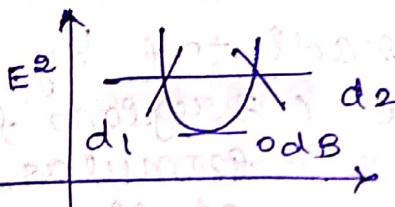
$$\theta = \frac{\lambda g}{\pi(d_1 - d_2)}$$



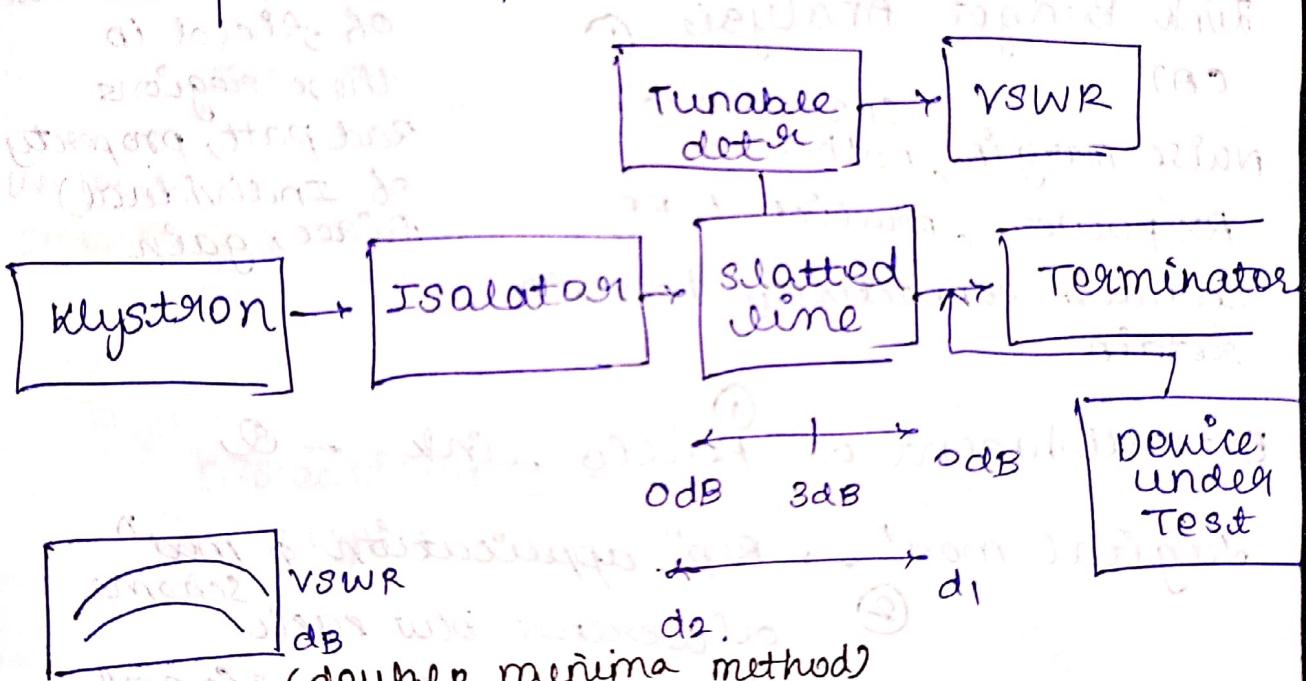Half power in Elect $= \left(\frac{E}{\sqrt{2}}\right)^2$



$$T = \frac{P_{\text{far}}}{P_{\text{ref}}}$$

Impedance Measurement:

Relationship b/w VSWR and Reflection coefficient

- * Bridge (Balance Bridge) → Low microwave frequencies

- * Slotted line → Medium and high.

- * Impedance meters → Direct, High freq.

- * Network Analyser → Medium, High freq


- ↳ s-parameter accounted $Z_0 = 50\Omega$

$$\bar{Z} = Z_0 \frac{1+|T|}{1-|T|}$$


known Impedance + sparameter valuation.

$$\text{Impedance} = Z_0 \frac{1+j\tan\phi}{1-j\tan\phi}$$

→ directional coupler
Sig

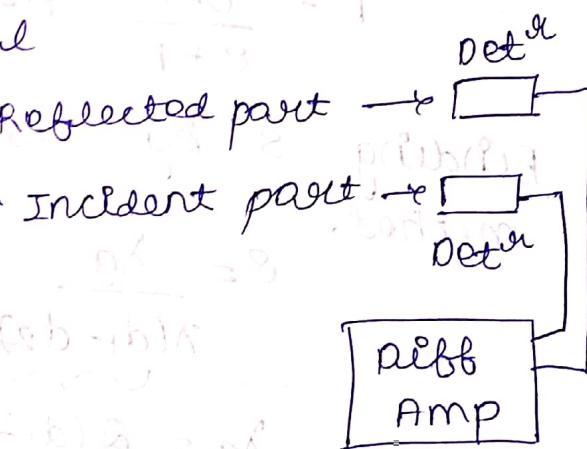

Balance Bridge

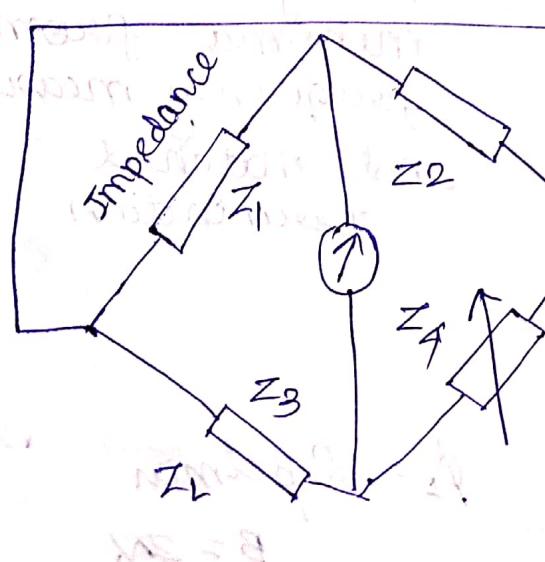

→ All impe. matches

Galvanometer zero deflection

→ mismatch also shown in Galvanometer

$$\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}$$

$$Z_3 = \frac{Z_1}{Z_2} \times Z_4 \quad \text{if } Z_3 \text{ is unknown.}$$

and initially fixing variable impedance Z_4 and fixed $Z_1 + Z_2$

impedance tuning we can get null deflection

$$\text{phase: } \theta_1 + \theta_3 = \theta_2 + \theta_4$$

slotted line section

$$Z_L = \frac{Z_0}{1 + |\Gamma|}$$

$$|\Gamma| = \frac{S-1}{S+1}$$

$$S = VSWR$$

Finding S by using double minima method.

$$S = \frac{\lambda_g}{\lambda}$$

$$\pi(d_1 - d_2)$$

$$\lambda_g = \varphi(d_1 - d_2)$$

High VSWR measurement put source under test

using φ successive minima from frequency measurement and matched termination

DUT \Rightarrow matches Impedance

Low VSWR


matched SRL

on phase variation:

$$\text{dis. mode} \\ \text{restoration} \rightarrow e^{j\theta z}$$

$$\phi_2 = 2\beta d_{\min}$$

$$\beta = \frac{2\pi}{\lambda_g}$$

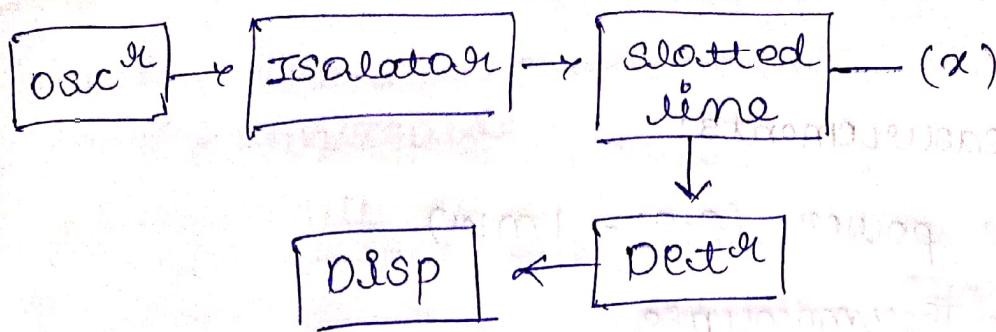


1. Load $\rightarrow S$
2. Matched $\rightarrow d_{min} (d_1)$
Termination
3. perfect conductor $\rightarrow V_{min} \rightarrow d_2'$
(move slotted line)

$$d_{min} = d_2 - d_1$$

Smith chart

\rightarrow VSWR circle

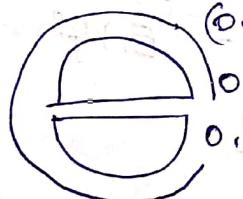$\rightarrow d_{min}$ - plotting towards load



short \ll Impedance \gg open end
ckt end

for admittance

$$Y = \frac{1}{Z}$$

$$Y = \frac{1}{Z + 0.5j}$$

15.08.25

power measurements:

very low power ($0.01 - 1 \text{ mW}$)

↳ Thermocouple

low power ($0.1 - 10 \text{ mW}$)

↳ Balometer

medium power ($10 \text{ mW} - 1 \text{ W}$)

↳ Balometer with directional coupler

High power ($1 \text{ W} - 1 \text{ KW}$)

↳ calorimetric watt

very low power:

Sb-Bi Thermocouple - wires joined

together - plates get heated - EMF

gets generated between Sb-Bi

low power

Balometer → positive temperature variances



Either in waveguide meters (0°C) or co-axial cables.

→ positive ($P \uparrow R \uparrow$) Barretters

→ negative ($P \uparrow R \downarrow$) Thermistors Resistors

Input power → waveguide
 C-slit to detect → galvanometer
 (null deflection = no power)
 variations → deflections
 in Resistivity

Medium power


Balometer + DC

→ couples the signals

- boosting up the signal.
- increase coupling factor

High power

calorimetric wattmeter

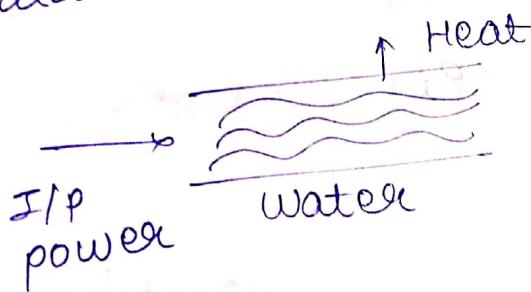

→ temperature variations)

checks the Inlet and outlet temp. variation

$$P = 4.187 \cdot c \cdot V_d \cdot \Delta T \cdot W$$

c - specific heat of water

V - rate of water

d - density of water

Attenuation measurement:

SUT by subtracting reflection


loss from insertion loss.

Forward \rightarrow DUT

reflected power

coupled power

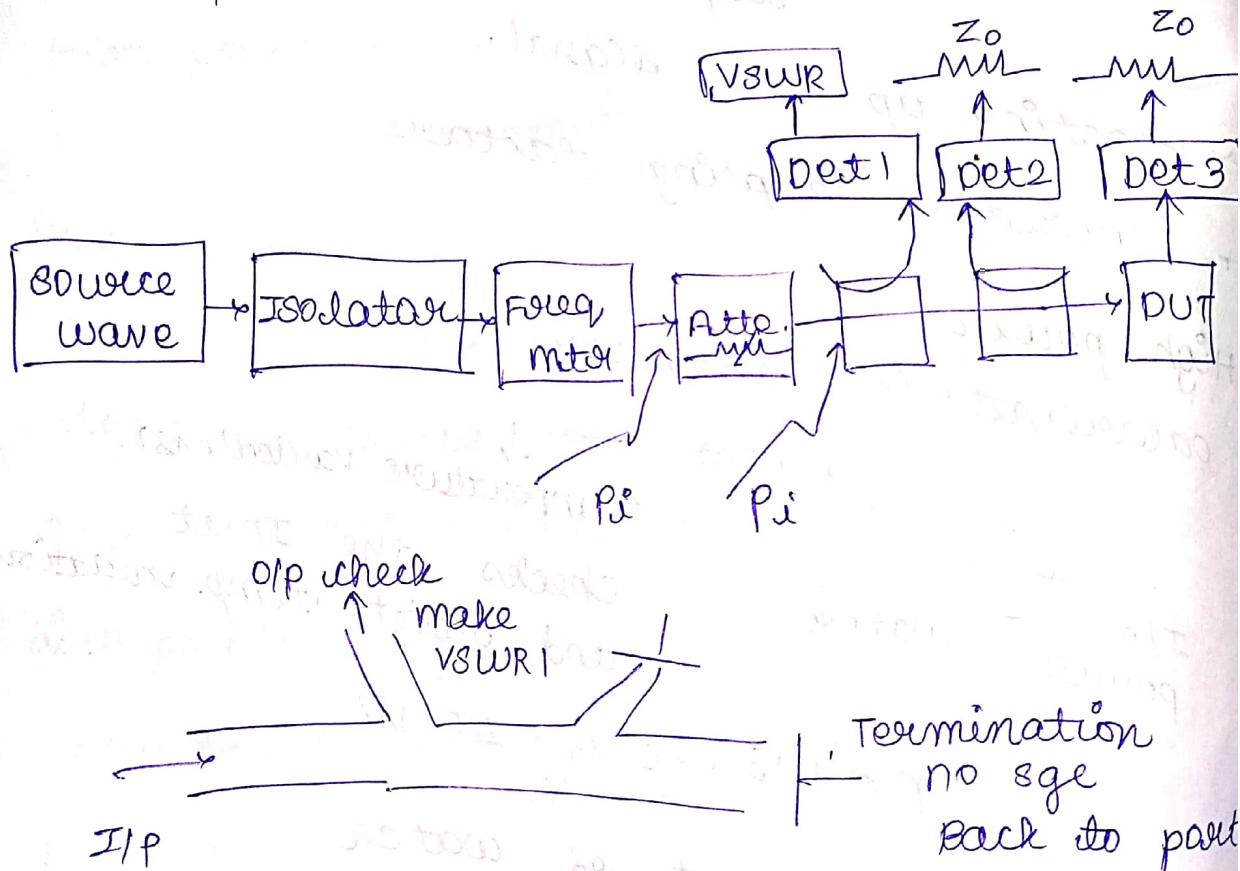output part \rightarrow matched termination




freeze no reflection

reflected power \rightarrow VSWR \rightarrow Det 1

DUT \rightarrow Ter

\rightarrow From 1 what charge

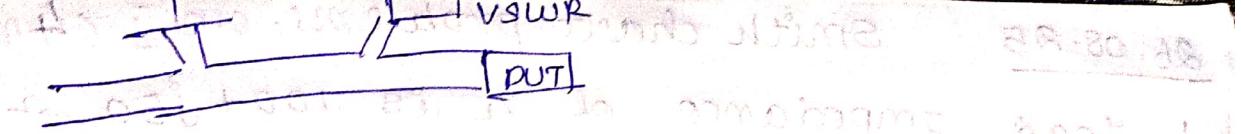(Refⁿ return loss as other
loss) parts are not at Ter. now



- VSWR at coupling point.
- Variations give insertion loss.
- Attenuation loss = Reflection loss - Insertion loss.

Noise measurement

Spectrum Analyser



- with device, signal variations & without device variation (difference provides noise figure)

- S/N over particular spectrum.

- * Thermistors not used in real time approach

- * Calorimetric value is not for real time not for RF comm.

- * Low + medium power we engage \rightarrow bolometer is normally of use.

Q6.08.25

Smith chart problems. C1A-11 (4 marks)

1. Load impedance of Z_L is $100 + j50 \Omega$ is connected to 50Ω transmitter line. Plot normalized load on Smith chart. Determine Γ_L both magnitude and phase. Calculate VSWR.
2. For the transmitter line with $Z_0 = 75\Omega$ the Γ_L at the load is measured as $0.4 \angle 60^\circ$. Locate Γ_L Refⁿ coefficient. Determine Z_L , calculate VSWR.
3. The transmission line of characteristic impedance 50Ω is terminated with a load $Z_L = 25 - j25 \Omega$. Plot the load on the Smith chart and draw constant VSWR circle. Determine VSWR from the load $\frac{1}{8}$ from the load.

Given:

$$1. Z_0 = 50 \Omega$$

$$Z_L = 100 + j50 \Omega$$


$$\bar{Z}_L = \frac{100 + j50}{50} = 2 + j1$$

$$\text{Ref}^n \text{ coeff (power)} = 0.8 \angle 128^\circ$$

$$\text{VSWR} = 2.6$$


Q1).

Smith Chart

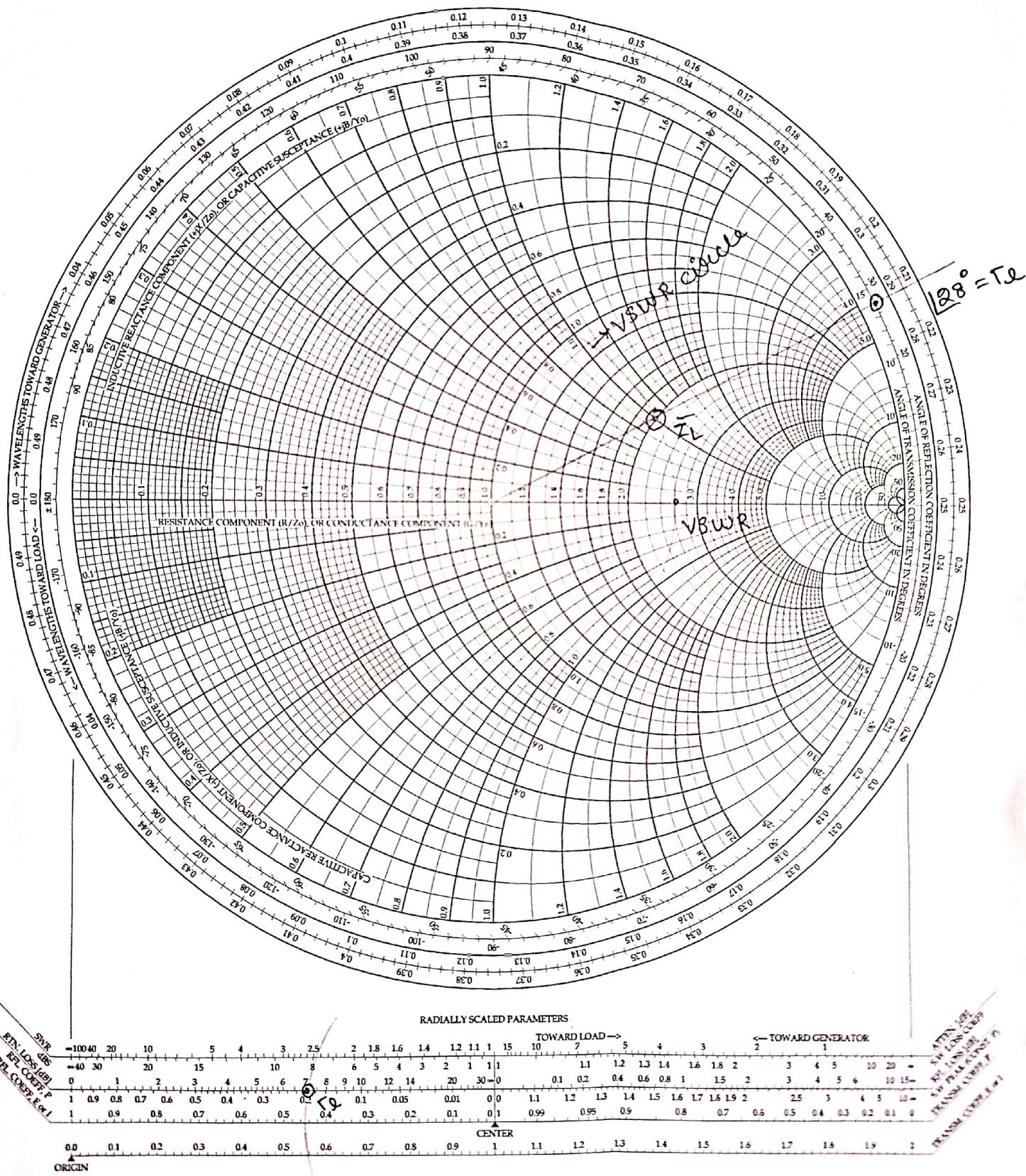


2) 22)

Smith Chart

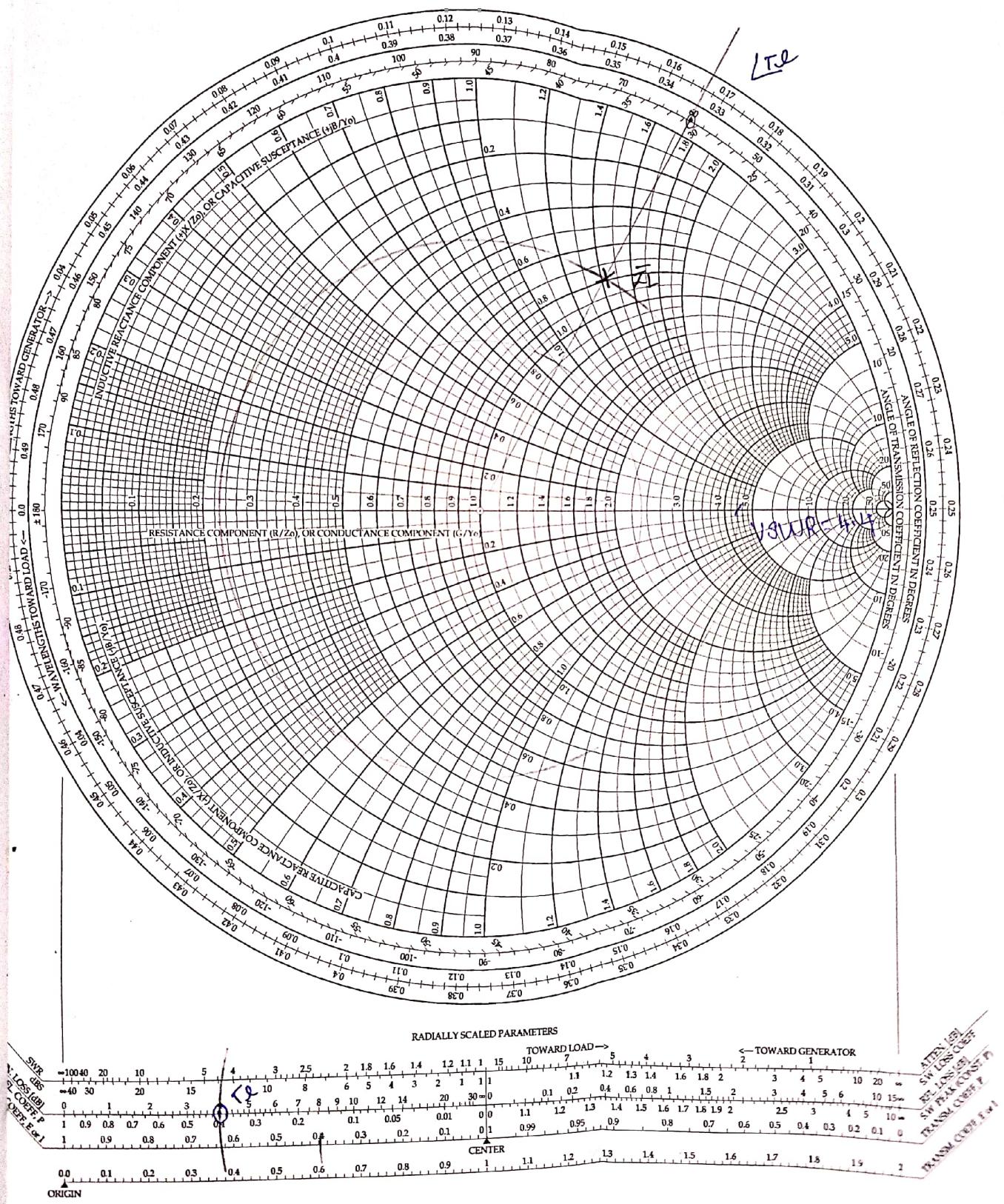

DATE

3) Q3)

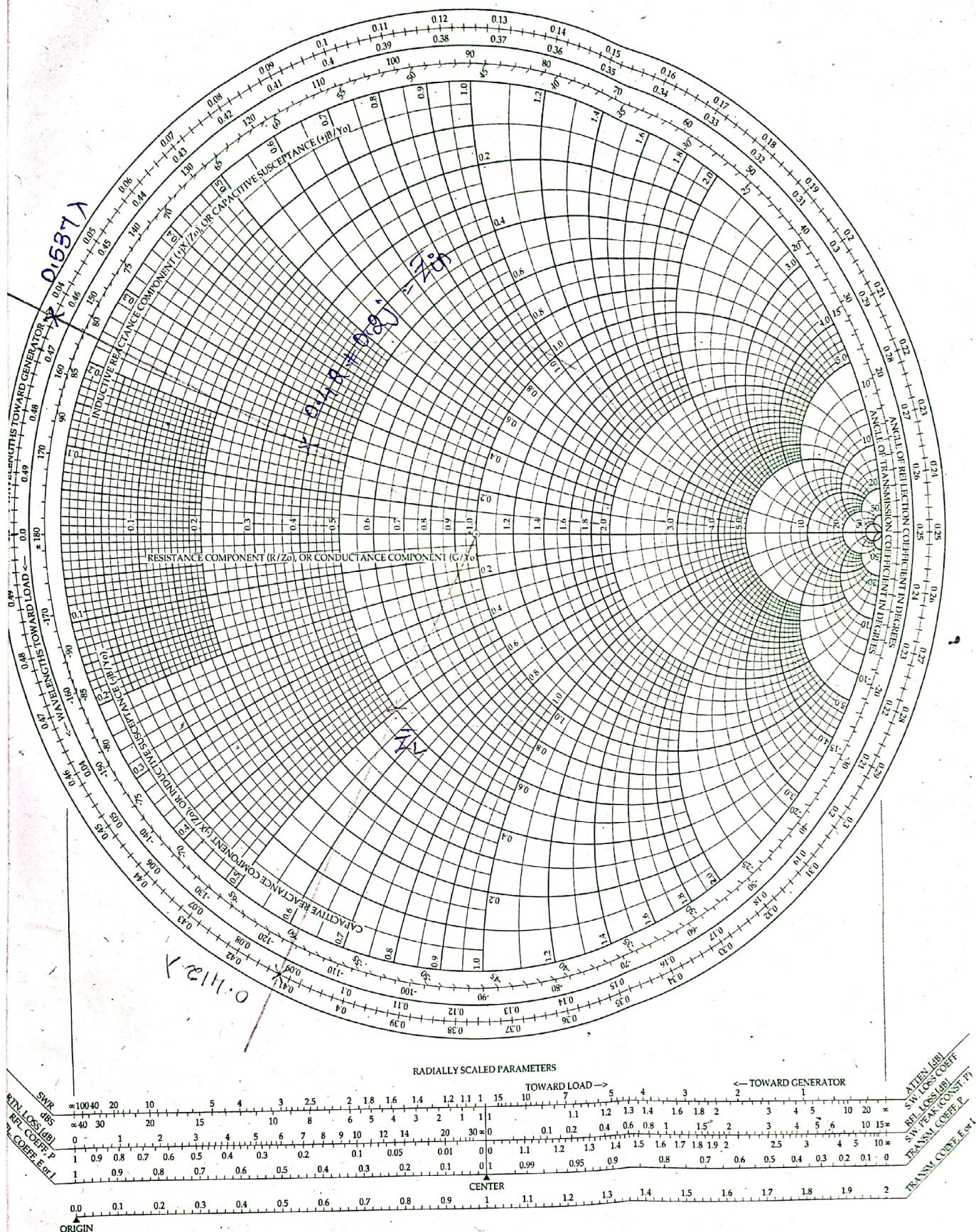

Smith Chart

Q) Refⁿ coefficient = 0.4 L60°

$$\bar{Z}_L = \frac{Z_L}{Z_0}$$

$$0.8 + 1.4j = \underline{\bar{Z}_L}$$

$$Z_0 = 75$$

$$Z_L = 60 + 105j$$

A-II

$$= 20 = 5 \times 4$$

$$0 = 30 \text{ (Either or)} = 10 \times 3$$

$$\underline{\underline{50}}$$

$$2. Z_{le} = 0.85 - 0.5j$$

$$\bar{Z}_L = \underline{\underline{0.5 - 0.5j}} = 0.5 - 0.5j$$

$$\bar{Z}_{in} = 0.42 + 0.2j$$

$$Z_{in} = (0.42 + 0.2j) 50 = 21 + 10j$$

Towards Genⁿ: Z_L given and find source

Towards Load: Z_S given and find Load.