

18.09.85

UNIT - IV

Mixers And Detectors

Mixers:


- Converting RF → Baseband / IF frequency.
 - Baseband + LO → RF (RF TX^g)
-
- upconversion (TX^g) downconversion (RX^g)

upconversion:


In TX^g, mixer converts a low freq Baseband sig (audio or data) into high freq RF sig. mixing Baseband with LO signal to produce new signal at the sum of ori. freq (sometime diff)

down conversion: converts high freq. RF back down to low frequency using IF or baseband by mixing RF with LO signal

Generic Transceiver:

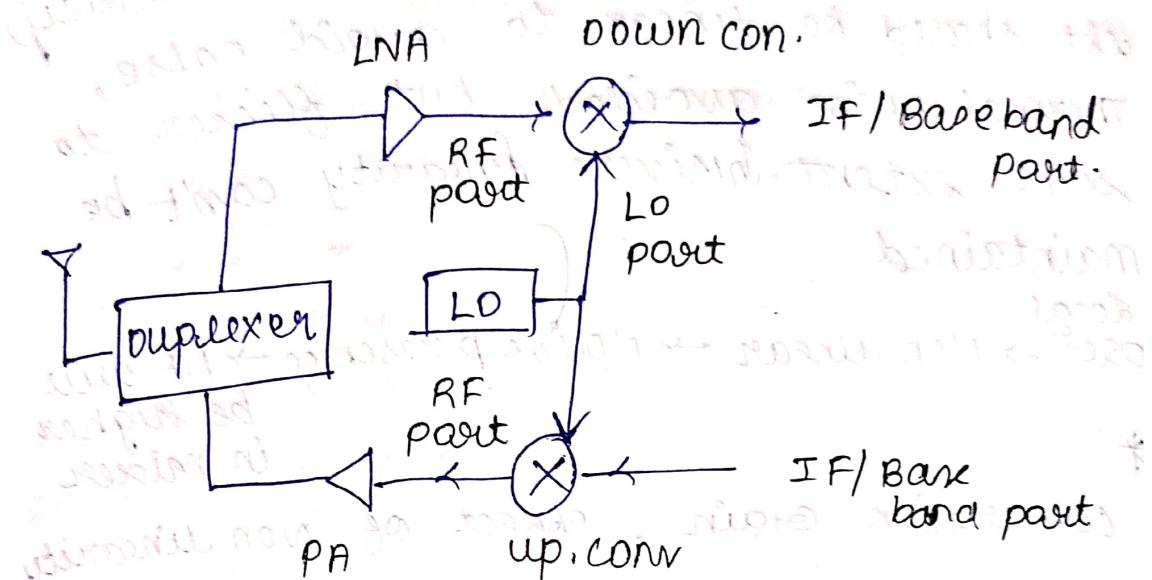

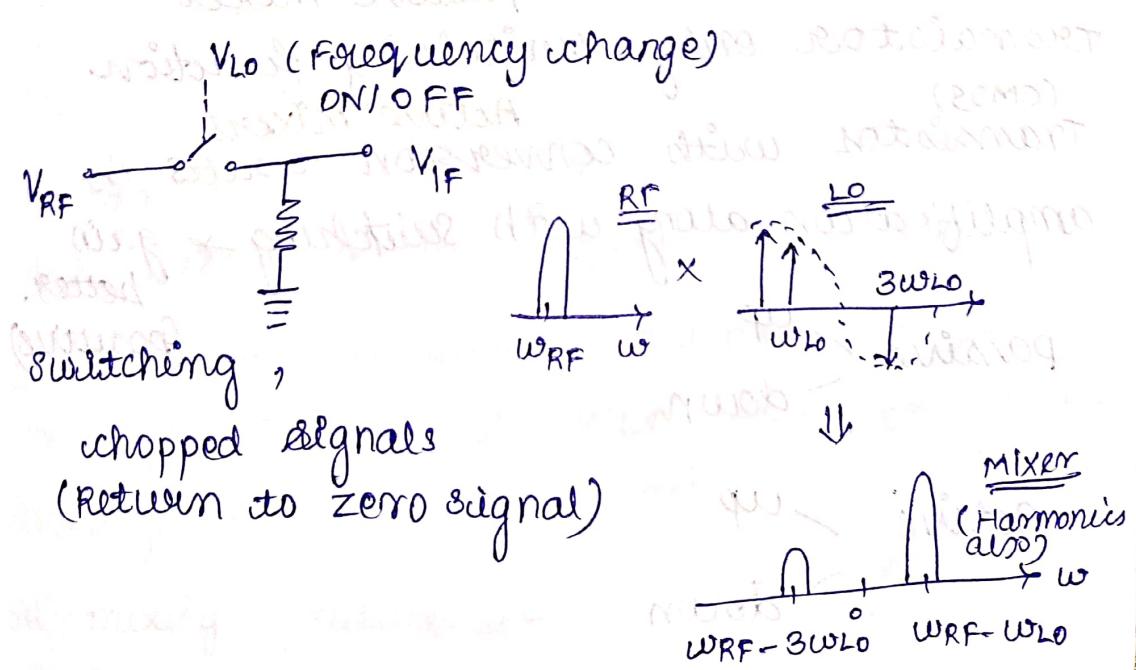- abrupt change in LO frequency, decides frequency at end of mixers.
- 1ckt mixes the RF S/I/P with all LO harmonics - mixing spurs.



Performance parameters:

1. Noise & Linearity
2. Gain
3. port-to-port feed through.


* Thermal noise + Flicker noise (due to non linearity)

Ckt should be linear to avoid noise,
Thermal noise avoided but flicker to some extent. In mixer linearity can't be maintained

Local oscillator → Non linear → Noise presence → NF will be higher in mixer


* Conversion gain, effect of non linearity leads to Amplitude suppression leads to -ve value hence conversion loss, switching function

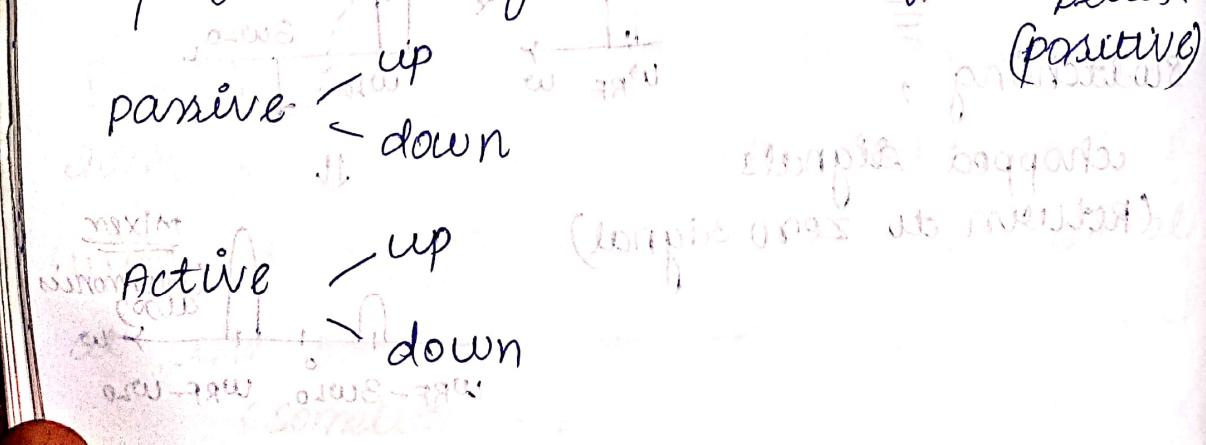Transistor only switching function
(CMOS) Active mixers
Transistor with conversion results in amplification along with switching → gain better.



- * 3-point N/W \rightarrow isolated each other
 ↗ LO port
 ↗ I/P port
 ↗ O/P port

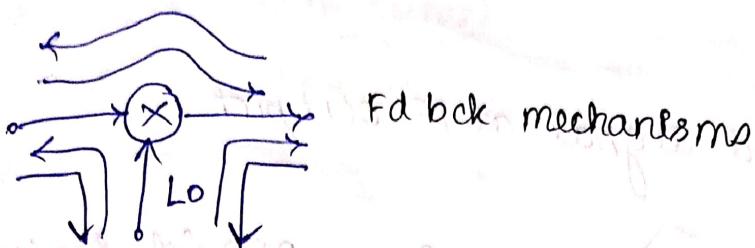poor ISolation \rightarrow RF and LO component leakages (through ports)




LO to RF feed through

LO to IF feed through

RF to IF feed through

unbalanced \rightarrow parasitic capacitances \rightarrow

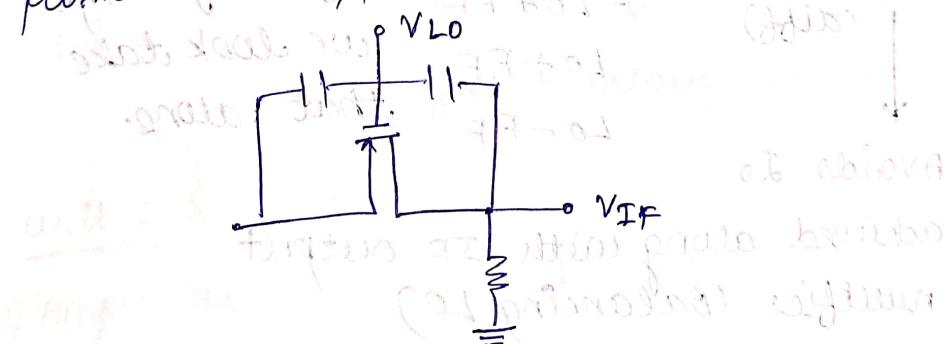parasitic AC shunters \rightarrow Back to RF.



LO to RF:

self mixing + DC offset

In direct conv. RXR \rightarrow LO & RF close \rightarrow
 Through feedthrough \rightarrow LO re-enter mixer
 through RF to mix itself

self mixing produces DC component (or) low
 frequency component

DC offset can interfere with accurate detection of low freq or DC signals leading to signal distortion.

LO and IF Interference with Baseband Signal

RF and IF:

unwanted signal at IF output

Balanced mixers - soln \rightarrow Avoid feedthrough
Nullify the effect in circuit level
 $LO - IF \Rightarrow$ output: $LO + RF$ carries feedthrough

If $LO, LO \Rightarrow -LO - RF$ If any comp,
↓ (diff) $-LO + RF$ we look take
 $LO + RF$ that alone.
 $LO - RF$

Avoids LO

achieved along with IF output
nullifies (Balancing LO)

single Balanced double Balanced

RF to IF \Rightarrow output RF and diff O/p

If LO, LO, RF, RF
Balanced both LO and RF in output
(double balanced mixer)

30.09.85

Mixers:


→ produces IF/Baseband signal
on TX → upconversion mixer

[Baseband + LO \Rightarrow RF]

on RX → downconversion mixer


[RF + LO \Rightarrow IF/Baseband]

LO \Rightarrow switching

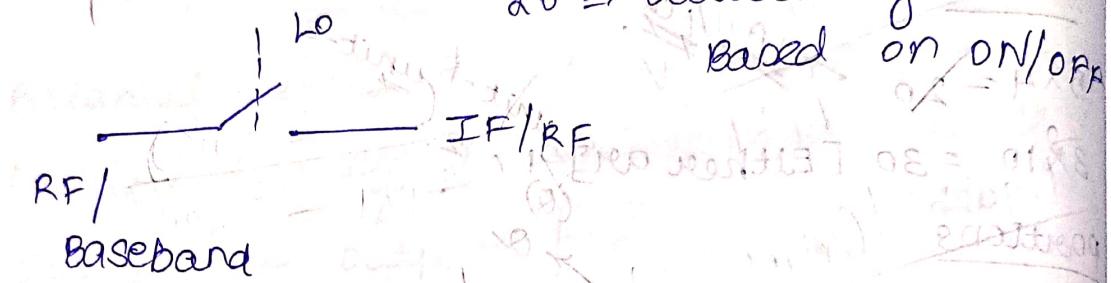


* LO as switch on FP, leads to frequency shifts.

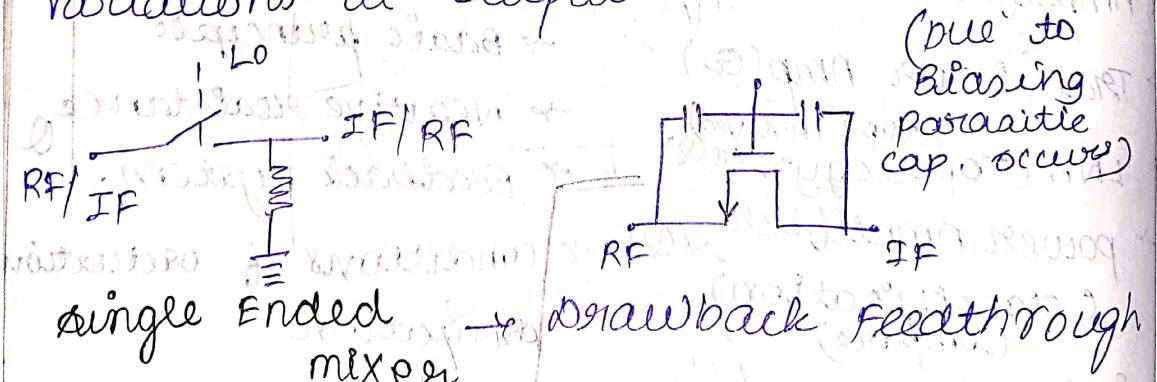* LO is preferably sinusoidal signal, switching occurs, chopped signal as input leads to frequency variations at output.



LO to RF feedthrough occurs because of parasitic capacitances along with IF, RF and LO occurs.

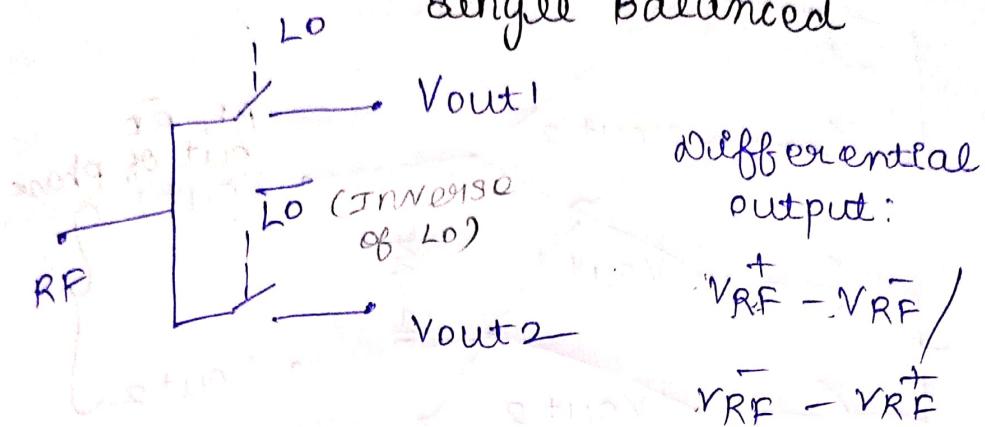
* To suppress this Balanced mixers
are used (differential results)





output now:

IF, LO, IF, RF; hence LO gets
cancelled

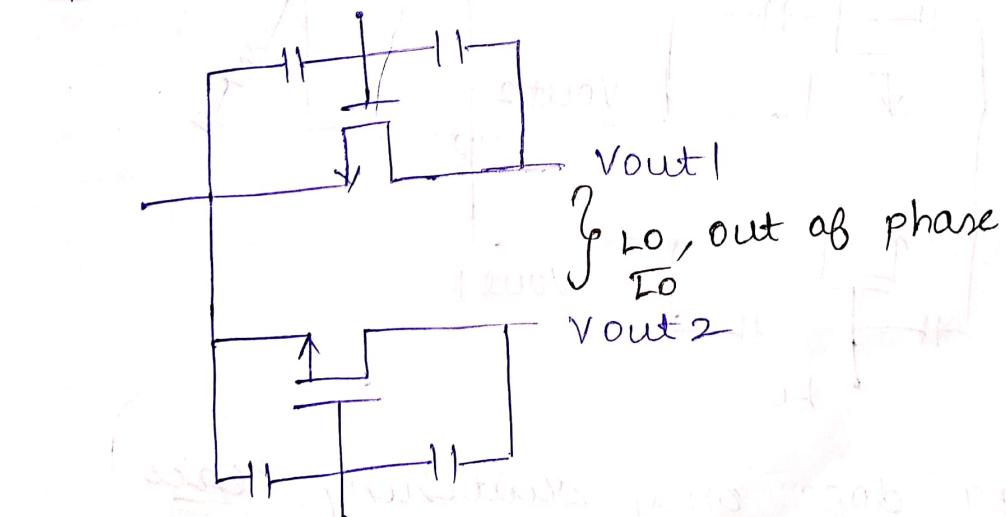* Even harmonics are been suppressed
IIP2 (Intercept point) \rightarrow Improve
Input power to swing for longer
time since even harmonics are
suppressed. (IIP2 - Better)



Double Balanced:

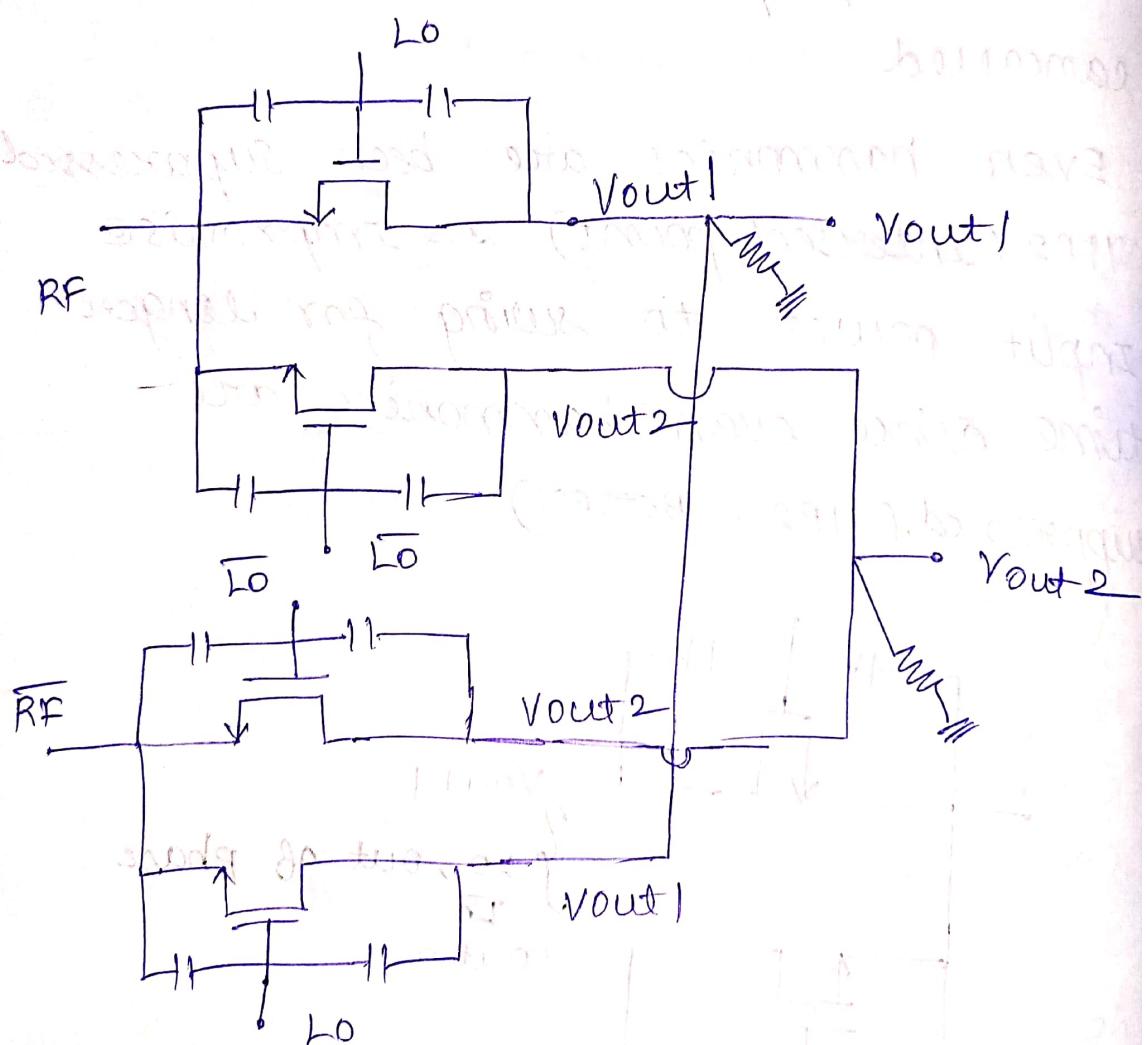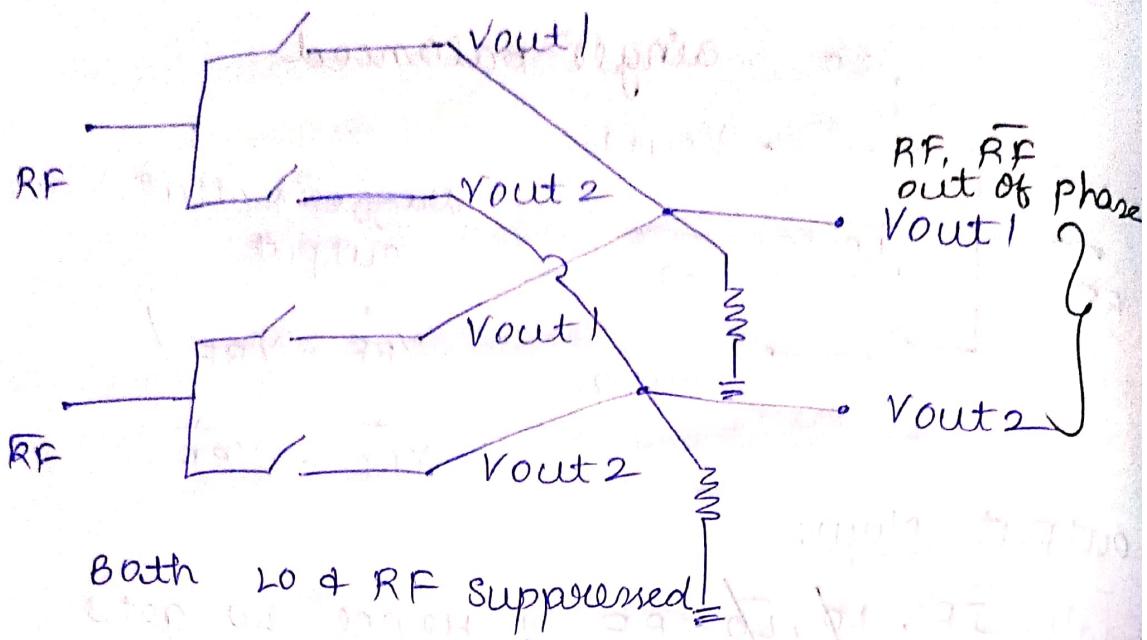


FET does only switching hence passive mixers.

Mixers \rightarrow conversion loss.

passive mixers \rightarrow negative gain.

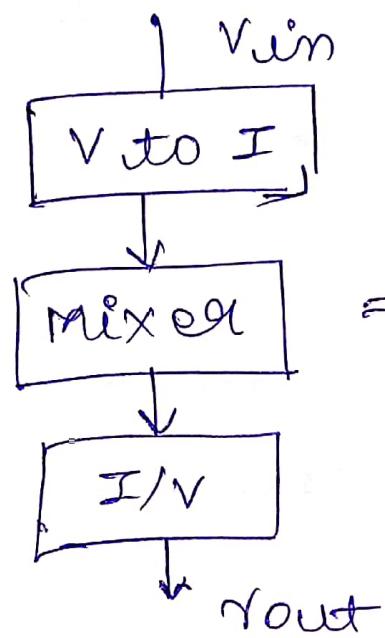
In active mixers, negative mixers removed by using V to I conversion block and vice versa



\Rightarrow mixing in terms of current hence avoid voltage drops, which occurs in passive mixers can be avoided in active mixers

* Active mixers at TX end

mixer \rightarrow power amp

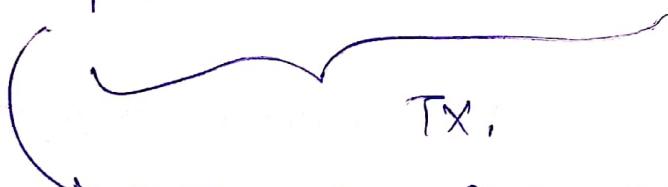

\rightarrow drop of mixer can be addressed.

RX \rightarrow passive mixers

02. 10. 25

Mixers

passive - voltage switch

Active mixers:

characteristics:

Noise figure

conversion gain

Image frequency


IMD - Inter Modulation Distortion (non-linearity)

V-I converter conversion gain

I-Mixer conversion gain

I-V converter conversion gain


Block diagram:

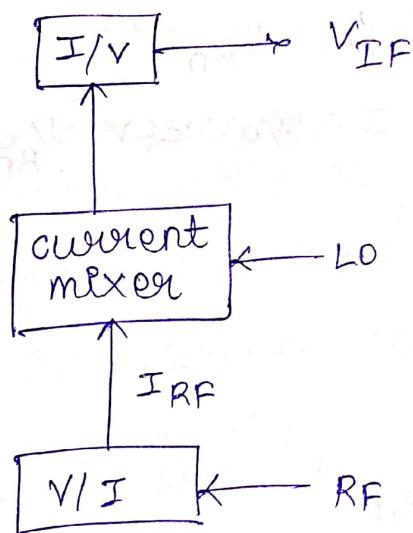

1. conversion gain

* circuit diagram using single

Balanced

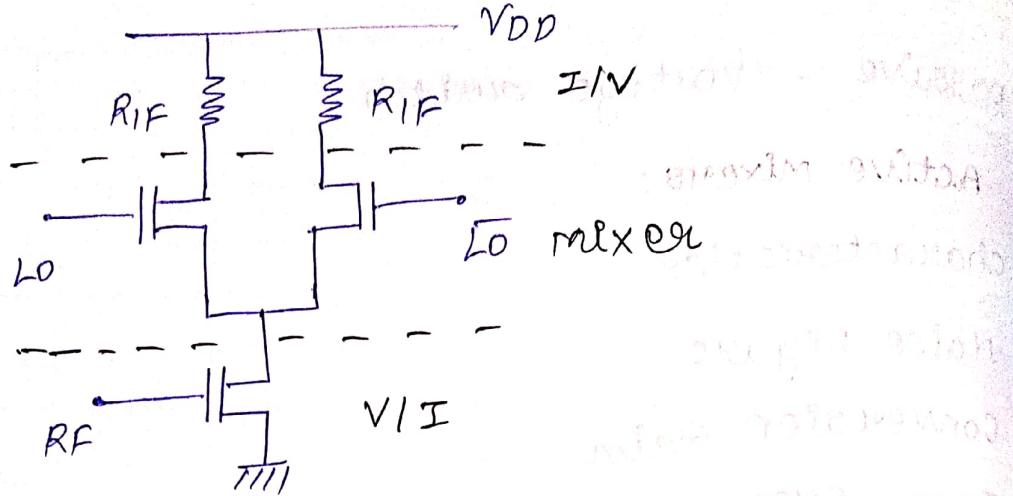

Mixers \rightarrow DC source and free mixing

Accounting g_m V_{DD} $I \rightarrow LO \rightarrow$ mixing
 $LO + LO$ as switch passes across the
 resistors we yield voltage

$$\text{conversion gain} = \frac{V_{IF}}{V_{RF}}$$

$$I_{RF} = V_{RF} g_m \quad g_m = 1/R_D$$

$$I = V/R = V_o / R_D$$

$$I_{IF} = I_{RF} \cos \omega L_0 t$$

$$I_{IF} = I_{RF} \cos \omega L_0 t$$

$$V_{IF} = I_{IF} \times R_{IF}$$

$$= I_{RF} \cos \omega L_0 t \times R_{IF}$$

$$= V_{RF} g_m \cos(\omega L_0 t) \times R_{IF}$$

$$CGI = \frac{V_{IF}}{V_{RF}} = g_m \cos(\omega L_0 t) R_{IF}$$

$g_m R_{IF}$ = Quantified amount

Not a conversion loss

2. Noise Figure

$$NF = \frac{8NR_{O/P}}{8NR_{S/P}}$$

NF = conversion Gain

mixer:

$$V_{IF} = V_{LO} \times V_{RF}$$

$$V_{LO} = A_{LO} \cos(\omega_{LO}t)$$

$$V_{LO} = A_{LO} \cos(Q\pi f_{LO}t)$$

$$V_{RF} = A_{RF} \cos(2\pi f_{RF}t)$$

$$V_{IF} = A_{LO} A_{RF} \cos(2\pi f_{LO}t) \cos(2\pi f_{RF}t)$$

$$V_{IF} = \frac{A_{LO} A_{RF}}{2} \left[\cos 2\pi [f_{LO} + f_{RF}]t + \cos 2\pi [f_{LO} - f_{RF}]t \right]$$

$$V_{IF} = \frac{A_{LO} A_{RF}}{2} \cos 2\pi (f_{LO} - f_{RF})t$$

Image Frequency:

An image frequency is a frequency that produces some IF frequency which causes interference to intended frequency.

$$\text{Eg: } f_{LO} = 110 \text{ MHz}$$

$$f_{IM1} = f_{LO} - f_{IF} \quad (\text{contains } f_{RF} = 100 \text{ MHz info})$$

$$= f_{LO} + f_{IF}$$

$$f_{IM1} = \frac{(f_{RF} - f_{IF})}{100 - 10} = 90 \text{ MHz}$$

$$= 100 + 10 = 120 - 10 = 110 \text{ MHz}$$

$$(f_{RF} + f_{IF})$$

Now f_{IM1} as input (no info) $f_{IM1} - f_{LO} = 10 \text{ MHz}$ (coarse)

same frequency but if Amplitude differs easy to neglect Image freq component.

↑ } same as input (Image)

- * Image rejection filter to avoid, tune it.

80 - 120 MHz \rightarrow LNA \rightarrow Image Reg Filter \rightarrow Mixer

(Band filter)

Non-linearity Effects. $V = V_{in} + V_{in}^2 + V_{in}^3 + \dots$

$$V_{in} = A \cos \omega t$$

Image modulation

squaring

distortion (IMD)

$$V_{in}^2 = A^2 \cos^2 \omega t$$

$$= \frac{A^2}{2} (1 + \cos 2\omega t)$$

$$= \frac{A^2}{2} + \frac{A^2}{2} \cos 2\omega t$$

\downarrow second harmonies

DC component

$$V_{in}^3 = (A \cos \omega t)^3 = A^3 \cos^3 \omega t$$

$$= A^3 \left[\frac{3}{4} \cos \omega t + \frac{1}{4} \cos 3\omega t \right]$$


Fundamental

Third

Harmonics

fundamental freq \rightarrow Grain Expansion
(Amplitude) \rightarrow Grain compression

Eg: In cc f^n

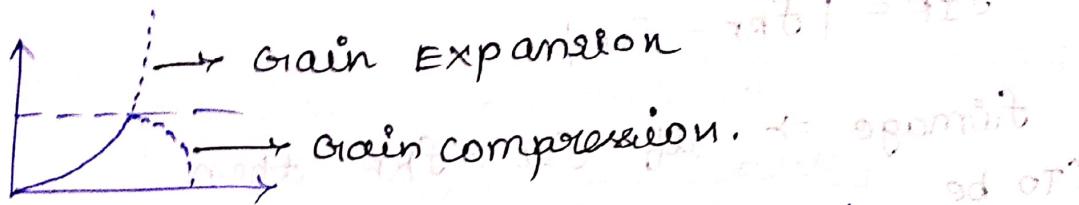

IIP 2 - second harmonics is 1 dB
down the fundamental freq
(Intercept point)

$$V_{IF} = V_{LO} \times V_{RF}$$

$$= A_1 A_2 [\cos \omega_1 t \times \cos \omega_2 t]$$

$$(V_{IF})^2 = A_1^2 A_2^2 (\cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t)^2$$

$$= A_1^2 A_2^2 (\cos \omega_1^2 t + \cos \omega_2^2 t + 2 \cos \omega_1 \omega_2 t +$$

$$+ \cos \omega_1^2 t + \cos \omega_2^2 t - 2 \cos \omega_1 \omega_2 t)$$

Fund freq + Non linearity \rightarrow Additional distortion \leftarrow to Fundamental (IMD)

To overcome \Rightarrow sharp filtering effects
choice of ω_{LO} ≈ 0.01

Non linear Image Frequency ≈ 0.001

06.10.85

Image Rejection mixer:

f_{RF}, f_{LO}, f_{IF}

$$f_{IF} = |f_{RF} - f_{LO}|$$

f_{image} \Rightarrow if $f_{LO} > f_{RF}$ then
(To be removed) $f_{img} = f_{LO} + f_{IF}$

if $f_{LO} < f_{RF}$ then

$$f_{LO} - f_{IF}$$

filter suppresses original info hence
phase shift in LO

* split RF

* split LO (90° shift on one path)
and another original

* combine.

$$v_{RF} = V_{RF} \cos(\omega_{RF} t)$$

$$v_{LO} = V_{LO} \cos(\omega_{LO} t)$$

Let:

$$v_{LO,I} = V_{LO} \cos(\omega_{LO} t)$$

$$v_{LO,Q} = V_{LO} \sin(\omega_{LO} t) \text{ Quadrature}$$

$$v_{IF,I} = v_{RF} \times v_{LO,I}$$

$$= V_{RF} (\cos \omega_{RF} t) \times V_{LO} \cos(\omega_{LO} t)$$

$$V_{IF, I} = \frac{V_{RF} V_{LO}}{2} [\cos(\omega_{RF} - \omega_{LO})t + \cos(\omega_{RF} + \omega_{LO})t]$$

①

$$V_{IF, Q} = V_{RF} \cos(\omega_{RF}t) \times V_{LO} \sin(\omega_{LO}t)$$

$$= \frac{V_{RF} V_{LO}}{2} [\sin(\omega_{RF} - \omega_{LO})t + \sin(\omega_{RF} + \omega_{LO})t]$$

$$V_{IF} = e^{j(\omega_{RF} - \omega_{LO})t} + e^{j(\omega_{RF} + \omega_{LO})t}$$

After LPF

$$V_{IF} = e^{j(\omega_{RF} - \omega_{LO})t} - \cos(\omega_{RF} + \omega_{LO})t$$

$$= \cos(\omega_{RF} - \omega_{LO})t + j \sin(\omega_{RF} + \omega_{LO})t$$

when phase shift $\sin \rightarrow \cos \Rightarrow$ same phase
 (inphase details)

$$f_{image} = f_{IF} + f_{LO}, f_{LO} - f_{IF}$$

down conversion part working

$$f_{image} = f_{LO} - f_{IF}$$

Instead of RF, f_{image} freq.

In ①

$$V_{IF, I} = \frac{V_{image} V_{LO}}{2} [\cos(\omega_{LO} - \omega_{IF} - \omega_{LO})t + \cos(\omega_{LO} - \omega_{IF} + \omega_{LO})t]$$

$$= \frac{V_{image} V_{LO}}{2} [\cos(-\omega_{IF})t + \cos(\omega_{LO} - \omega_{IF})t]$$

on LPF

constant and oscillating terms

$$V_{\text{image}, Q} = \frac{V_{\text{image}, LO}}{2} [\sin(\omega_{LO} - \omega_{IF} - \omega_{LO}) e^{j\theta} + j \sin(\omega_{LO} - \omega_{IF} + \omega_{LO}) e^{j\theta}]$$

$$V_{\text{image}, Q} = V_{\text{image}, LO} [\sin(-\omega_{IF}) + j \sin(\omega_{LO} - \omega_{IF})]$$

on using combiner

$$\cos(-\theta) = \cos \theta$$


$$\sin(-\theta) = -\sin \theta$$

$$V_{IF, \text{image}} = \cos(\omega_{IF}) - j \sin(\omega_{IF})$$

Again, doing phase shift

$$V_{IF, \text{image}} = 0 \quad [\cos(\omega_{IF}) - \cos(\omega_{IF}) = 0]$$

Block diagram:

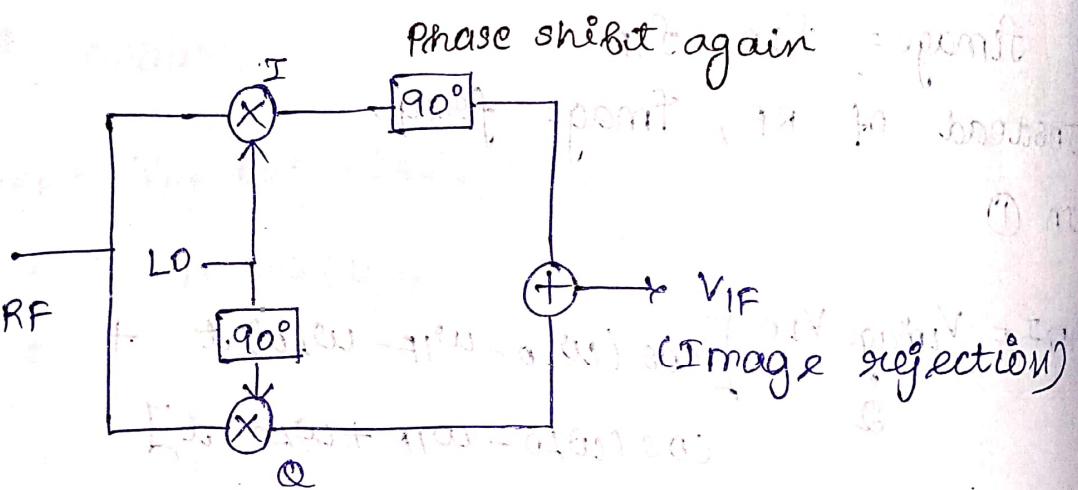

Types:

1. Quadrature Image Rejection
2. Single Balanced Image rejection
3. Double Balanced Image Rejection

→ Feedthrough presents in Quadrature
IRM

→ Single & double balanced overcomes
feedthrough too.

single Balanced Image Rejection mixer:

