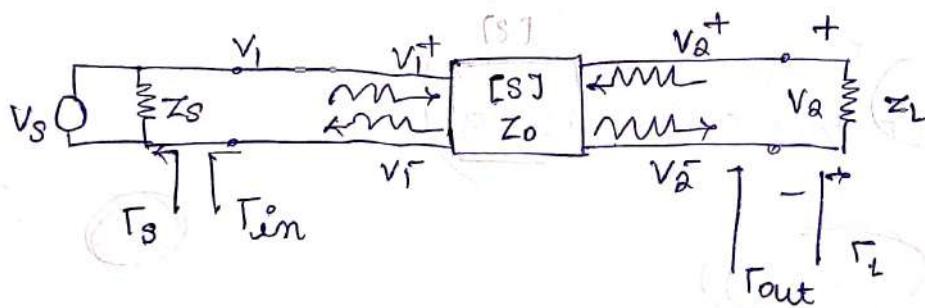


Microwave Amplifiers and Oscillators

1. Power Gain Z_1, Z_2
2. Availability Gain Z_S, Z_L (Mismatch at I/p change in input side only I/p side)
3. Transducer gain (Accounts mismatch in both end TX & RX)

Design we go with this gain.



for proper match

$$\Gamma_{out} = \Gamma_L$$

→ Let system is idle → power o/p is perfectly matched Gain
→ only $Z_0 \rightarrow$ Available change in power gain

→ Accounting Z_0 and Z_L

power Gain:

$$G_t = \frac{P_L}{P_{in}}$$

power dissipated in load z_L to power delivered to input of a port network. Gain is independant of z_S and z_L

Available power Gain

$$G_A = \frac{P_{Avn}}{P_{Avs}}$$

Ratio of power available from a port network to power available from the source. This assumes conjugate matching of both the source and load depends on z_S and not z_L

Transducer power gain:

$G_T = P_L / P_{Avs}$ is the ratio of power delivered to load to power available from source. This depends on both z_S and z_L

Reflection coefficient seen looking toward load

$$T_L = \frac{z_L - z_0}{z_L + z_0}$$

Reflection coefficient seen looking towards source

$$T_S = \frac{z_S - z_0}{z_S + z_0}$$

If any mismatch

$$V_2^+ = T_L V_2^-$$

In source

$$V_1^+ = \Gamma_S V_1^-$$

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+ = S_{11} V_1^+ + S_{12} T_L V_2^- \quad \textcircled{1}$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+ = S_{21} V_1^+ + S_{22} T_L V_2^- \quad \textcircled{2}$$

To find

$$\Gamma_{\text{in}} = \frac{V_1^-}{V_1^+}$$

From ① $V_1^- = S_{11} V_1^+ + S_{12} V_2^+ = S_{11} V_1^+ + S_{12} T_L V_2^-$

Sub ② in ① we get

$$V_1^- = S_{11} V_1^+ + S_{12} T_L (S_{21} V_1^+ + S_{22} T_L V_2^-)$$

$$V_1^- = S_{11} V_1^+ + S_{12} T_L S_{21} V_1^+ + S_{12} S_{22} T_L^2 V_2^-$$

$$V_1^- = V_1^+ (S_{11} + S_{12} S_{21} T_L) + S_{12} S_{22} T_L^2 V_2^-$$

From ②

$$V_2^- = S_{21} V_1^+ + S_{22} T_L V_2^-$$

$$V_2^- (1 - S_{22} T_L) = S_{21} V_1^+$$

$$V_2^- = \frac{S_{21} V_1^+}{1 - S_{22} T_L} \quad \text{--- } \textcircled{3}$$

Sub ③ in ①

$$V_1^- = S_{11} V_1^+ + S_{12} T_L \left(\frac{S_{21} V_1^+}{1 - S_{22} T_L} \right)$$

$$V_1^- = S_{11} V_1^+ + \frac{S_{21} S_{12} V_1^+ T_L}{1 - S_{22} T_L}$$

$$V_1^- = \left(S_{11} + \frac{S_{21} S_{12} T_L}{1 - S_{22} T_L} \right) V_1^+$$

$$\boxed{\frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{21} S_{12} T_L}{1 - S_{22} T_L}}$$

$$T_{in} = S_{11} + \frac{S_{21} S_{12} T_L}{1 - S_{22} T_L} = \frac{Z_{in} + Z_0}{Z_{in} - Z_0}$$

Now

$$T_{out} = \frac{V_2^-}{V_2^+}$$

In ①

$$(S_{11} T_S V_1^- + S_{12} V_2^+) = V_1^-$$

$$V_1^- (1 - S_{11} T_S) = S_{12} V_2^+ \text{ to plug in}$$

$$\frac{V_1^-}{V_1^+} = \left(\frac{S_{12}}{1 - S_{11} T_S} \right) V_2^+ \quad \text{--- ④}$$

Now in ②

$$V_2^- = S_{21} T_S V_1^- + S_{22} V_2^+ \quad \text{--- ⑤}$$

Add ④ in ⑤ ① in ② due

$$V_2^- = S_{21} \Gamma_S \left(\frac{S_{12}}{1 - S_{11} \Gamma_S} \right) V_2^+ + S_{22} V_2^+$$

$$\frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{21} S_{12} \Gamma_S}{1 - S_{11} \Gamma_S}$$

$$\boxed{\Gamma_{\text{out}} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}}$$

At part 1; the total voltage is

$$V_1 = V_1^+ + V_1^-$$

But we know that

$$\Gamma_{\text{in}} = \frac{V_1^-}{V_1^+}$$

$$V_1^- = \Gamma_{\text{in}} V_1^+ \text{ hence}$$

$$V_1 = V_1^+ + \Gamma_{\text{in}} V_1^+ = V_1^+ (1 + \Gamma_{\text{in}})$$

Looking at source side the source

V_S is divided between Z_S and Z_{in} hence

$$V_1 = V_S \cdot \frac{Z_{\text{in}}}{Z_{\text{in}} + Z_S}$$

We also know that

$$\tau_{in} = \frac{z_{in} - z_0}{z_{in} + z_0}$$

Multiply both sides by $z_{in} + z_0$

$$\tau_{in} (z_{in} + z_0) = z_{in} - z_0$$

$$\tau_{in} z_{in} + \tau_{in} z_0 = z_{in} - z_0$$

$$(\tau_{in} - 1) z_{in} = -(1 + \tau_{in}) z_0$$

Multiply by -1 and solve z_{in}

$$(1 - \tau_{in}) z_{in} = (1 + \tau_{in}) z_0$$

$$z_{in} = z_0 \left(\frac{1 + \tau_{in}}{1 - \tau_{in}} \right)$$

so

$$v_i = v_s \frac{z_{in}}{z_s + z_{in}} = v_i^+ + v_i^- = v_i^+ (1 + \tau_{in})$$

Now;

$$v_s \frac{z_{in}}{z_s + z_{in}} = v_i^+ (1 + \tau_{in})$$

$$v_i^+ = \frac{v_s \frac{z_{in}}{z_s + z_{in}}}{1 + \tau_{in}} \quad \text{--- (6)}$$

we also know that

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \Rightarrow Z_{in} = Z_0 \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right)$$

same for source

$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} \Rightarrow Z_S = Z_0 \left(\frac{1 + \Gamma_S}{1 - \Gamma_S} \right)$$

Sub ⑦ & ⑧ in ⑥

$$v_i^+ = v_s \cdot \frac{\frac{Z_{in}}{Z_S + Z_{in}}}{1 + \Gamma_{in} (1 + \Gamma_S)} = v_s (1 - \Gamma_S)$$
$$v_i^+ = v_s \left(Z_0 \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right) \right) / \frac{Z_S + Z_{in}}{1 + \Gamma_{in}}$$

$$v_i^+ = v_s \cdot \frac{Z_0 \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right)}{\frac{Z_0 \left(\frac{1 + \Gamma_S}{1 - \Gamma_S} \right) + Z_0 \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right)}{1 + \Gamma_{in}}}$$

$$v_i^+ = v_s \cdot \frac{Z_0 \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right)}{\frac{Z_0 \left[\left(\frac{1 + \Gamma_S}{1 - \Gamma_S} \right) + \left(\frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right) \right]}{1 + \Gamma_{in}}}$$

$$v_1^+ = v_s \cdot \frac{\left[\frac{(1 + \tau_{in})}{1 - \tau_{in}} \right]^{m_i} - 1}{\left[\frac{(1 + \tau_s)}{1 - \tau_s} + \frac{(1 + \tau_{in})}{1 - \tau_{in}} \right]} \quad \text{①}$$

$$v_1^+ = \frac{v_s}{1 + \tau_{in}} \cdot \frac{\left[\frac{(1 + \tau_{in})}{1 - \tau_{in}} \right]^{m_i} - 1}{\left[\frac{(1 + \tau_s)}{1 - \tau_s} + \left(\frac{(1 + \tau_{in})}{1 - \tau_{in}} \right)^{m_i} - 1 \right]} \quad \text{②}$$

Multiply ② with $(1 - \tau_s)(1 - \tau_{in})$ on both sides

$$v_1^+ = \frac{v_s}{1 + \tau_{in}} \cdot \frac{\left[\frac{(1 + \tau_{in})}{1 - \tau_{in}} \right]^{m_i} (1 - \tau_s)(1 - \tau_{in})}{\left[\frac{(1 + \tau_s)}{1 - \tau_s} + \left(\frac{(1 + \tau_{in})}{1 - \tau_{in}} \right)^{m_i} \right] (1 - \tau_s)(1 - \tau_{in})}$$

$$v_1^+ = \frac{v_s}{1 + \tau_{in}} \cdot \frac{(1 + \tau_{in})(1 - \tau_s)}{(1 + \tau_s)(1 - \tau_{in}) + (1 + \tau_{in})(1 - \tau_s)}$$

$$v_1^+ = v_s \cdot \frac{1 - \tau_s}{(1 + \tau_s)(1 - \tau_{in}) + (1 + \tau_{in})(1 - \tau_s)} \quad \text{③}$$

① Expanding $\frac{(1+\tau_s)(1-\tau_{in})}{(1-\tau_s)(1-\tau_{in})}$ $\left(\frac{1+\tau_s}{1-\tau_s}\right) \cdot 2V = P_{IV}$

$$(1+\tau_s)(1-\tau_{in}) = (1-\tau_{in}) + \tau_s(1-\tau_{in})$$
$$\Rightarrow 1-\tau_{in} + \tau_s(1-\tau_{in})$$

②

$$(1+\tau_{in})(1-\tau_s) = (1-\tau_s) + \tau_{in}(1-\tau_s)$$

Adding Both

$$(1-\tau_{in}) + \tau_s(1-\tau_{in}) + (1-\tau_s) + \tau_{in}(1-\tau_s)$$

$$1 - \tau_{in} + \tau_s - \tau_s \tau_{in} + 1 - \tau_s + \tau_{in} - \tau_{in} \tau_s$$

$$\alpha - 2\tau_s \tau_{in} = \alpha(1 - \tau_s \tau_{in}) \quad \text{--- (10)}$$

Sub (10), $\alpha = \frac{V_1 + V_2}{2}$

$$V_1 + = V_2 \left[\frac{1 - \tau_s}{2(1 - \tau_s \tau_{in})} \right]$$

$$V_1 + = \frac{V_2}{2} \frac{1 - \tau_s}{1 - \tau_s \tau_{in}} \quad \text{--- (11)}$$

By poynting's theorem

$$P_{in} = \frac{1}{2} |V_1 +|^2 (1 - \tau_{in}^2)$$

Sub (11) here

$$P_{\text{in}} = \frac{|V_S|^2}{8Z_0} \frac{|(1 - T_S)|^2}{|1 - T_S T_{\text{in}}|^2} (1 - |T_{\text{in}}|^2)$$

By Poynting's theorem

$$P_L = \frac{|V_A|^2}{2Z_0} (1 - |T_L|^2)$$

From ②

$$V_A = S_{21} V_1 + S_{22} T_L V_2$$

$$V_A (1 - S_{22} T_L) = S_{21} V_1$$

$$V_A = \frac{S_{21} V_1}{1 - S_{22} T_L}$$

$$|V_A|^2 = \frac{|S_{21}|^2 |V_1|^2}{|1 - S_{22} T_L|^2}$$

$$P_L = \frac{|V_S|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |T_L|^2) |1 - T_S|^2}{|1 - S_{22} T_L|^2 |1 - T_S T_{\text{in}}|^2}$$

$$G_L = \frac{P_L}{P_{\text{in}}} = \frac{\frac{|V_S|^2}{8Z_0} \frac{|S_{21}|^2 (1 - |T_L|^2)^2 (1 - |T_S|^2)^2}{|1 - S_{22} T_L|^2 |1 - T_S T_{\text{in}}|^2}}{\frac{|V_S|^2}{8Z_0} \frac{|(1 - T_S)|^2 (1 - |T_{\text{in}}|^2)}{|1 - T_S T_{\text{in}}|^2}}$$

$$G_1 = \frac{1V_S|^2}{8Z_0} \frac{18|s_1|^2 (1 - |T_L|^2) (1 - |s_1|^2)}{|1 - s_22 T_L|^2 |1 - r_s T_{in}|^2} \times \frac{8Z_0}{1V_S|^2} \frac{(1 - r_s T_{in})^2}{(1 - s_1)^2 (1 - r_{in})^2}$$

$$G_1 = \frac{18|s_1|^2 (1 - |T_L|^2)}{(1 - |r_{in}|^2) (1 - s_22 T_L)^2}$$

— 12

proper match, power Gain.

Available power Gain:

Input side matched, thro complex conjugate match

$$P_{in} = \frac{1}{8Z_0} (V_i +)^2 (1 - |r_{in}|^2)$$

$$= \frac{1V_S|^2}{8Z_0} \frac{|1 - r_s|^2}{|1 - r_s T_{in}|^2} (1 - |r_{in}|^2)$$

$$P_{avS} = P_{in} |T_{in}|^2 \quad T_{in} = r_s^*$$

$$= \frac{1V_S|^2}{8Z_0} \frac{|1 - r_s|^2}{|1 - r_s r_s^*|^2} (1 - |r_s^*|^2)$$

Available power gain

$$G_A = \frac{P_{SVR}}{P_{AVS}}$$

$$G_T = \frac{P_L}{P_{AVS}}$$

only real component (remove)

Complex

$$P_{AVS} = \frac{|V_S|^2}{8Z_0} \frac{|1 - \Gamma_S|^2}{(1 - |\Gamma_S|^2)} \quad \checkmark \quad (13)$$

power available in the network

P_{AVN}, maximum power delivered to

load

$$P_L = \frac{|V_I|^2}{8Z_0} \frac{18|\Gamma| |(1 - \Gamma_L)|^2}{|1 - S_{22}\Gamma_L|^2} \quad (1 - \Gamma_L)^2$$

$$P_L = \frac{|V_S|^2}{8Z_0} \frac{|S_{21}| |(1 - \Gamma_L)|^2 (1 - \Gamma_S)^2}{|1 - S_{22}\Gamma_L|^2 |1 - \Gamma_S T_{in}|^2} \quad (13.a)$$

$$P_{AVN} = P_L | \Gamma_L = \Gamma_{out}$$

we know that

$$T_{in} = \gamma_{11} + \frac{\gamma_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \quad (13.b)$$



$$T_{out} = S_{22} + \frac{S_{12} S_{21} T_S}{1 - S_{11} T_S}$$

$$(1 - T_S T_{in}) = 1 - T_S \left(S_{11} + \frac{S_{12} S_{21} T_L}{1 - S_{22} T_L} \right)$$

$$= (1 - S_{22} T_L) - T_S \left[(S_{11} (1 - S_{22} T_L)) + S_{12} S_{21} T_L \right]$$

$$\frac{(1 - S_{22} T_L)}{(1 - S_{22} T_L - T_S)} = 1 - T_S$$

$$= (1 - S_{22} T_L) - S_{11} T_S (1 - S_{22} T_L) - S_{12} S_{21} T_S T_L$$

$$= (1 - S_{22} T_L) [1 - S_{11} T_S] - S_{12} S_{21} T_S T_L$$

$$\frac{(1 - S_{22} T_L)}{(1 - S_{22} T_L - S_{12} S_{21} T_S T_L)} = 1 - T_S$$

wkt $T_{out} = S_{22} + \frac{S_{12} S_{21} T_S}{1 - S_{11} T_S}$

$$T_{out} = S_{22} (1 - S_{11} T_S) + S_{12} S_{21} T_S$$

$$\frac{S_{12} S_{21} T_S}{1 - S_{11} T_S} = S_{22} (1 - S_{11} T_S)$$

$$T_{out} (1 - S_{11} T_S) = S_{22} (1 - S_{11} T_S) + S_{12} S_{21} T_S$$

$$S_{12} S_{21} T_S = (1 - S_{11} T_S) T_{out} - S_{22} (1 - S_{11} T_S)$$

$$L(15)$$

out ⑤ in ④

$$(1 - S_{22} \Gamma_L) (1 - S_{11} \Gamma_S) - [(1 - S_{11} \Gamma_S) \Gamma_{out} - S_{22} (1 - S_{11} \Gamma_S)] \Gamma_L$$

$$1 - S_{22} \Gamma_L$$

Factor of $(1 - S_{11} \Gamma_S)$

$$(1 - S_{11} \Gamma_S) [(1 - S_{22} \Gamma_L) - \Gamma_{out} \Gamma_L + S_{22} \Gamma_L]$$

$$1 - S_{22} \Gamma_L$$

$$(1 - S_{11} \Gamma_S) (1 - S_{22} \Gamma_L - \Gamma_{out} \Gamma_L + S_{22} \Gamma_L)$$

$$1 - S_{22} \Gamma_L$$

$$\frac{(1 - S_{11} \Gamma_S) (1 - \Gamma_{out} \Gamma_L)}{1 - S_{22} \Gamma_L} = 1 - \Gamma_S \Gamma_{in}$$

NOW $\left| \begin{array}{l} 1 - \Gamma_S \Gamma_{in} \\ \Gamma_L = \Gamma_{out}^* \end{array} \right.$

$$= \frac{(1 - S_{11} \Gamma_S) (1 - \Gamma_{out} \Gamma_{out}^*)}{1 - S_{22} \Gamma_{out}^*}$$

$$= \frac{(1 - S_{11} \Gamma_S) (1 - \Gamma_{out} \Gamma_{out}^*)}{1 - S_{22} \Gamma_{out}}$$

$$\frac{|1 - T_{S1} \omega_n|^2}{|1 - S_{22} T_{out}|^2} = |1 - 8_{11} T_3|^2 (1 - |T_{out}|^2)^2$$

(16)

Sub (16) in (13.a) and $T_L = T_{out}^*$

$$P_L = \frac{|V_{S1}|^2}{8Z_0} \frac{|8_{21}|^2 (1 - |T_{out}|^2) (1 - |T_3|^2)}{|1 - 8_{22} T_{out}|^2 \cdot |1 - 8_{11} T_3|^2 (1 - |T_{out}|^2)^2}$$

$$P_{avm} = \frac{|V_{S1}|^2}{8Z_0} \frac{|8_{21}|^2 (1 - |T_{out}|^2) (1 - |T_3|^2)}{|1 - 8_{11} T_3|^2 (1 - |T_{out}|^2)^2}$$

$$P_{avm} = \frac{|V_{S1}|^2 |8_{21}|^2 (1 - T_3)^2}{8Z_0 |1 - 8_{11} T_3|^2 (1 - |T_{out}|^2)}$$

(17)

Available power G_A

$$G_A = \frac{P_{avm}}{P_{av8}}$$

$$= \frac{|V_{S1}|^2 |8_{21}|^2 (1 - |T_3|^2)}{8Z_0 |1 - 8_{11} T_3|^2 (1 - |T_{out}|^2)} \times \frac{\frac{8Z_0 (1 - |T_3|^2)}{|V_{S1}|^2 (1 - |T_3|^2)}}{|V_{S1}|^2 (1 - |T_3|^2)}$$

$$G_{IA} = \frac{18211^2 (1 - |\Gamma_{S1}|^2)}{(1 - 822\Gamma_S)^2 (1 - |\Gamma_{out}|^2)} \quad (18)$$

Transducer power gain G_{IT}

$$G_{IT} = \frac{P_L}{P_{avS}}$$

$$= \frac{1V_S|^2}{8Z_0} \times \frac{18211^2 (1 - |\Gamma_L|^2) (1 - |\Gamma_S|^2)}{(1 - 822\Gamma_L)^2 (1 - \Gamma_S \Gamma_{in})^2} \times \frac{8Z_0 (1 - |\Gamma_S|^2)}{|1V_S|^2 / (1 - |\Gamma_S|^2)}$$

$$G_{IT} = \frac{18211^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{(1 - \Gamma_S \Gamma_{in})^2 |1 - 822\Gamma_L|^2} \quad (19)$$

A special case of G_{IT} when both out and input are matched for zero reflection (in contrast to conjugate matching) then $\Gamma_L = \Gamma_S = 0$ hence

$$G_{IT} = 18211^2$$

Another case is unilateral transducer power gain G_{ITU} , where $S_{12} = 0$

From (13.b) $\Gamma_{in} = S_{11}$ when $S_{12} = 0$

hence in (19)

$$G_{TU} = \frac{1821.1^2 (1 - |S_{11}|^2) (1 - |S_{21}|^2)}{|1 - S_{11}S_2|^2 |1 - S_{22}S_1|^2}$$

1. For $Z_0 = 50\Omega$ the operating freq. of χ^a is 1GHz and 8 parameters are $S_{11} = 0.5 \angle -100^\circ$

$$S_{12} = 0.25 \angle 80^\circ$$

$$S_{21} = 0.5 \angle 70^\circ$$

$$S_{22} = 0.15 \angle -25^\circ$$

Find power gain, Available power gain and Transducer power gain where source impedance is 25Ω and load impedance is 40Ω .

$$\frac{\text{Gain}}{\text{dB}} = \frac{Z_L - Z_0}{Z_0 + Z_L} = \frac{40 - 50}{25 + 50} = -0.333 \text{ dB}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{40 - 50}{40 + 50} = -0.111$$

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$0 = S_{12} \text{ makes } 16 = 40 \quad \text{(d.e)} \quad \text{incorrect}$$

(P) do work

$$T_{in} = ((0.5 \angle -100^\circ) + \frac{((0.85 \angle 30^\circ)(5 \angle 70^\circ)(-0.111))}{(-0.05030 + 0.0234j)})$$

$$= -0.06099 - 0.6219j$$

$$T_{in} = 0.68490 \angle -95.60^\circ$$

$$T_{out} = \frac{s_{22} + s_{12}s_{21}T_8}{1 - s_{11}T_8}$$

$$(P_{out}.d\delta)_{cal,01} = [P_{out}.d\delta = 0]$$

$$T_{out} = ((0.5 \angle 25^\circ) + \frac{((0.25 \angle 30^\circ)(5 \angle 70^\circ)(-0.333))}{(1 - ((0.5 \angle 100^\circ)(-0.111)))})$$

$$= 0.5486 - 0.61995^\circ$$

$$= 0.8218 \angle -48.489$$

$$T_{out} = 0.8516 \angle -45.698$$

The power Gain

$$G_1 = 18^2(1 - |T_L|^2)$$

$$\frac{18^2}{(1 - |T_{in}|^2)(1 - |s_{22}T_L|^2)} = 40$$

$$s_1 G_1 = (0.85)^2 = 0.0625$$

$$s_{21} = (5)^2 = 25$$

$$G_1 = \frac{25 \times 0.987679}{0.60949 \times (1.05056)^2}$$

$$G_1 = \frac{25 \times 0.987679}{0.60949 \times 1.10868}$$

$$= \frac{24.6919}{0.672681}$$

$$\boxed{G_1 = 36.7067}$$

$$10 \log(36.7067) = 15.647 \text{ dB}$$

Available power Gain:

$$G_{IA} = \frac{(821)^2 (1 - |T_S|^2)}{|1 - S_{11} T_S|^2 (1 - |T_{out}|^2)}$$

$$= \frac{25 \times 0.889111}{0.96989 \times 0.87477}$$

$$= \frac{22.2277}{0.266496}$$

$$\boxed{G_{IA} = 83.4072}$$

$$10 \log(83.4072) = 19.212 \text{ dB}$$

Transducer power Gain:

$$G_T = \frac{(S_21)^2 (1 - |T_S|^2) (1 - |T_L|^2)}{(1 - |T_{in}|^2)(1 - S_{22}|T_L|^2)}$$
$$= \frac{25 \times 0.889111 \times 0.987679}{1.002682 \times 1.103680}$$
$$= \frac{21.95390}{1.106640}$$

$$G_T = 19.838$$

$$10 \log(19.833) = 13 \text{ dB.}$$

01.09.85

stability :

- maintaining between i/p & o/p .
- Based on i/p & o/p matching conditions we check for the \star stability
- system gain should not vary based on input and output load $\Rightarrow \star$ design.

5 Tests

- * $K-\Delta$ Test (Routh's condition)
- * stability circle - Smith chart
- * μ -Test

stability in two ways

- * unconditionally stable

$|T_{in}| < 1$ for any load $|T_L| |T_S|$

* conditionally stable (unstable)

$$|\Gamma_{in}| < 1 \quad \text{range of } \Gamma_S + \Gamma_L$$

(retaining $\Gamma_S + \Gamma_L$ in range \rightarrow stable else not)

$$|\Gamma_{in}| = \left| \frac{s_{11} + s_{12}s_{21}\Gamma_L}{1 - s_{22}\Gamma_L} \right| < 1$$

$$|\Gamma_{out}| = \left| \frac{s_{22} + s_{21}s_{12}\Gamma_S}{1 - s_{11}\Gamma_S} \right| < 1$$

If unilateral $s_{12} = s_{21} = 0$ (No transition)

$$|\Gamma_{in}| = s_{11}$$

$$|\Gamma_{out}| = s_{22}$$

Plane of $\Gamma_L + \Gamma_S \leftarrow \Gamma_{in} + \Gamma_{out}$

unilateral \leftarrow basis, accounts on it

K - Δ Test:

For stable system

$$\Delta = s_{11}s_{22} - s_{12}s_{21} < 1$$

$$K = \frac{1 - s_{11}^2 - s_{22}^2 + \Delta^2}{2s_{12}s_{21}} > 1$$

If any one satisfies \Rightarrow marginally stable

- * $K > 1 ; \Delta \angle 1 \Rightarrow$ unconditionally stable (Aim)
- * $K < 1 ; \Delta \angle 1 (\text{or}) K > 1 ; \Delta \angle 1$
- * $K < 1 ; \Delta \angle 1 \Rightarrow$ unstable

+ Fix Bias

+ stability \Rightarrow check Noise figure F_{noise}

$S_{11}, \angle 1$ & proper match at load \Rightarrow stable

Range of stability $\rightarrow \sigma$ -circle

μ -Test :

$$\frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}| + |S_{12}S_{21}|}$$

$\mu > 1 = \text{stable}$


$\mu < 1 = \text{unstable}$


Stability circle :

center C_L ; Radius $= R_L \Rightarrow$ output stability

center C_S ; Radius $R_S \Rightarrow$ Input stability

$$|S_{11}| < 1$$

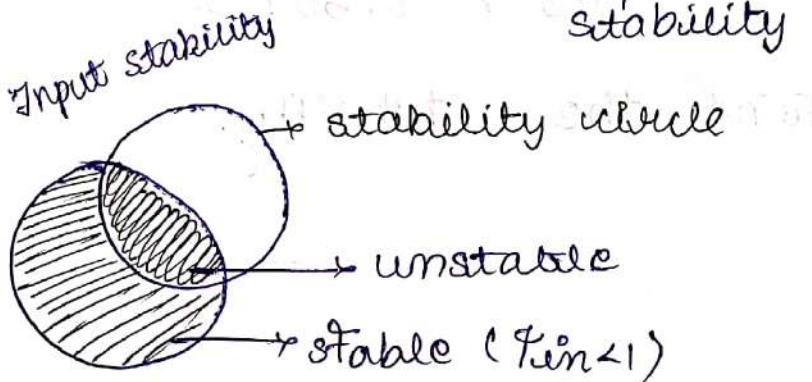

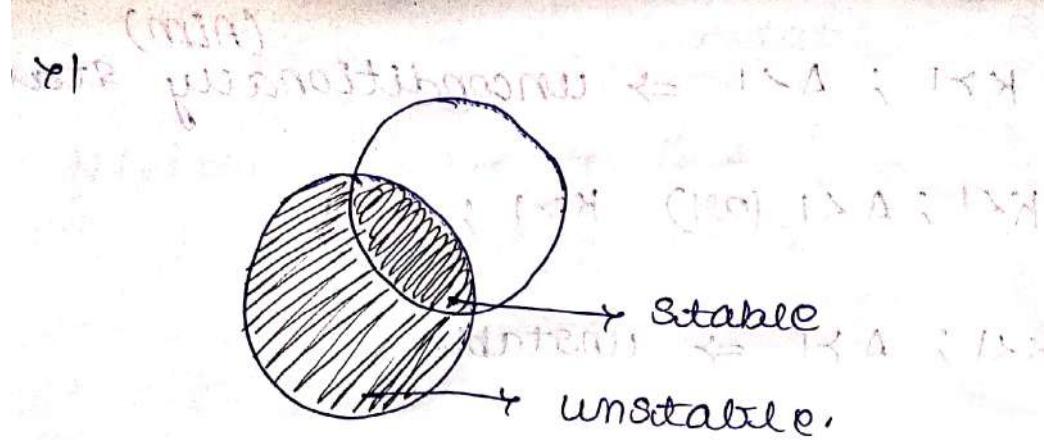

$$G = \frac{(s_{11} - \Delta s_{22}^*)^*}{|s_{11}|^2 - |\Delta|^2}$$

$$R_S = \frac{|s_{12}s_{21}|}{|s_{11}|^2 - |\Delta|^2}$$

$$R_L = \frac{(s_{22} - \Delta s_{11}^*)^*}{|s_{22}|^2 - |\Delta|^2}$$

$$R_L = \frac{|s_{12}s_{21}|}{|s_{22}|^2 - |\Delta|^2}$$

For $s_{11} = 0.869 \angle 159^\circ - A$

~~two two~~ $s_{12} = 0.031 \angle 9^\circ - B$

~~two two~~ $s_{21} = 4.250 \angle 61^\circ - C$

~~two two~~ $s_{22} = 0.507 \angle -117^\circ - D$

in the stability.

→ complex mode

→ Type $0.869 \angle -159^\circ \Rightarrow$ Shift + RCL press A.

make others as B, C, D/M.

To call press Alpha + variable

soln

$$\Delta = S_{11}S_{22} - S_{12}S_{21} \\ = 0.336182 \angle -95.986$$

a) K - Δ Test

$$K = \frac{1 - 1811^2 - 1822^2 + |\Delta|^2}{2|S_{12}S_{21}|} \\ = \frac{1 - (0.869)^2 - (0.507)^2 + (0.336)^2}{2 \times 0.13175} \\ = \frac{1 - (0.869)^2 - (0.507)^2 + (0.336)^2}{0.12635}$$

$$K = 0.3821 < 1$$

$$\Delta = 0.336182 < 1$$

conditionally stable

$$\text{and } 0.3821 < 1 \text{ & } 0.336182 < 1$$

$$\text{and } 0.3821 < 0.336182 \approx 0.3360 \approx 1$$

b) S-circle

I/p stability circle

$$c_S = \frac{(S_{11} - \Delta S_{22}^*)}{|S_{11}|^2 - |\Delta|^2} * \text{Polar form}$$

$$R_S = \frac{|S_{12} S_{21}|}{|S_{11}|^2 - |\Delta|^2}$$

O/p stability circle

$$c_L = \frac{(S_{22} - \Delta S_{11}^*)}{|S_{22}|^2 - |\Delta|^2} * \text{Polar form}$$

$$R_L = \frac{|S_{12} S_{21}|}{|S_{22}|^2 - |\Delta|^2}$$

I/P S.C. + (Feedback) - (Losses) =

$$c_S = (1.094 L - 16\alpha)^* = 1.09 L 16\alpha$$

$$R_S = 0.205$$

O/p

$$c_L = (1.592 L - 132.3)^* = 1.592 L 132.3$$

$$R_L = 0.91395$$


Basic radius = 7.6 cm;

$$\underline{c_S} \Rightarrow 1.09 \times R = 1.09 \times 7.6 = 8.284 \text{ cm}$$

$$\underline{R_S} \Rightarrow 0.205 \times R = 0.205 \times 7.6 = 1.558 \text{ cm}$$

DATE

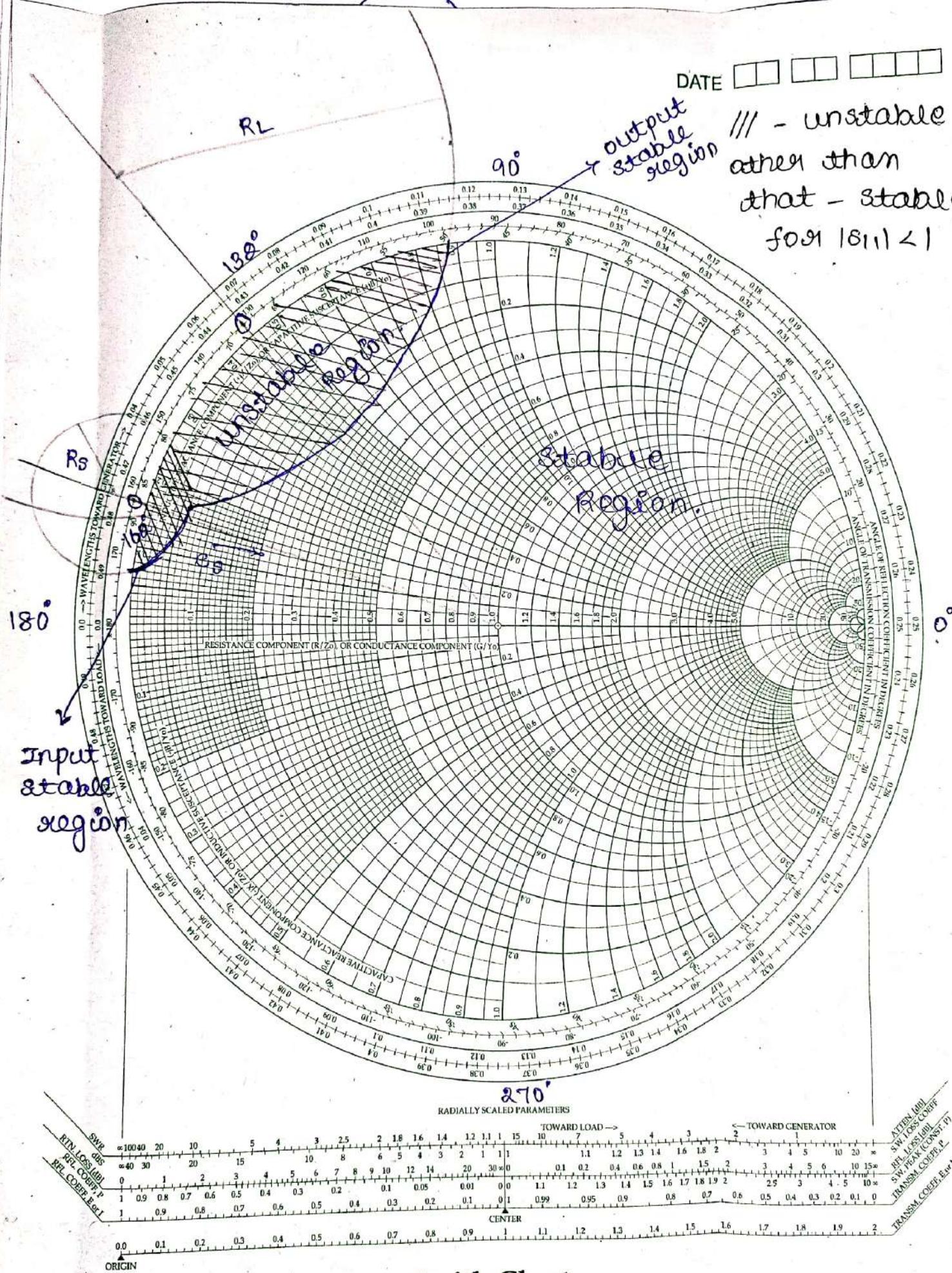*output
stable
region* // - unstable
other than
that - stable
for $1811 \angle 1$



Smith Chart

$$G_L = 1.592 \times 7.6 = 12.0992$$

$$R_L = 0.9189 \times 7.6 = 6.94556$$

c) M-TPSit

$$= \frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}^*| + |S_{12}S_{21}|}$$

$$= \frac{1 - (0.869)^2}{0.8895 + 0.13175}$$

$$= \frac{0.244839}{0.36125}$$

$$\mu = 0.6777$$

$\mu < 1 \Rightarrow$ unstable

3. FOR $S_{11} = 1.08 \angle -159^\circ$

$$S_{12} = 0.031 \angle -9^\circ$$

$$S_{21} = 4.850 \angle 61^\circ$$

$$S_{22} = 1.52 \angle -117^\circ$$

check for stability using all 3 Tests.

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

$$\Delta = 1.4403 \angle 86.7783$$

a) K - Δ Test

$$K = \frac{1 - |s_{11}|^2 - |s_{22}|^2 + |\Delta|^2}{2|s_{12}s_{21}|}$$

$$K = \frac{1 - 1.0404 - 2.3104 + 2.07446}{2 \times 0.13175} = 1.1384 - 0.024$$

$$K = -1.0487$$

$K < 1$ $\Delta \neq 1$ conditionally stable

b) μ - Test

$$\mu = \frac{1 - |s_{11}|^2}{|s_{22} - \Delta s_{11}| + |s_{12}s_{21}|}$$

$$\mu = \frac{1 - (1.02)^2}{0.08854 + 0.13175}$$

$$= \frac{-0.0404}{0.22029}$$

$$= -0.1883$$

$\mu < 1$ primary residence may stabilize

conditionally stable

$$0.8854 - 0.08854 = 4$$

Stability circle:

0

I/p stability circle:

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)}{(S_{11})^2 - |\Delta|^2}$$

$$C_S = (1.1332 \angle -154)^\circ$$

$$C_S = (1.1332 \angle -154)^\circ = 1.1332 \angle 154$$

$$R_S = \frac{1812 S_{21}}{1811^2 - |\Delta|^2} = \frac{0.13175}{0.0340}$$

$$R_S = 0.12740$$

30 k.p. Stability circle margin graph of

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)}{(S_{22})^2 - |\Delta|^2}$$

$$C_L = (0.87528 \angle -170.5)^\circ$$

$$C_L = 0.87528 \angle 170.5$$

$$R_L = \frac{1812 S_{21}}{1822^2 - |\Delta|^2} = \frac{0.13175}{0.2359}$$


$$R_L = 0.558414$$

$$C_S = 7.6 \times 1.132 = 8.6032$$

$$R_S = 7.6 \times 0.12740 = 0.96824$$

1zin1x1

DATE

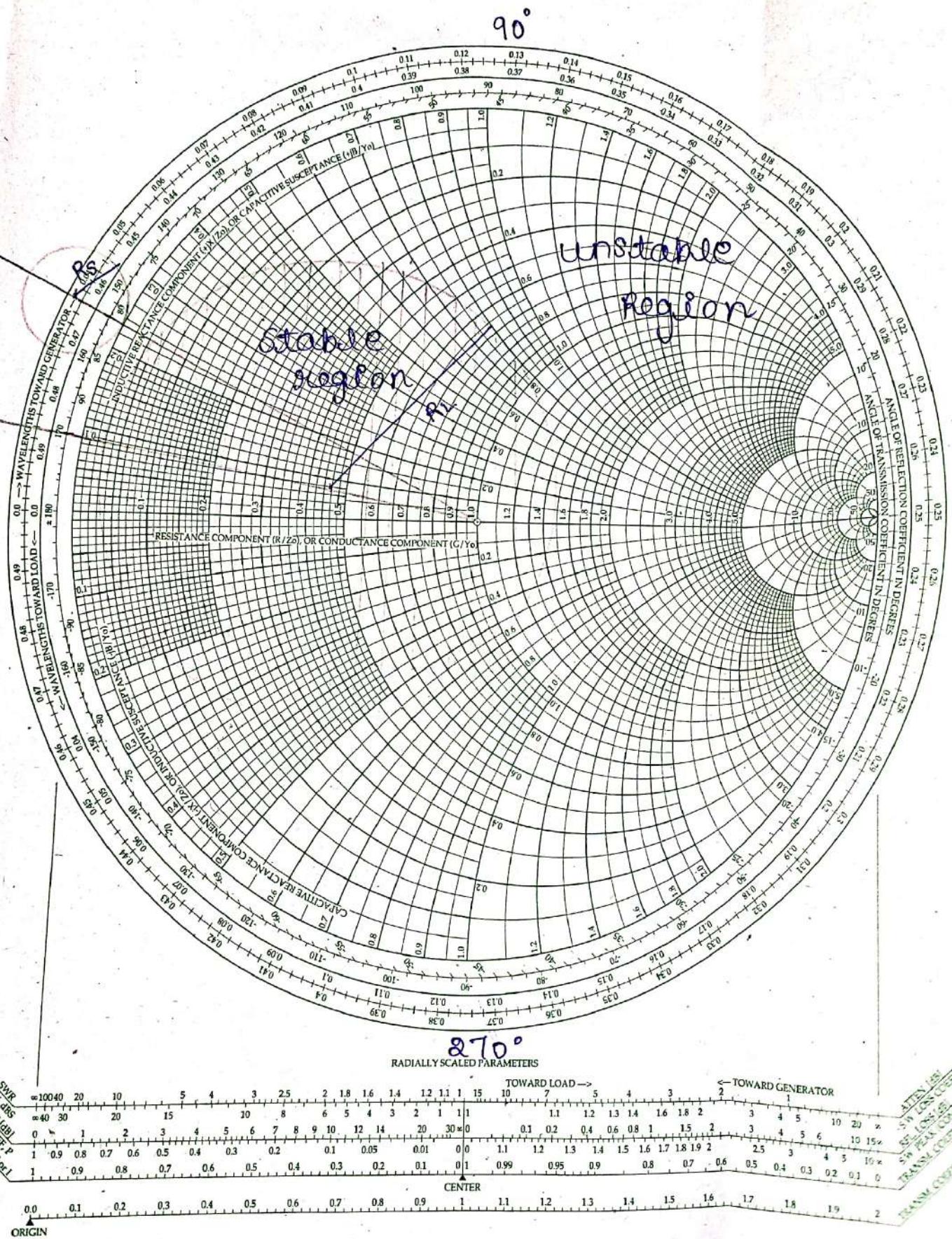

Smith Chart

$$Q_L = 7.6 \times 0.87528$$

$$Q_L = 6.85212$$

$$R_L = 0.55841 \times 7.6$$

$$R_L = 4.2189$$

Q3. Q9. & 5.


Higher the input impedance,
higher the gain.


- Imp for design.
- stability of system.
- Gain of system
- To design proper matching at input and output, By that achieving better gain so we tend to match complex conjugate.

$$S_S = S_{in}^*$$

$$S_{in} = S_S^*$$

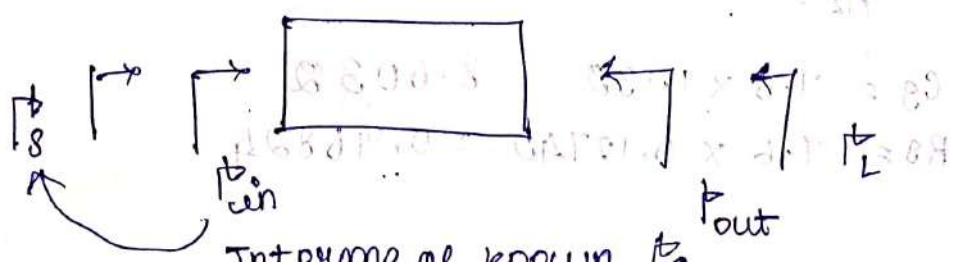- calculate S_S
- once knowing S_S and S_L we can design



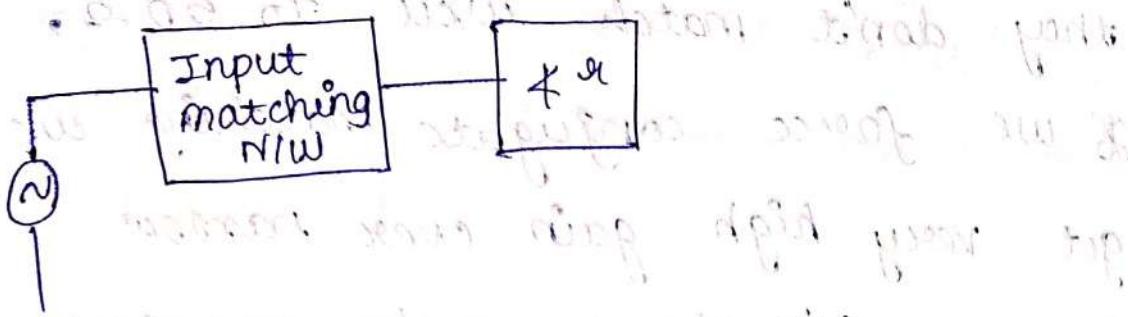

single stage Transistor Amplifier Design

conjugate matching

$$r_{in} = r_s^* \quad r_{out} = r_L^*$$


matching \rightarrow Transducer gain G_{IT}

- * After stability of transistor has been determined and stable regions for r_s and r_L have been located on Smith chart, the input and output section can be designed (matching).

- * G_{IT} is fixed for a transistor. The overall amplifier gain depend on how well we design source gain (G_S) and load gain (G_L). Maximum gain occurs only when we achieve conjugate matching (input & output impedances are complex conjugates of Transistor's Impedances)

- * Real transistors often have large reflection coefficients ($|S_{11}|, |S_{22}|$) as

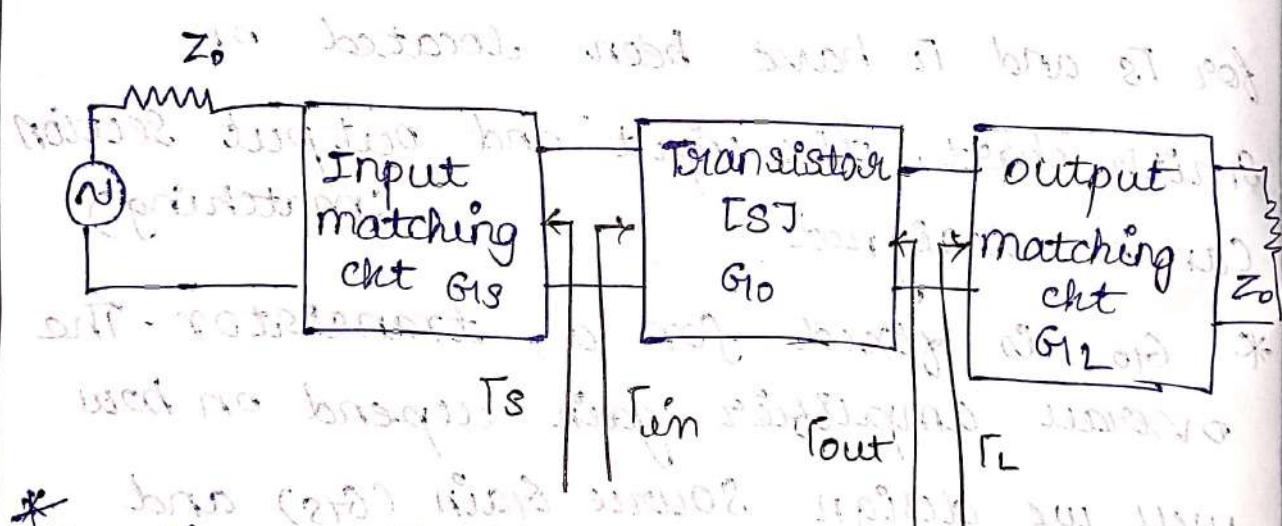they don't match well to $50\ \Omega$, & we force conjugate matching w/ get very high gain over narrow frequency band. To make amplifier work over wider bandwidth, designers reduce gain by choosing a match that is not perfect (less than maximum) which gives balanced and useful frequency response.



* A single stage microwave transistor amplifier can be modeled by the above circuit where matching networks are used on both sides of transistor to transform the input and output impedances Z_0 to source and load impedances Z_s and Z_L .

* The most useful gain is Transistor power gain which accounts both source and load mismatch

What

$$G_{IT} = \frac{18g_{m1}^2 (1 - |T_{S1}|^2) (1 - |T_{L1}|^2)}{|1 - T_{S1}T_{L1}|^2 |1 - S_{22}T_{L1}|^2}$$

We can define separate effective gain factors for input (source) matching network, the transistor and output (load) matching networks

$$G_{IS} = \frac{1 - |T_{S1}|^2}{|1 - T_{S1}T_{en}|^2}$$

$$G_{IO} = 18g_{m1}^2$$

$$G_{IL} = \frac{1 - |T_{L1}|^2}{|1 - S_{22}T_{L1}|^2}$$

$$\text{Overall } G_{IT} = G_{IS} G_{IO} G_{IL}$$

The Effective gains G_{IS} and G_{IL} of matching network may be greater than unity, because the unmatched transistor would incur power loss due to reflections at input and output of network transistor and matching action can reduce these losses

If the transistor is unilateral

$S_{12} = 0$ then $T_{in} = S_{11}$, $T_{out} = S_{22}$

$$G_{TU} = G_{1S} G_{1O} G_{1L}$$

$$G_{1S} = \frac{1 - |TS|^2}{|1 - S_{11} TS|^2}$$

$$G_{1O} = \frac{1 - |TL|^2}{|1 - S_{22} TL|^2} = T_{1O}$$

$$G_{1L} = \frac{1 - |TL|^2}{|1 - S_{22} TL|^2} = T_{1L}$$

Now $G_{1S} = \frac{1 - |TS|^2}{|1 - S_{11} TS|^2}$ and $G_{1O} = \frac{1 - |TL|^2}{|1 - S_{22} TL|^2}$ and we just take the two conditions for a maximum

The maximum power transfer from input matching network to transistor will occur when

$$T_{in} = T_S^* \quad \text{--- ①}$$

The maximum power transfer from transistor to output matching network will occur when

$$T_{out} = T_L^* \quad \text{--- ②}$$

Assuming lossless matching sections, these conditions maximize overall Transducer gain

$$G_{TU} = \frac{(1 - |TS|^2)^2 (1 - |TL|^2)^2}{(1 - S_{11} TS)^2 (1 - S_{22} TL)^2}$$

and two bias supplies to maintain optimum operating conditions.

$$T_{in} = T_S^* \text{ in } G_{IS} \text{ hence}$$

$$|1 - T_S T_{in}|^2 = (1 - |T_S|^2)^2$$

$$G_{IS} = \frac{(1 - |T_S|^2)^2}{(1 - |T_S|^2)(1 - |T_S|^2)} = \frac{1}{1 - |T_S|^2}$$

$$T_{out} = T_L * \text{ in } G_{IL}$$

$$G_{IL} = \frac{1 - |T_L|^2}{|1 - S_{22}T_L|^2}$$

$$G_{ITmax} = \frac{1}{1 - |T_S|^2} \cdot (1 - |S_{21}|^2) \cdot \frac{1 - |T_L|^2}{|1 - S_{22}T_L|^2}$$

In addition with conjugate matching and lossless matching sections, the input and output ports of Γ_S matched to Z_0 .

In general case with bilateral ($S_{12} \neq 0$) T_{in} is affected by T_{out} so input and output sections must be matched simultaneously.

$$\text{wkt } T_{in} = \frac{S_{11} + S_{12}S_{21}T_L}{1 - S_{22}T_L}$$

$$T_{out} = \frac{S_{22} + S_{12}S_{21}T_S}{1 - S_{11}T_S}$$

Applying ① and ② above

$$T_S^* = S_{11} + \frac{S_{12}S_{21}T_L}{1 - S_{22}T_L}$$

$$T_L^* = \frac{s_{22} + s_{12}s_{21}T_S}{1 - s_{11}T_S}$$

To solve for T_S

$$T_S = \frac{s_{11} + s_{12}s_{21}T_L^*}{(1 - s_{22}T_L^*)} \quad (1)$$

$$(T_S^*)^* = s_{11}^* + \frac{s_{12}^* s_{21}^* T_L^*}{1 - s_{22}^* T_L^*} \quad (2)$$

airside N^* & P^* by T_L^*

$$T_S = \frac{s_{11}^* + s_{12}^* s_{21}^* T_L^*}{1 - s_{22}^* T_L^*} \quad (3)$$

Now: $T_L^* = s_{22} + \frac{s_{12}s_{21}T_S}{1 - s_{11}T_S}$

$$T_L^* = s_{22} + \frac{s_{12}s_{21}T_S}{1 - s_{11}T_S} \quad (4)$$

$$T_L^* = \frac{s_{22} + s_{22}s_{11}T_S + s_{12}s_{21}T_S}{1 - s_{11}T_S} \quad (5)$$

$$T_L^* = \frac{s_{22} + (s_{11}s_{22} - s_{12}s_{21})T_S}{1 - s_{11}T_S} \quad (6)$$

We know $\Delta = s_{11}s_{22} - s_{12}s_{21}$

$$T_L^* = \frac{s_{22} - \Delta T_S}{1 - s_{11}T_S} \quad (7)$$

Sub: T_L^* in T_S

$$\frac{1}{\Gamma_L^*} = \frac{1 - S_{11}\Gamma_S}{S_{22} - \Delta\Gamma_S}$$

$$\Gamma_S = [S_{11}^* + \frac{S_{12}^* S_{21}^*}{1 - S_{11}\Gamma_S} - \frac{S_{22}^*}{S_{22} - \Delta\Gamma_S}] +$$

$$[\Gamma (1 - S_{11}^* + S_{12}^* S_{21}^*)] + \Gamma (1 - S_{11}\Gamma_S - S_{22}^* (S_{22} - \Delta\Gamma_S))$$

$$\Gamma_S - S_{11}^* = \frac{S_{12}^* S_{21}^*}{1 - S_{11}\Gamma_S - S_{22}^* (S_{22} - \Delta\Gamma_S)}$$

$$\Gamma_S - S_{11}^* = \frac{S_{12}^* S_{21}^* (S_{22} - \Delta\Gamma_S)}{1 - S_{11}\Gamma_S - S_{22}^* (S_{22} - \Delta\Gamma_S)}$$

$$\Gamma_S - S_{11}^* = \frac{S_{12}^* S_{21}^* (S_{22} - \Delta\Gamma_S)}{1 - S_{11}\Gamma_S - S_{22}^* (S_{22} - \Delta\Gamma_S)} = S_{22}^* S_{21}^*$$

$$1 - S_{11}\Gamma_S - |S_{22}|^2 + S_{22}^* \Delta\Gamma_S$$

$$\Gamma (1 - S_{11}^* + |S_{22}|^2 - 1) + \Gamma (1 - S_{11}\Gamma_S - S_{22}^* \Delta\Gamma_S)$$

$$(\Gamma_S - S_{11}^*)(1 - S_{11}\Gamma_S - |S_{22}|^2 + S_{22}^* \Delta\Gamma_S) = S_{12}^* S_{21}^* (S_{22} - \Delta\Gamma_S)$$

$$\Rightarrow \Gamma_S - S_{11}\Gamma_S - \Gamma_S |S_{22}|^2 + S_{22}^* \Delta\Gamma_S - S_{11}^* + S_{11}^* S_{11}\Gamma_S + S_{11}^* |S_{22}|^2 - S_{11}^* S_{22}^* \Delta\Gamma_S = S_{12}^* S_{21}^* S_{22} - S_{12}^* S_{21}^* \Delta\Gamma_S$$

~~minimizing objective function~~

~~Grouping~~

$$[(\Delta S_{22}^* - S_{11})]^{\Gamma_S^2} + [(1 - |S_{22}|^2 + S_{11}^* S_{11} - S_{11}^* S_{22}^* \Delta + S_{12}^* S_{21}^* \Delta)] \Gamma_S$$

$$+ [-S_{11}^* + S_{11}^* |S_{22}|^2 - S_{12}^* S_{21}^* S_{22}^*] = 0$$

$$[(\Delta s_{22}^* - s_{11})] T_3^2 + [(1 - \Delta s_{22}^*)^2 + 18_{111}^2 - \Delta (s_{11}^* s_{22}^* - s_{12}^* s_{21}^*)] T_3 + [s_{11}^* (-1 + (\Delta s_{22}^*)^2) - s_{12}^* s_{21}^* s_{22}^*] = 0.$$

$$(\Delta s_{22}^* - s_{11}) T_3^2 + (1 - (\Delta s_{22}^*)^2 + 18_{111}^2 - 1\Delta)^2 T_3 + (-)[s_{11}^*(1 - (\Delta s_{22}^*)^2) + s_{12}^* s_{21}^* s_{22}^*] = 0.$$

$$(\Delta s_{22}^* - s_{11}) T_3^2 + (1 - (\Delta s_{22}^*)^2 + 18_{111}^2 - 1\Delta)^2 T_3 - s_{11}^* - s_{11}^* s_{22}^* s_{22}^* + s_{12}^* s_{21}^* s_{22}^*$$

$$(\Delta s_{22}^* - s_{11}) T_3^2 + (1 - (\Delta s_{22}^*)^2 + 18_{111}^2 - 1\Delta)^2 T_3 - (s_{11}^* - (\Delta s_{22}^* [s_{11}^* s_{22}^* - s_{12}^* s_{21}^*]))$$

$$(\Delta s_{22}^* - s_{11}) T_3^2 + (1 - (\Delta s_{22}^*)^2 + 18_{111}^2 - 1\Delta)^2 T_3 - (s_{11}^* - s_{22}^* \Delta^*)$$

→ common

$$(s_{11} - \Delta s_{22}^*) T_3^2 + (1\Delta^2 - |s_{11}| + 18_{221} - 1) T_3 + (s_{11}^* - \Delta^* s_{22}^*) = 0.$$

Solution to Quadratic Equation

$$T_3 = \frac{-B_1 \pm \sqrt{B_1^2 - 4AC_1}}{2C_1}$$

Similarly, for $T_2 = \frac{-B_2 \pm \sqrt{B_2^2 - 4AC_2}}{2C_2}$

$$r_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2|C_2|}$$

NOW $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$\therefore C_1 = S_{11} - \Delta S_{22}^*$$

$$\text{and } C_2 = -S_{22} - \Delta S_{11}^*$$

we know that

$$A = S_{11} - \Delta S_{22}^*$$

$$B = |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2 - 1/2$$

$$c = S_{11}^* - \Delta^* S_{22}$$

$$c = (S_{11} - \Delta S_{22}^*)^* = A^*$$

so constant is complex conjugate of quadratic coefficient

$$\text{let } C_1 = A = S_{11} - \Delta S_{22}^*$$

$$\text{hence } c = C_1^* = A^*$$

$$\text{wkt } r_S = \frac{B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$c = A^* \text{ hence}$$

$$r_S = \frac{-B \pm \sqrt{B^2 - 4(A)(A^*)}}{2A}$$

$$r_S = \frac{-B \pm \sqrt{B^2 - 4|\Delta|^2}}{2A}$$

But $A = c_1$ hence

$$T_S = B_1 \pm \sqrt{B_1^2 - 4|c_1|^2}$$

Always $K > 1$, thus unconditionally stable devices can always be conjugately matched for maximum gain and potentially unstable devices can be conjugately matched if $K > 1$ and $|A| < 1$

when $S_{12} = 0$ and $T_S = S_{11}$ and $R_L = S_{22}$

$$G_{ITU\ max} = \frac{S_{11}}{1 - S_{11}^2} \frac{(1821)^2}{1 - 18_{21}^2} \cdot 1$$

If the tr. is unconditionally stable $K > 1$ then

$$G_{IT\ max} = \frac{1821}{18_{12}^2} (K - \sqrt{K^2 - 1})$$

$G_{IT\ max}$ = matched gain.

G_{msg} = Maximum stable gain

$$G_{msg} = \frac{1821}{18_{12}^2}$$

- a. Design an Amplifier for maximum gain at 4 GHz using impedance matching network. calculate

and plot input return loss and gain from 3 GHz to 5 GHz. The transistor is a GaAs MESFET with the following S parameters with $Z_0 = 50 \Omega$

For 3 GHz

$$S_{11} = 0.80 \angle -89^\circ$$

$$S_{12} = 0.03 \angle 56^\circ$$

$$S_{21} = 2.86 \angle 99^\circ$$

$$S_{22} = 0.76 \angle -41^\circ$$

For 4 GHz

$$S_{11} = 0.72 \angle -116^\circ$$

$$S_{12} = 0.03 \angle 57^\circ$$

$$S_{21} = 2.60 \angle 76^\circ$$

$$S_{22} = 0.73 \angle -54^\circ$$

$$S_{11} = 0.66 \angle 142^\circ$$

$$S_{12} = 0.03 \angle 62^\circ$$

$$S_{21} = 2.39 \angle 54^\circ$$

$$S_{22} = 0.72 \angle -68^\circ$$

calculate i) K and ∇

ii) determine T_8 and T_L

iii) Final Gain

iv) Draw Impedance matching network

For 3 GHz

$$K = \frac{1 - S_{11}^2 - S_{22}^2 + |\Delta|^2}{2 |S_{12} S_{21}|}$$

$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

$$\Delta = 0.5916 \angle -121.94^\circ$$

$$K = \frac{0.13239}{2 \times 0.0858}$$

$$K = 0.7715 \text{ LO.}$$

$$\Delta = 0.592 < 1$$

$$K = 0.7715 < 1$$

Hence conditionally stable.

For 4GHz RPT

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

$$\Delta = 0.4875 \leq 1.62.28$$

$$K = \frac{0.18635}{2 \times 0.078}$$

$$K = 1.19455 \text{ is unconditionally stable (ii)}$$

$\Delta < 1 + K \gamma$ Hence unconditionally stable.

For 5GHz

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

$$\Delta = 0.41768 \leq 155.508$$

$$K =$$

$$\frac{0.22045}{2 \times 0.0717}$$

$$K = 1.537$$

$K \neq 0$ hence unconditional
stable

We can proceed with design at

4 GHz

i) To find maximum gain we
design matching sections for a conjugate
match to the transistor hence $T_S = T_{in}^*$

and $T_L = T_{out}^*$

$$T_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$T_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^*$$

$$C_2 = S_{22} - \Delta S_{11}^*$$

FOR 4 GHz

$$B_1 = 0.7479$$

$$B_2 = 0.7769$$

$$C_1 = 0.72 \angle 116^\circ - 0.355875 \angle -108.28 = 0.370448 \angle -123$$

$$C_2 = 0.73 \angle -54^\circ - 0.351 \angle 46.28 = 0.38507 \angle -61.033$$

$$T_8 = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2|C_1|}$$

$$T_8 = \frac{0.7479 \pm \sqrt{(0.7479)^2 - 4(0.370448)^2}}{2 \times 0.370448} \text{ } \underline{-128.4}$$

$$T_8 = \frac{0.7479 \pm 0.108115}{0.740896} \text{ } \underline{-128.4}$$

For stability take negative sign

$$T_8 = \frac{0.645785}{0.740896} \text{ } \underline{-128.4}$$

$$T_8 = 0.872 \text{ } \underline{128.4^\circ}$$

$$T_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2|C_2|} \text{ } \underline{14.2|C_2|} = 14.2|C_2| = 14.2 \times 0.38507 = 5.41891$$

$$T_L = \frac{0.7769 \pm \sqrt{(0.7769)^2 - 4(0.38507)^2}}{2 \times 0.38507} \text{ } \underline{-61.033}$$

$$= \frac{0.7769 \pm 0.102264}{0.37298 + 1.01j} \text{ } \underline{0.77014} \text{ } \underline{-61.033}$$

~~Take negative sign~~ \rightarrow $0.77014 - 61.033 = 0$

$$T_2 = \frac{0.1674636}{0.770141 - 61.03}$$

$$T_2 = 0.87616103$$

III) Gain.

$$G_S = \frac{1}{1 - T_S^2} = \frac{1}{1 - (0.872)^2}$$

$$G_S = 4.1733$$

$$G_S|_{dB} = 6.2048 \text{ dB.}$$

$$G_O = 18211 = (2.60) \stackrel{Q}{=} 6.76 = 8.299 \text{ dB}$$

$$\begin{aligned} G_L &= \frac{1 - |T_L|^2}{(1 - S_{22} T_L)^2} = \frac{1 - (0.876)^2}{(1 - [6.73.1 - 54])^2} \\ &= \frac{1 - (0.876)}{|0.87361 - 12.091|^2} \\ &= \frac{0.232624}{0.189576} = 1.67 \end{aligned}$$

$$G_L|_{dB} = 2.218 \text{ dB.}$$

$$G_T = G_S + G_O + G_L$$

$$G_T = 4.1733 + 6.76 + 1.67 = 12.6033$$

$$G_T|_{dB} = 6.2048 + 8.299 + 2.218 = 16.7 \text{ dB.}$$

Lumped Networks

1. Make sure one L and c

Capacitor Z_s

$$-1.789 \rightarrow 0.4$$

$$0.4 - (-1.789) = 2.189j = jB$$

$$X_c = \frac{1}{B} = \frac{1}{2.189j} = -0.4568j$$

$$\begin{aligned}\text{Normalized hence } X_c &= -0.4568j \times 50 \\ &= -22.8414j\end{aligned}$$

$$X_C = \frac{1}{j\omega C} = -88.8414j$$

$$X_C = \frac{-j}{\omega C} = -88.8414j$$

$$X_C = \frac{1}{\omega C} = 88.8414$$

$$X_C = \frac{1}{2\pi f C} = 88.8414$$

$$\frac{1}{2\pi f C} = 88.8414$$

$$\frac{1}{2\pi \times 4 \times 10^9} = 88.8414C$$

$$3.978873 \times 10^{-11} = 88.8414C$$

$$88.8414C = 3.978873 \times 10^{-11}$$

$$C = 1.07419 \text{ pF}$$

Inductor Z_L

$$-2 \rightarrow 0$$

$$0 - (-2) = 2j$$

$$j\omega L = 2j \times 50 \text{ (normalised)}$$

$$j\omega L = 100j$$

$$2\pi f L = 100$$

$$2\pi \times 4 \times 10^9 \times L = 100$$

$$100 = 2\pi \times 4 \times 10^9 L$$

$$L = 3.9788 \text{ nH}$$

FAR ZL

capacitor:

$$-0.583j \rightarrow 0.88j$$

$$0.88 - (-0.583) = 0.803j \Rightarrow B$$

$$X_C = \frac{1}{B} = -1.2453j.$$

$$\text{normalised } X_C = -62.266j$$

$$\frac{-j}{\omega C} = -62.266j$$

$$\frac{1}{2\pi f \times C} = 62.266$$

$$\frac{1}{2\pi \times H \times 10^9} = 62.266 C$$

$$3.978873 \times 10^{-11} = 62.266 C$$

$$62.266 C = 3.978873 \times 10^{-11}$$

$$C = 0.6390 \text{ pF}$$

Inductor

$$-5j \rightarrow 0j$$


$$0 - (-5j) = 5j \times 50 = 250j$$

$$j\omega L = 250j$$

$$2\pi \times 4 \times 10^9 L = 250$$


$$L = 9.947 \text{ nH}$$

Lumped Networks :

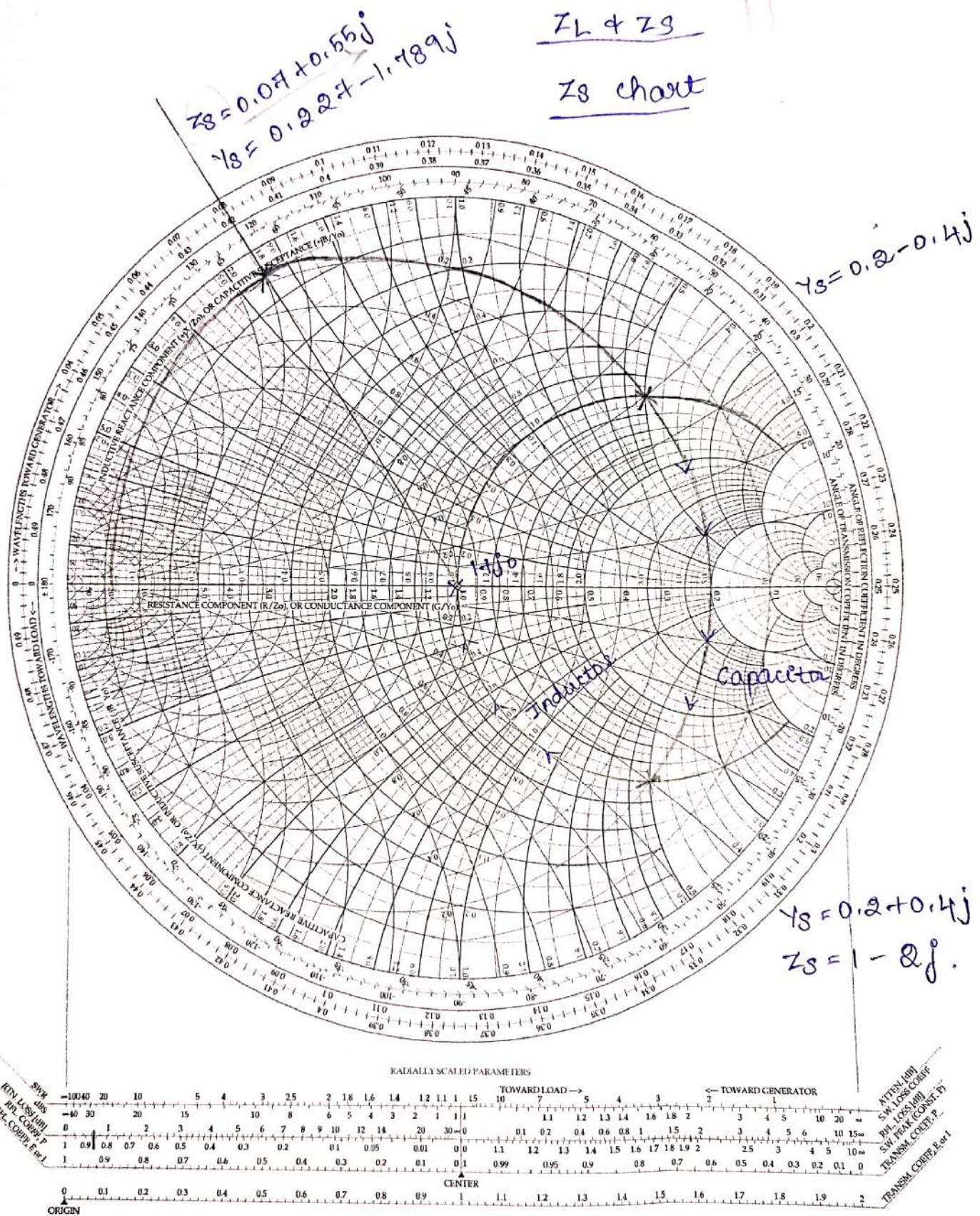

Z_L chart

90

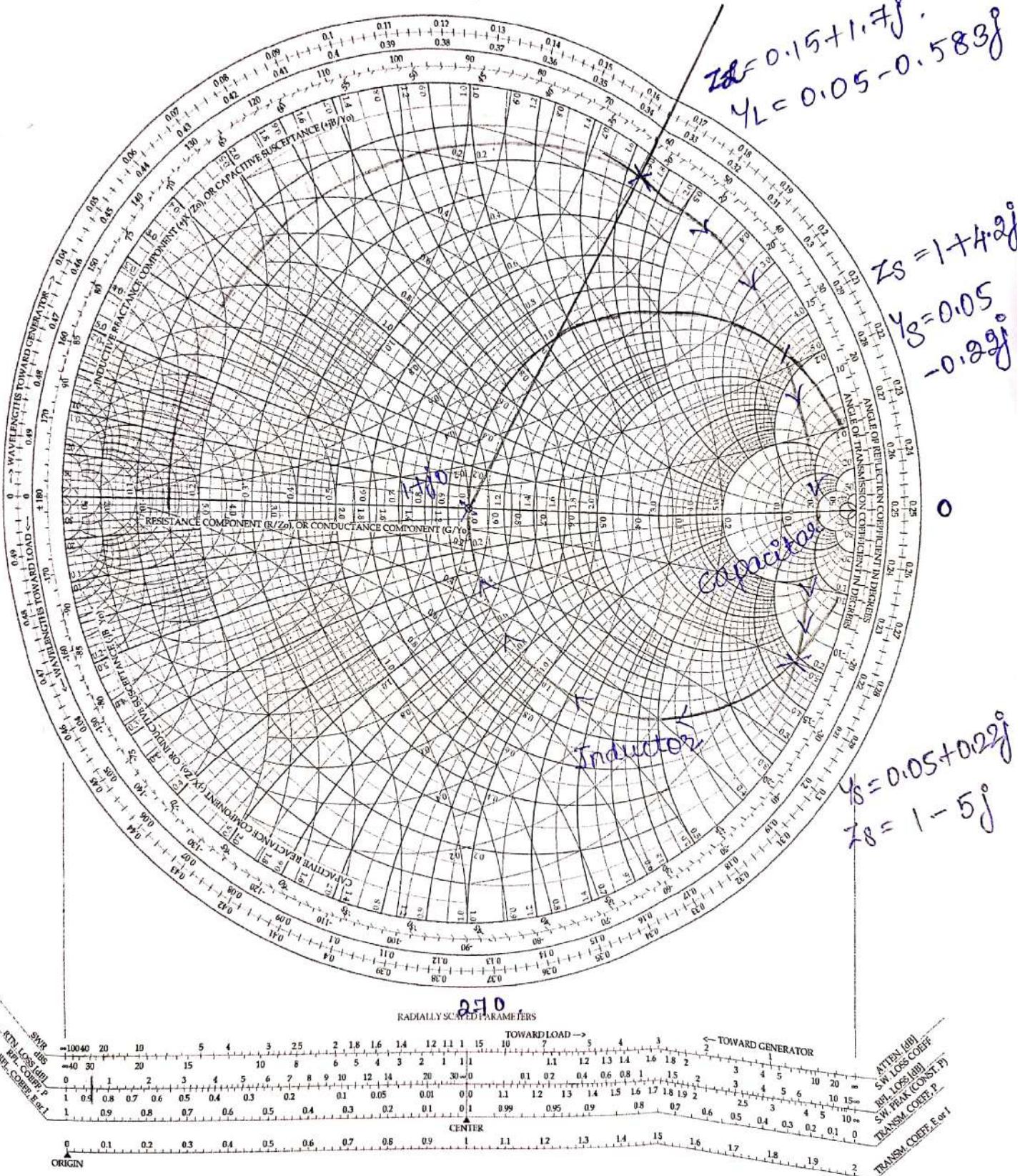

08.09.25

(optimum r_s, r_L picked up) stability
 Noise figure \rightarrow Gain \downarrow \rightarrow r_s (noise figure)
 choice of Biasing method (tuned) over optimum r_s, r_L

Low Noise Amplifier - Topology

+ common source LNA { Based on CMOS

+ common gate LNA { Technology due to


* Resistive load

* Resistive feedback load (match gain and stability)

* Inductive load \rightarrow power consumption less (useful)

In Resistive load \rightarrow more prone to power consumption not easy to achieve gain factor

common source - Resistive load

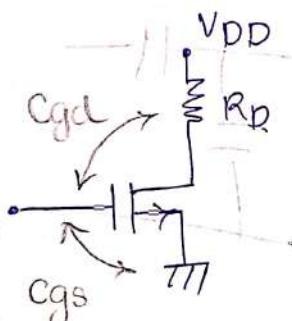

$$\text{Gain } (A) = g_m R_D$$

g_m = Transconductance

Due to Biasing - parasitic capacitance



generated on its own, to compensate we go with Impedance matching network

Generally \rightarrow degenerative

\rightarrow shunt reactive

$R_D \gg$ Effect of par cap

common source - resistive feedback load:

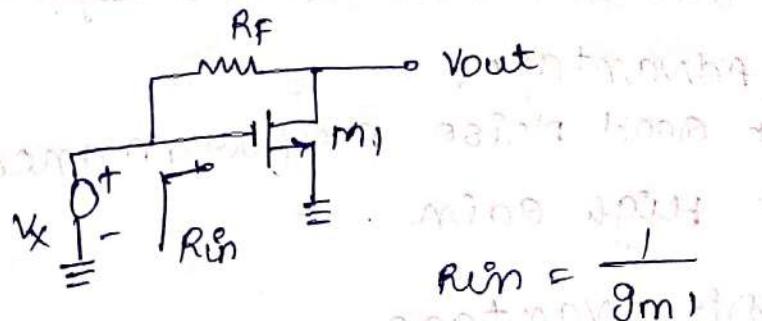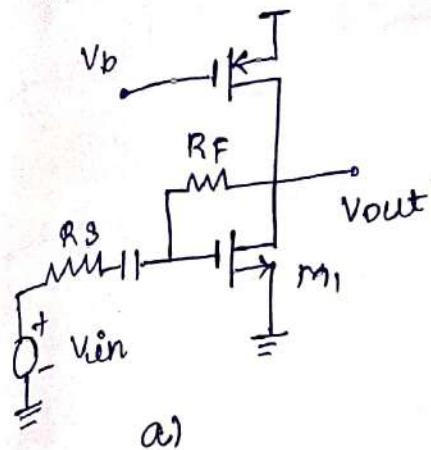



$$V_x = g_m V_{IN}, V_x R_F = V_{OUT}$$

$$AV = -\frac{R_F}{R_S}$$

$$\frac{V_{OUT}}{V_X} = 1 - \frac{R_F}{R_S}$$

Alternative: Inductive loads

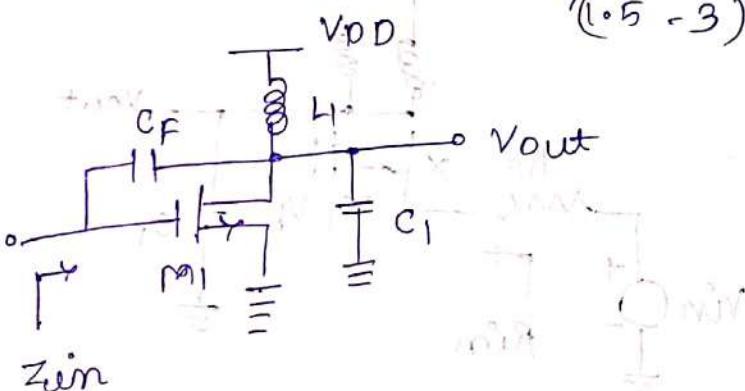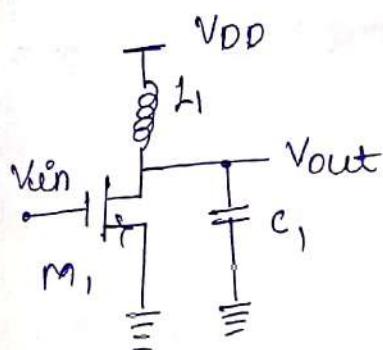common source - inductive load $NF = 1.3 / (1.5 - 3)$



- * Inductive load replaces a resistive load \rightarrow High impedance at operating frequency \rightarrow High gain without noise penalty of a resistor
- * Input matching achieved via gate inductance or source degeneration.
- * Voltage gain = $g_m L_1 \omega$

* feedback stabilizes the amplifier and improves linearity.


Advantage:

- + Good Noise performance
- + High gain

Disadvantage:

- Narrow Bandwidth
- poor stability in absence of matching
- sensitive in parasitic capacitance.

common Gate with Inductive Load

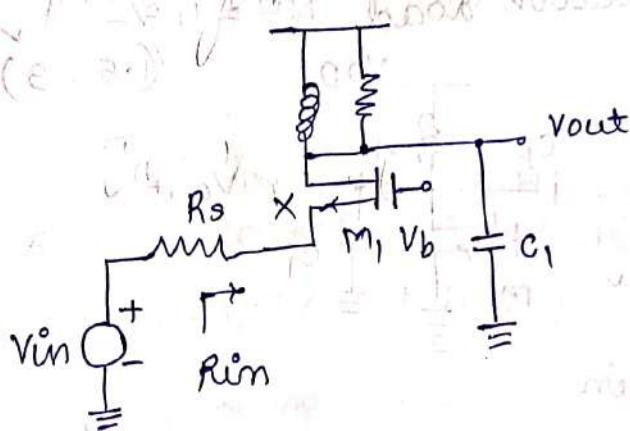

* Gate terminal is ac grounded, the input signal is applied to the source terminal and output taken from drain

* The Input impedance is low

* High stability

* broadband

* Easy impedance matching


Advantages:

- * Low input impedance for easy matching
- * High stability
- * Low sensitive to parasitic capacitors


Disadvantages:

- * power consumption trade-off
- * Dependence on transconductance.
- Reason to move from common source to common gate
- * Broadband operation is needed (Eg. UWB, 802.11)
- * Stability is critical especially at high frequencies
- * Linearity is prioritized over noise figure in interference-heavy environment
- * Design simplicity and reduced component count are desired particularly in cost sensitive or wide band applications
- * High frequency performance is required, when parasitics heavily impact the design.

Cascode LNA:

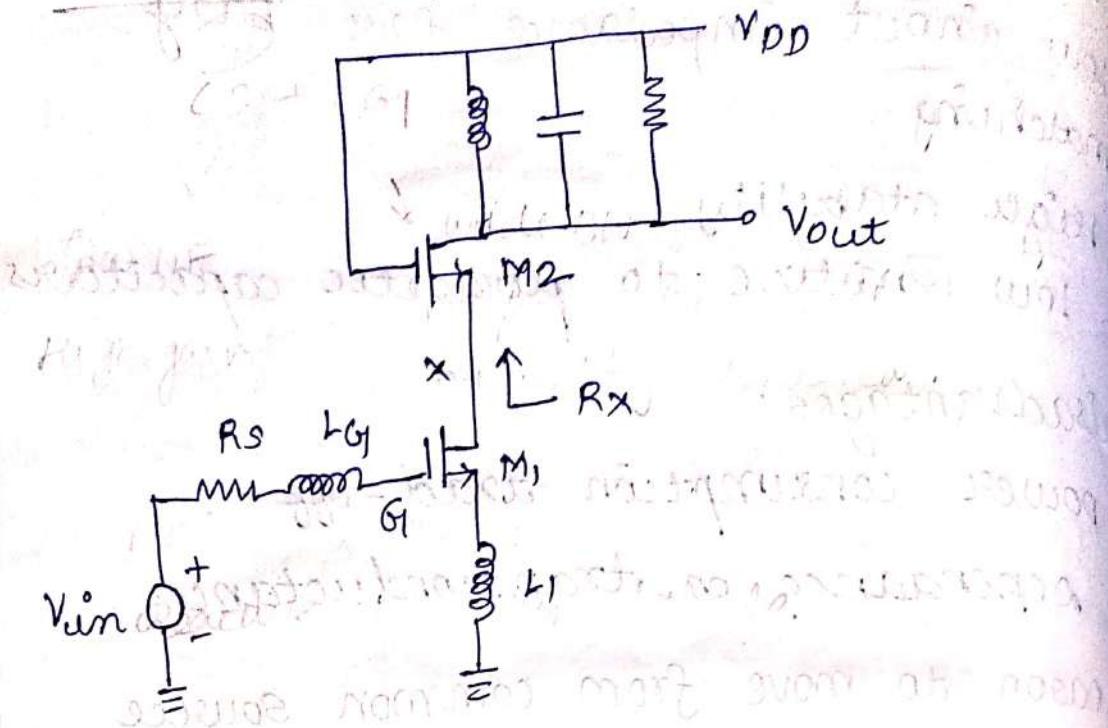

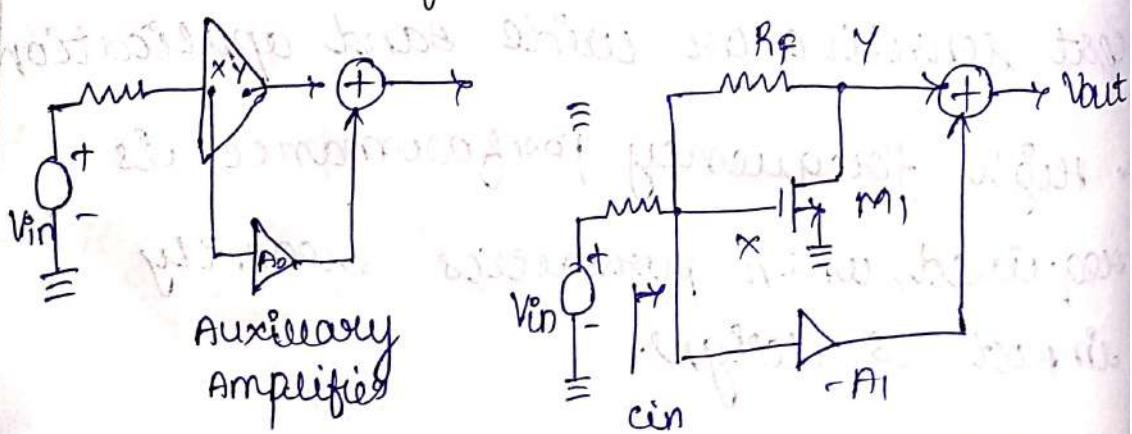- * The cascode LNA is maximum used in RF-front end designs.
- * It combines the strength of common source (CS) and common gate (CG) stages to achieve balance a low noise, high stability
- * It is a two stage amplifier consisting of a CS transistor followed by a CG transistor.
- Noise cancelling LNA



$$A_1 = 1 + R_F / R_S$$

Reactance cancelling LNA:

- + Reactance cancelling involves adding reactive components that are equal in magnitude but opposite in phase to unwanted reactances which neutralises the effects.
- + source degeneration inductance:
Inductance in series with source of transistor which cancel out input capacitance of transistor to improve input impedance matching.

09.09.85

- to show the parameter to find Γ_{in}
- + $\Gamma_{in} = \text{Gain, NF (Balance) we see}$ - or for optimum Γ_{in} the best able
 - + what might be Γ_{in} to achieve Gain & NF
 - + check for stability
 - + If conditional find out range using Smith chart

Noise circle:

$c_{noise} = \text{complex in}$

Nature

$$\text{SIC}_{noise} = \frac{\Gamma_{opt}}{1+N}$$


$$\sigma_{noise} = \sqrt{\frac{N(N+1) - |\Gamma_{opt}|^2}{1+N}}$$

$$N = (F_{\text{target}} - F_{\text{min}}) / (1 + \Gamma_{\text{opt}})$$

$$(NF)^{\text{dB}}_{\text{target}} = 10 \log F_{\text{target}}$$

F_{min} = minimum NF possible to achieve through device

$$\frac{R_n}{50} = g_n$$

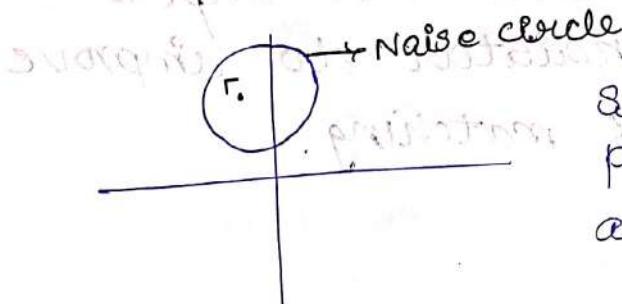

since Inside possible to achieve NF.

5. For a frequency of 2GHz and $Z_0 = 50\Omega$, draw a noise circle for 1dB, 2dB and 3dB employing HEMT

min NF is 0.6 dB ($NF_{\text{min}} = 0.6 \text{ dB}$) and

$R_n = 4\Omega$, possible optimum ref' coeff

$\Gamma_{\text{opt}} = 0.30 L^{-45^\circ}$ R_n : Internal resistance

$\Gamma_{\text{opt}} = 0.218 - j0.218$ g_n : Normalised Internal resistance.

and the parameters are

$$S_{11} = 0.46 L^{-35^\circ}$$

$$S_{12} = 0$$

$$S_{21} = 100dB, 15dB, 20dB$$

$$S_{22} = 0.50 L^{-10^\circ}$$

$$F_{\text{target}} = 1, 2, 3 \text{ dB}$$

$$\text{Gain target} = 100 \text{ dB}, 15, 20 \text{ dB}$$

scale
Let $F_{target} = 2 \text{ dB} \Rightarrow \text{Noise Figure}$

$$F_{target} = 10^{2/10} = 1.58 \checkmark$$

$$NF_{min} = 0.6 \text{ dB} \checkmark$$

$$F_{min} = 10^{0.06} = 1.148 \checkmark$$

$$N = \frac{(1.58 - 1.14) |1 + (0.412 - j0.212)|^2}{4 \times 4/50}$$

$$N = \frac{(0.44)(1.2305)^2}{4 \times 0.08} = \frac{0.44 \times 1.514}{0.32}$$

$$\boxed{N = 2.081}$$

$$C_{noise} = \frac{0.30 L^{-45^\circ}}{1 + 2.08} = 0.0974 L^{-45^\circ}$$

$$R_{noise} = \frac{\sqrt{N(N+1) - 1} P_{opt} l^2}{1 + N}$$

$$= \frac{\sqrt{2.08(3.08) - 10.31^2}}{1 + 2.08}$$

$$= \frac{\sqrt{6.4064 - 0.09}}{3.08} = \frac{2.51324}{3.08}$$

$R_{noise} = 0.81598 \text{ (measured)}$ Not in scale through RF port Smith chart

Gain margin

$$g_s = \frac{G_1}{G_{\text{opt}}} \quad G_{\text{target}} = 20 \text{ dB} = 100$$

$$G_{\text{opt}} = 821 = 13 \text{ dB} = 398.107$$

$$g_s = \frac{100}{398.107} = 0.25118875$$

$$C_G = \frac{s_{11}^* g_s}{1 - [(1-g_s) |s_{11}|^2]} = \frac{(0.46135)(0.25118875)}{1 - [(1 - 0.25118875)(0.46)^2]}$$

$$= \frac{0.09465 + 0.06627j}{0.841551539}$$


$$= 0.11247 + 0.07874 = 0.137135$$

$$R_S = \frac{\sqrt{1-g_s} (1 - |s_{11}|^2)}{1 - [(1-g_s) |s_{11}|^2]} = \frac{\sqrt{1-0.25118875}}{\frac{(1 - (0.46)^2)}{0.841551539}}$$

$$R_S = \frac{0.8653388 \times 0.7884}{0.841551539}$$

$R_S = 0.81068$

Low Noise Amplifier

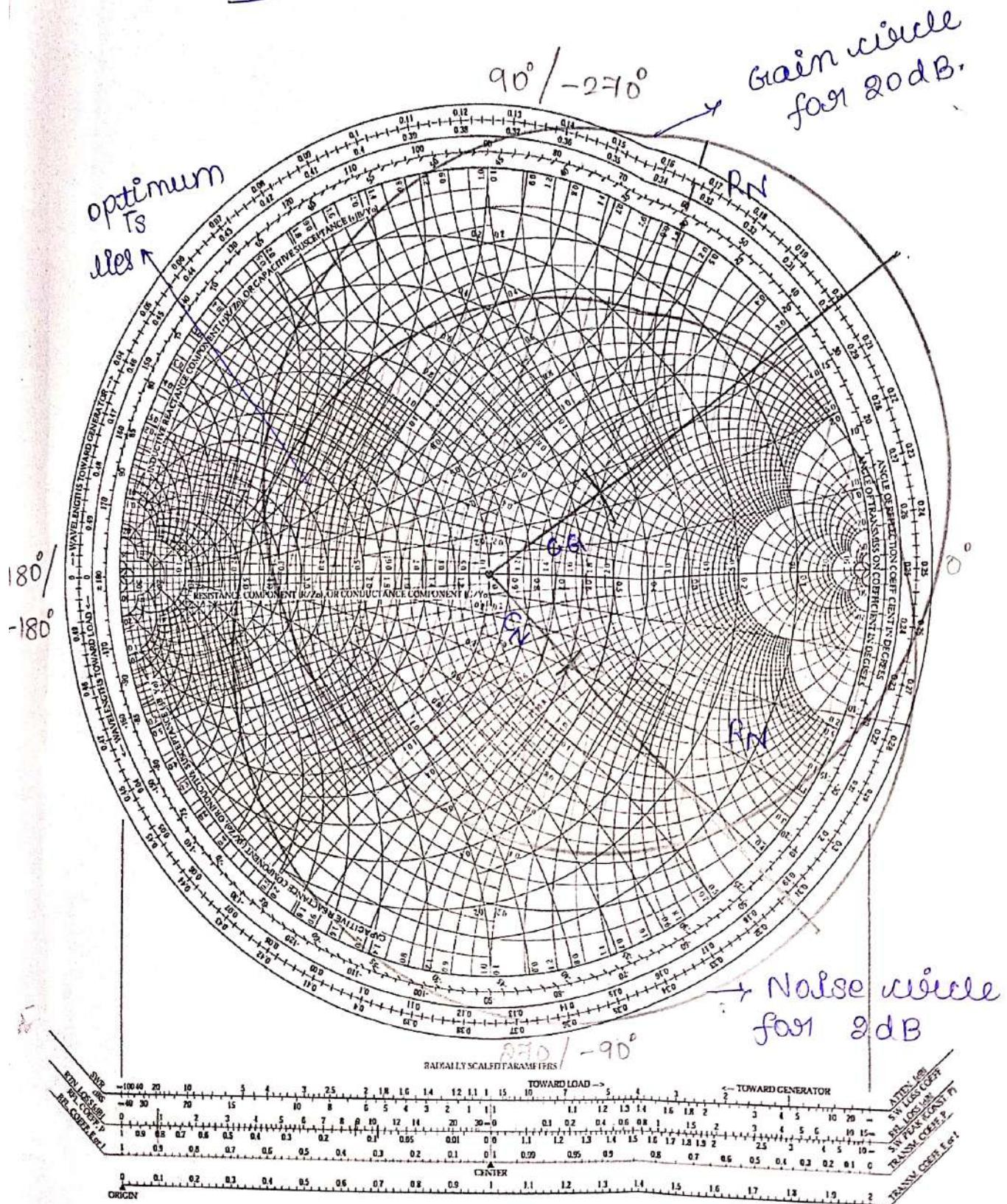

1. Mark angle of C_S , C_N and then measure value from the ref coeff P and plot, make the new point as center
2. With the radius R_S & R_N , measure from ref coeff and draw circle from new center (Intersection)

Stability:

i) $K - \Delta$ Test

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

$$\Delta = 0.23 \angle -45^\circ$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$$

$K = \text{not defined.}$

10.09.25

power amplifier:

- device in stable mode
- linearity maintenance
- n^{th} stage before antenna


Homogeneous principle

$$y = nx$$

$$\alpha \cdot y = \alpha nx$$

DC power gets modulated based on the input signal → Amplification.

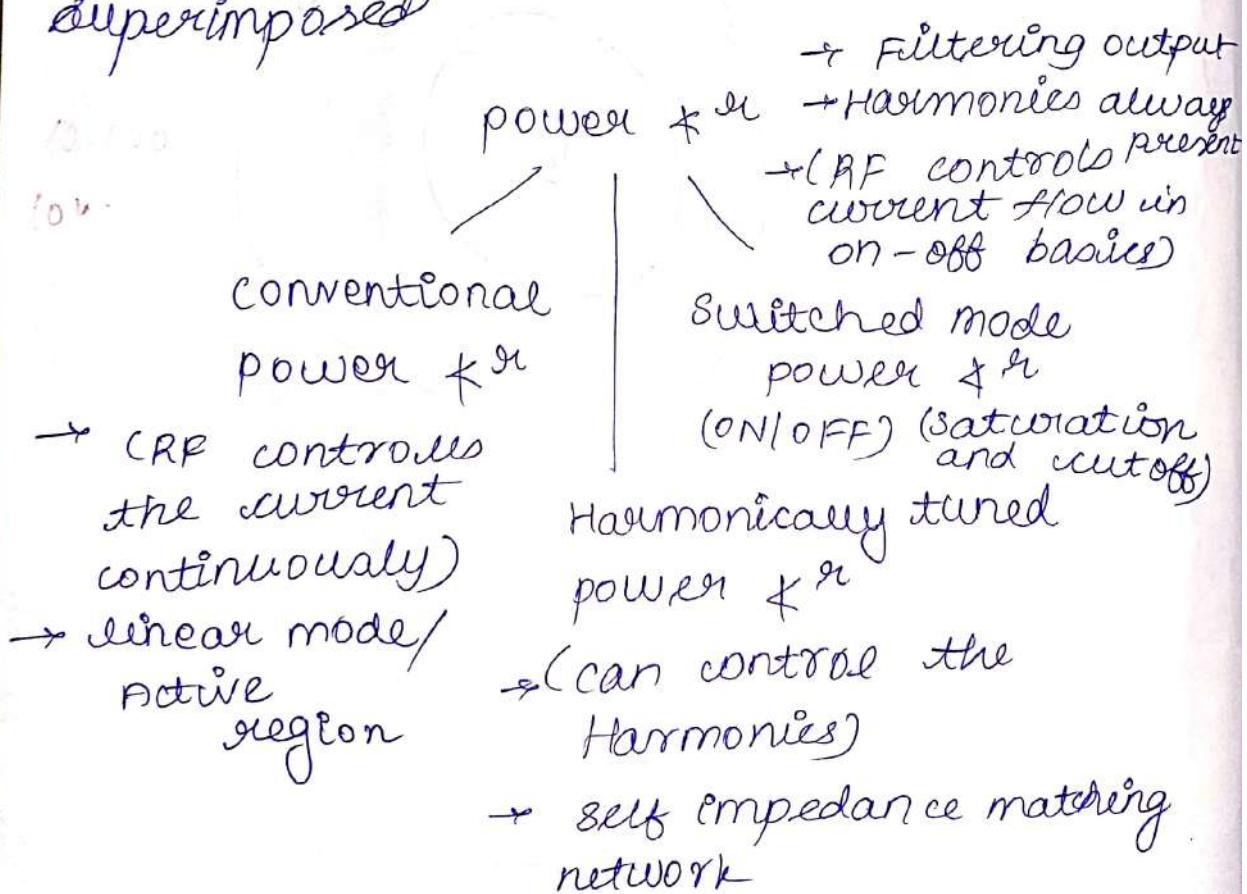RF modulates the input that DC power with RF input DC power gets superimposed



conventional $\eta \text{ (mod)}$ \downarrow linearity \uparrow

- class A (50% duty cycle Phase angle 180°)
- class B (phase angle $> 90^\circ \Rightarrow \eta = 80\%$)
- class C (phase angle $< 90^\circ \Rightarrow \eta = 90\%$)
- class AB
- cross over distortions

switched mode (Inductive load) $\eta \text{ (mod)}$ power \downarrow

- class D (Balanced Amplifiers) linearity (mod)
- class E (single ended)


harmonically tuned (Inductive load) $\eta \uparrow$ wider BW.

- F (odd no. of harmonics) power \downarrow
- F $^{-1}$ (Even harmonics) linearity (mod)
- T (2nd harmonics)

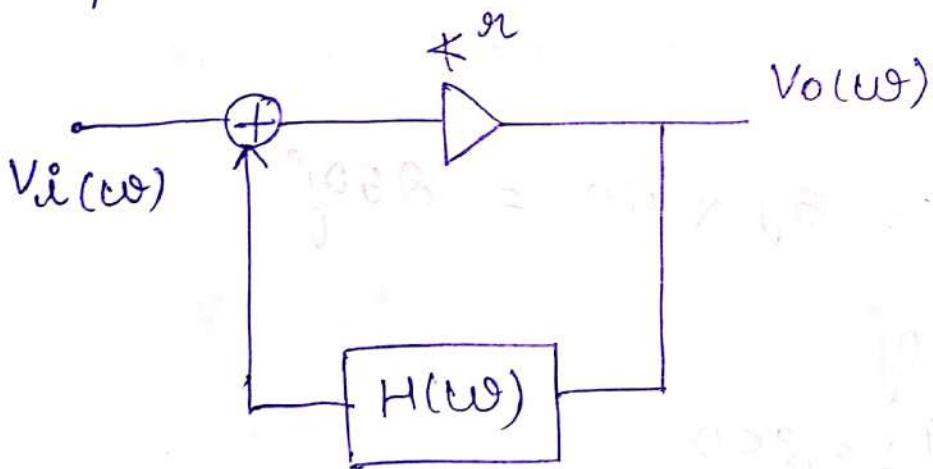15.09.25

Microwave oscillators:

- Non linear circuits
- Absence of input there is a possibility of output.
- It converts DC power to AC waveforms
- Amplifier circuit which has frequency dependant feedback which is given as input



$$V_o(\omega) = A V_i(\omega) + V_o(\omega) H(\omega) V_i(\omega)$$

$$\frac{V_o(\omega)}{V_i(\omega)} = \frac{A}{1 - AH(\omega)}$$

$$V_o(\omega) = \frac{A}{1 - AH(\omega)}, V_i(\omega)$$

$$V_i(\omega) = AV_i(\omega) = V_o(\omega) - A V_o(\omega) H(\omega)$$

$$V_o(\omega) = A V_i(\omega) + A V_o(\omega) H(\omega)$$

on making characteristic Equation zero.

Nyquist criteria $1 - AH(\omega) = 0 \Rightarrow$ At any one of frequency zero o/p

Barkhausen $AB = 1$ still o/p present.

$$If V_i(\omega) = 0$$



$$V_o(\omega) = A V_o H(\omega)$$

$$V_o(1 - AH(\omega)) = 0$$

→ Ensure that stability criteria damping at one point becomes zero and becomes stable

one part Negative resistance oscillator

GUNN } Negative resistance
IMPACT }

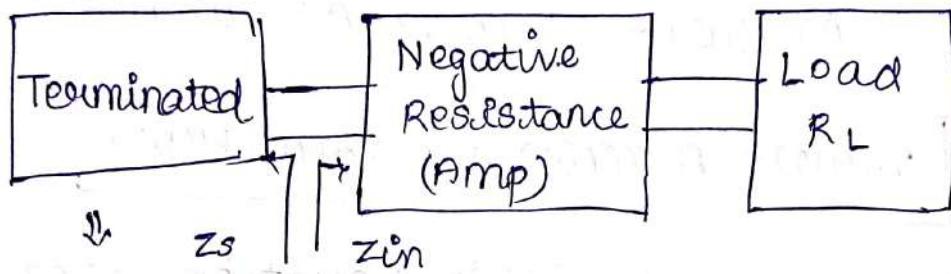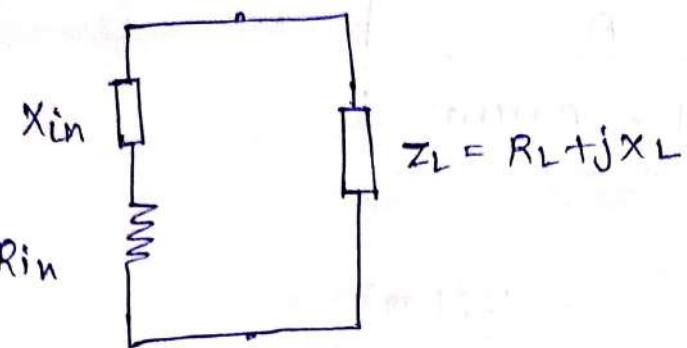

$$1 + H(j\omega) A = 0$$

NR device \rightarrow Amplifier $\rightarrow \Gamma_{in}, \Gamma_{out}$

compute
to find
stability
circle
region
with
50 Ω
imped.

Impedance matching Network

$\Gamma_{out} \leftrightarrow \Gamma_e$

dumped (or) stub

Apply KVL for the circuit

$$Z_{in} = X_{in} + R_{in}$$

Impedance \Rightarrow depends on I/V & frequency

$$Z_{in}(I, j\omega) = X_i(I, j\omega) + R_{in}(I, j\omega)$$

$$Z_L = R_L + jX_L$$

KVL

$$I(R_{in} + X_{in}) + IZ_L = 0 \Rightarrow I(Z_{in} + Z_L) = 0$$

$$\text{If } Z_L + Z_{in} = 0$$

then

$$Z_L = -Z_{in}$$

In RF I should be present hence
 $I \neq 0$ hence

$$Z_L + Z_{in} = 0$$

$$R_L + R_{in} = 0$$

$$X_L + X_{in} = 0$$

In what $R_L \uparrow$ then $R_{in} \downarrow$ hence balanced to yield 0.

If $R + ve \Rightarrow$ dissipation occurs

$R - ve \Rightarrow$ Energy source

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_L = \frac{-Z_{in} - Z_0}{-Z_{in} + Z_0}$$

$$\Gamma_L = \frac{-(Z_0 + Z_{in})}{-(Z_{in} - Z_0)} = \frac{-(Z_0 + Z_{in})}{Z_0 - Z_{in}}$$

$$\Gamma_L = -\frac{1}{\Gamma_{in}}$$

For unstable

R_{in} dep on I & f_w

ct.

$$R_{in} + R_L < 0$$


$$R_{in}(I, f_w) + R_L < 0$$

To make this stable, if slight variation in current (ΔI) and frequency (Δs)
 $s = \alpha + j\omega$
remains the same point.

ΔI & $\Delta s \rightarrow$ leads to damp out,
reduces damping oscillation makes out

stable

$\Delta I, \Delta s$ variation

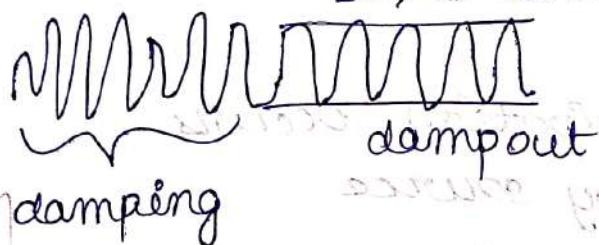

$$\frac{\partial \operatorname{Re}(Z_{in})}{\partial I} - \frac{\partial \operatorname{Im}(Z_L)}{\partial \omega} - \frac{\partial \operatorname{Im}(Z_{in})}{\partial I} \cdot \frac{\partial \operatorname{Re}(Z_L)}{\partial \omega} > 0$$

$$R_S = -\frac{R_{in}}{3}$$

$$X_S = -X_{in}$$

source

possibility of

osc?

$R_S \rightarrow$ possible to construct high osc. circuit

$$T_S = -T_{in} \text{ (proper Termination)}$$

1. Suppose a part of which uses negative resistance device whose $T_{in} = 1.85 \angle 40^\circ$, $Z_0 = 50\Omega$ for freq of 6 GHz. What should be the load matching network.

$$\text{soln: } T_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$Z_{in} = Z_0 \cdot \frac{1 + T_{in}}{1 - T_{in}}$$

$$Z_{in} = -44 + j123$$

$$T_{in} = -Z_{in}$$

$$Z_L = 44 + j123$$


$$T_{in} = 1.85 \angle 40^\circ$$

$$Z_{in} = 50 \angle 111.24^\circ$$

Load


Neglect

$$T_{in} = 1$$

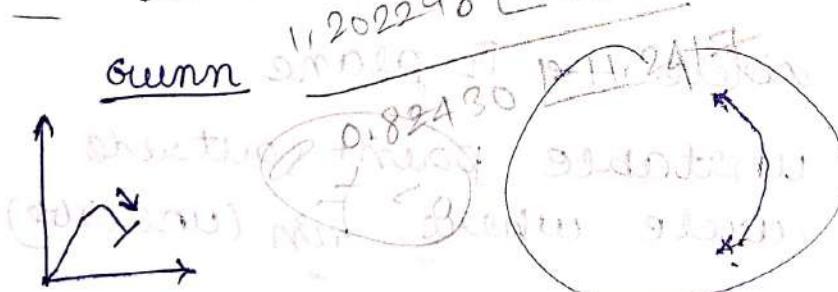

$$R_s = R_{in}$$

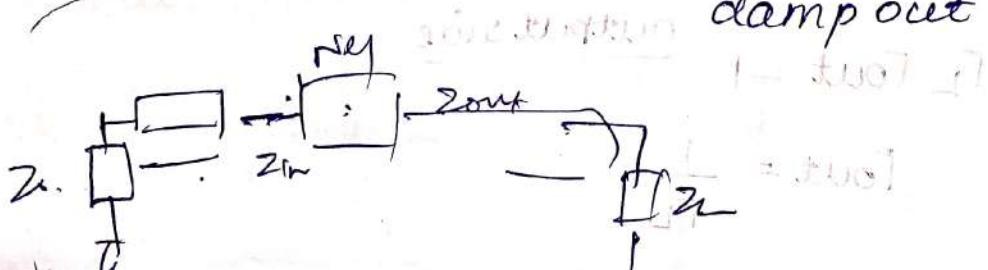$V \uparrow I \downarrow$ provides negative resistance \rightarrow Achieve $R_s \downarrow$ damp out.




17.09.85

Transistor oscillator

1. Highly unstable device designed.

MOSFET - common source

2. Identify Γ_L

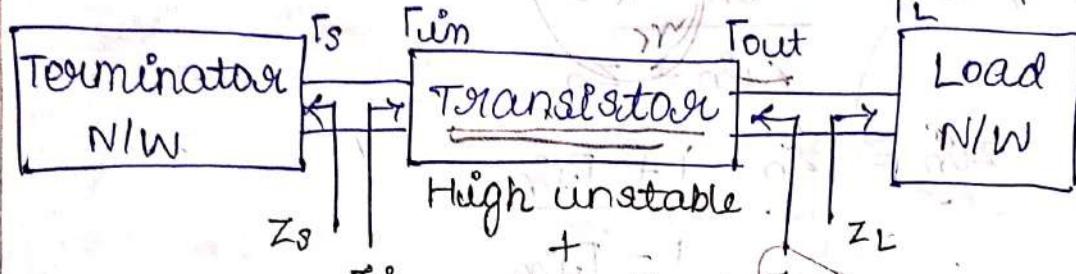

Jumped elements

stubs

dielectric resonators

To ensure unstability, input impedance
unstable

→ stability circle → Γ_L plane

if $\Gamma_L < 1$, unstable point outside
circle where Γ_{in} (unstable)

condition of oscillation

$$\Gamma_s \Gamma_{in} = 1$$

$$\Gamma_{in} = \frac{1}{\Gamma_s}$$

$$\Gamma_L \Gamma_{out} = 1 \quad \text{output side}$$

$$\Gamma_{out} = \frac{1}{\Gamma_L}$$

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{1}{\Gamma_S}$$

$$\frac{1}{\Gamma_S} = \frac{S_{11} - S_{11}S_{22}\Gamma_L + S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$= \frac{S_{11} - \Gamma_L (S_{11}S_{22} - S_{12}S_{21})}{1 - S_{22}\Gamma_L}$$

$$\frac{1}{\Gamma_S} = \frac{S_{11} - \Delta\Gamma_L}{1 - S_{22}\Gamma_L} \quad \Delta = S_{11}S_{22} - S_{12}S_{21}$$

$$1 - S_{22}\Gamma_L = S_{11}\Gamma_S - \Delta\Gamma_L\Gamma_S$$

$$\Gamma_L [S_{22} - \Delta\Gamma_S] = 1 - \Gamma_S S_{11}$$

$$\boxed{\Gamma_L = \frac{1 - \Gamma_S S_{11}}{S_{22} - \Delta\Gamma_S}}$$

$$T_{in} \Rightarrow Z_{in} = R_{in} + jX_{in}$$

↓

$$x_S = -X_{in}$$

$$R_S = -\frac{R_{in}}{3}$$

$$\text{Output} \Rightarrow Z_L = -Z_{out}$$

Dielectric resonators:

